



IIT ROORKEE



NPTEL ONLINE  
CERTIFICATION COURSE

# Charging Infrastructure

## Lecture-16


### Closed Loop Control of Single-phase Boost PFC Converter-IV

Dr. Apurv Kumar Yadav

Department of Electrical Engineering



# Recap

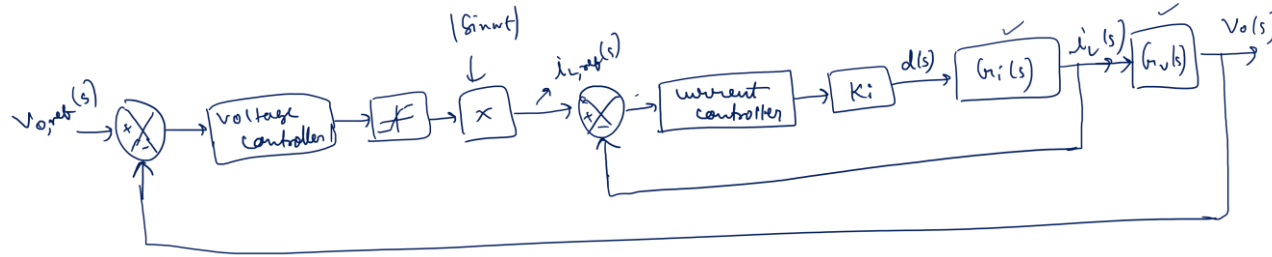

$$G_i(s) = \frac{i_L(s)}{d(s)}$$

$$G_v(s) = \frac{V_o(s)}{i_L(s)} \approx \frac{V_L(s)}{i_L(s)}$$

$$\left. \frac{\tilde{i}_L(s)}{\tilde{d}(s)} \right|_{V_s(s)=0} = \frac{|V_s|}{R_L(1-D)^2} \left[ \frac{R_L C s + 2}{s^2 L C (1-D)^2 + \frac{s}{R_L(1-D)^2} + 1} \right] = G_i(s)$$


## Power balance

$$\Rightarrow \frac{V_{s,pk}}{\sqrt{2}} \cdot \frac{I_{s,pk}}{\sqrt{2}} = V_o \cdot i_{conv}$$

$$\Rightarrow i_{conv} = \frac{V_{s,pk} I_{s,pk}}{2 V_o} \rightarrow (1)$$

$$\Rightarrow \tilde{i}_{conv}(s) = \frac{V_{s,pk}}{2 V_o} \tilde{i}_L(s) \quad \left( \begin{array}{l} |\tilde{v}_s| = 0 \\ V_o \rightarrow \text{is the operating point} \end{array} \right) \rightarrow (2)$$

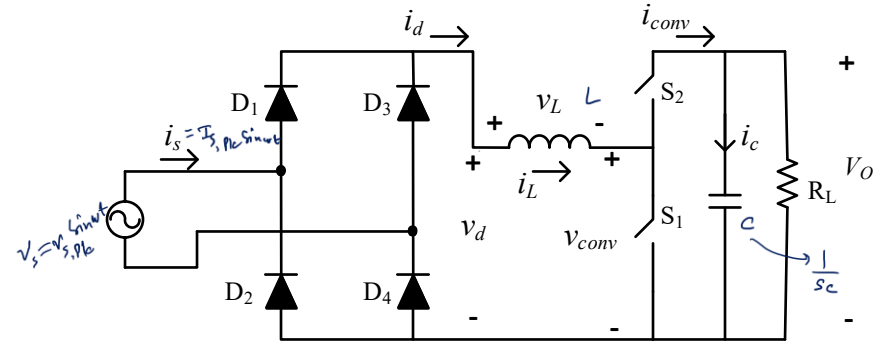
$$\begin{aligned} \Rightarrow \tilde{V}_o(s) &= \tilde{i}_{conv}(s) \cdot \left( \frac{R_L}{R_L s + 1} \right) \\ &= \tilde{i}_{conv}(s) \left[ \frac{R_L}{R_L s + 1} \right] \\ \tilde{V}_o(s) &= \frac{V_{s,pk}}{2 V_o} \tilde{i}_L(s) \left[ \frac{R_L}{R_L s + 1} \right] \end{aligned}$$




$$\Rightarrow \frac{\tilde{V}_o(s)}{\tilde{i}_L(s)} = \frac{V_{s, pk}}{2V_o} \left[ \frac{R_L}{R_L C s + 1} \right] \Big|_{\tilde{V}_s = 0}$$

$$\Rightarrow G_{v,i}(s) = \frac{V_{s, pk}}{2V_o} \left[ \frac{R_L}{R_L C s + 1} \right]$$



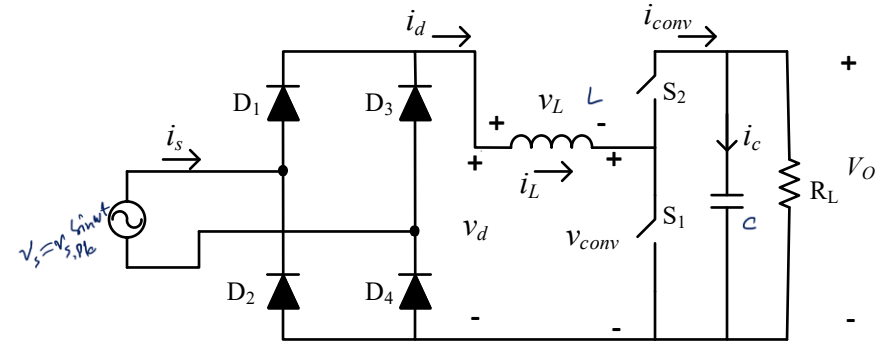
Gain,  $k_i = \frac{\text{Peak value of (control voltage)} \rightarrow \text{duty}}{\text{Peak value of input current}}$



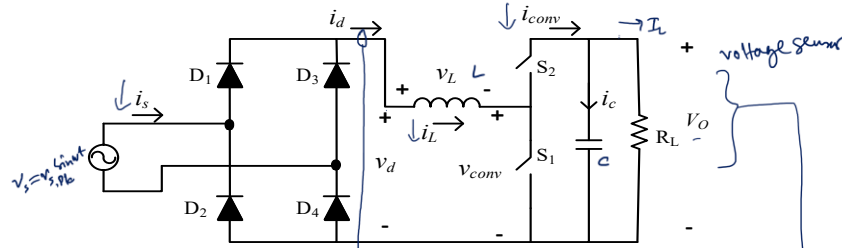


switching frequency ( $f_{sw}$ ) is kept constant  
 $0 < d < 1$

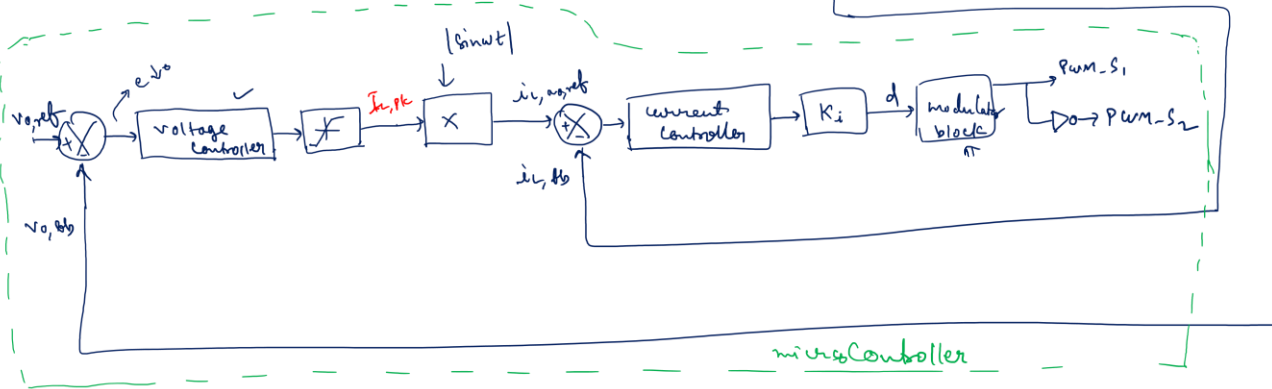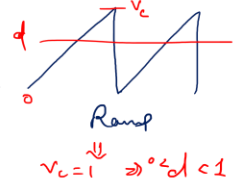
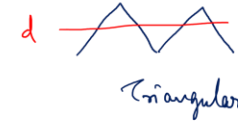
→ carrier signal → triangular or ramp  
 Carrier



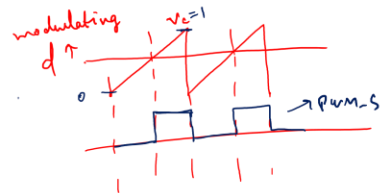$f_c \gg f_s$   
 $\Rightarrow f_c \gg f_m$




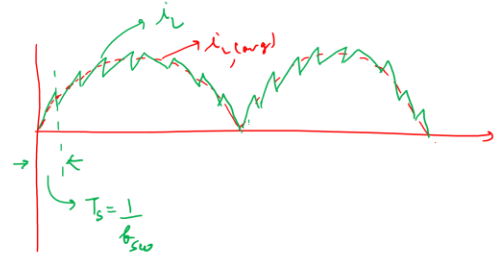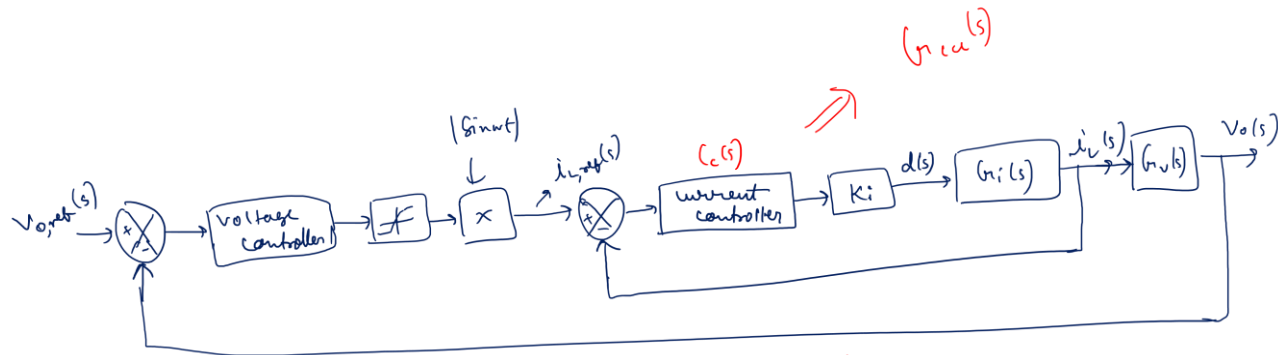Carrier  $\rightarrow$  modulating  
 $PWM_{S1} = 1$   
 Carrier  $<$  modulating  
 $PWM_{S1} = 0$



inner current loop is faster than the outer voltage loop

this is a "2fs" varying signal

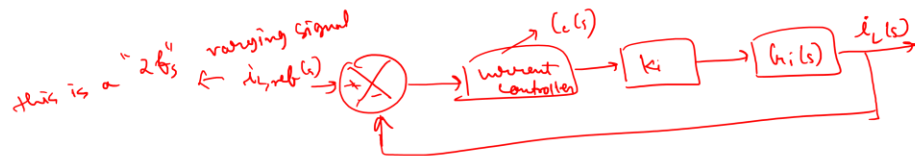

open loop T.F. of inner current loop  $\Rightarrow C(s) \cdot K_i \cdot G_i(s)$


$$\begin{aligned} \text{Ref} &\rightarrow \text{Summing Junction} \rightarrow e \rightarrow C(s) \rightarrow P(s) \rightarrow o/p \\ \Rightarrow \frac{o/p}{\text{Ref}} &= \frac{C(s)P(s)}{1 + C(s)P(s)} \Rightarrow C(s) \cdot P(s) \gg 1 \\ &\Rightarrow \frac{o/p}{\text{Ref}} = \frac{C(s)P(s)}{C(s)P(s)} = 1 \\ &\Rightarrow o/p = \text{Ref} \end{aligned}$$

① The current controller must be designed to track the "2fs" component  $\Rightarrow$  the gain of open loop transfer function must be very high at "2fs"

②  $B \cdot \omega_i \ll \omega_{sw} \approx B \cdot \omega_i = \frac{\omega_{sw}}{10} \Rightarrow$  good attenuation at ' $\omega_{sw}$ ' frequency

③ Sufficient PM, GM (PM = 35° to 60°)
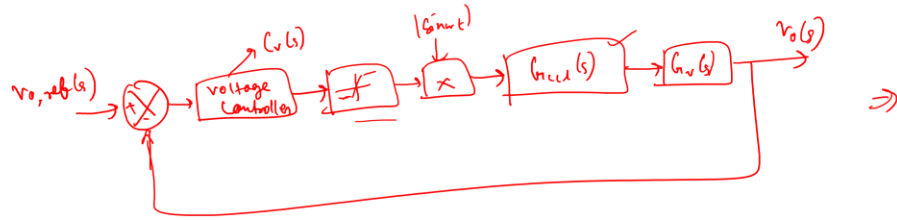
$$\Rightarrow G_{\text{cell}}(s) = \frac{C_c(s) \cdot K_i \cdot G_i(s)}{1 + C_c(s) \cdot K_i \cdot G_i(s)}$$



$$\Rightarrow \text{open loop T/F for voltage loop} = C_v(s) \cdot G_{\text{cell}}(s) \cdot G_v(s)$$

Criteria for voltage controller



- ① The very high gain at  $s=0$
- ② B.W.  $\approx 20-40\text{Hz}$

The switching freq. is constant  
 $\Rightarrow$  constant frequency control

Other control methods

① Peak current control  $\rightarrow$  variable frequency case

② Variable hysteresis control

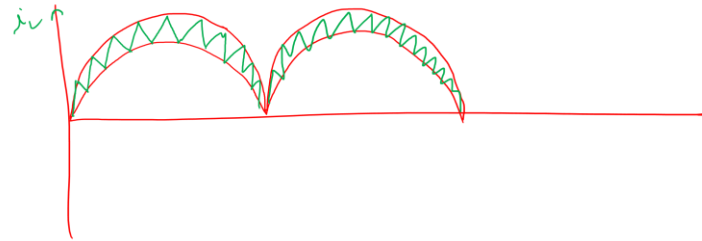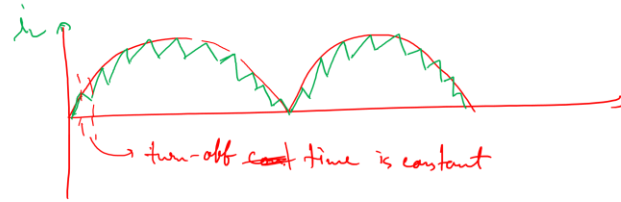



# Thank You

