



IIT ROORKEE



NPTEL ONLINE
CERTIFICATION COURSE

Charging Infrastructure

Lecture-5

Revisiting Diode Bridge Rectifier

Dr. Apurv Kumar Yadav
Department of Electrical Engineering



Recap

1. EV ecosystem $\begin{cases} \rightarrow \text{Low voltage Batteries (48v-72v)} \\ \rightarrow \text{High voltage Batteries (350v-500v)} \end{cases}$
2. DC charger \rightarrow DC EVSE (power conversion unit is kept outside the vehicle) \rightarrow off-board charger
3. AC charger \rightarrow AC EVSE (power conversion is taking place on the vehicle using an OBC)
4. Types of charger \rightarrow modes of charging, charger plugs, level of charging station.

AC-DC Converters

AC-DC Converter Requirement/need


- ① Conversion from AC voltage source to DC
- ② The controlled / regulated DC output voltage (the level of voltage can also be controlled) at the desired level
- ③ The current drawn from the source must have a unity power factor.
- ④ Current drawn must be having a sinusoidal variation.
(nearly)
- ⑤ Harmonic content should be less means THD is less.

1- ϕ input, 1- ϕ AC-DC Converter
3- ϕ input, 3- ϕ AC-DC Converter


1- ϕ Diode Bridge Rectifier (uncontrolled Rectifier)

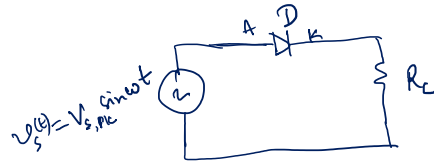(i) Half-bridge Rectifier (ii) full-bridge Rectifier

1- ϕ Half-bridge rectifier with Resistive load



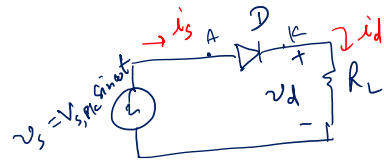'D' turns on when the ' v_s ' is in the positive half; it is reverse biased when ' v_s ' is in the negative half cycle.



$$v_d = \begin{cases} v_s, & v_s > 0 \\ 0, & v_s < 0 \end{cases}$$

average value of v_d , $V_{d,avg} = \frac{1}{T} \int_0^{T/2} (V_{s,pk} \sin \omega t) \cdot dt$

$$= \frac{V_{s,pk}}{\omega T} \left[-\cos \omega t \right]_0^{T/2}$$

$$= \frac{V_{s,pk}}{\omega T} \left(-\left(\cos \frac{\omega T}{2} - \cos 0 \right) \right)$$

$$= \frac{V_{s,pk}}{2\pi} \left(-\left(\cos \pi - \cos 0 \right) \right)$$


$$= \frac{V_{s,pk}}{2\pi} \left[-(-1-1) \right]$$


$$V_{d,avg} = \frac{V_{s,pk}}{\pi}$$

$$\omega = 2\pi b_s \quad (b_s = \text{supply frequency})$$

$$\Rightarrow T = \frac{1}{b_s}$$

$$\Rightarrow \omega T = 2\pi$$

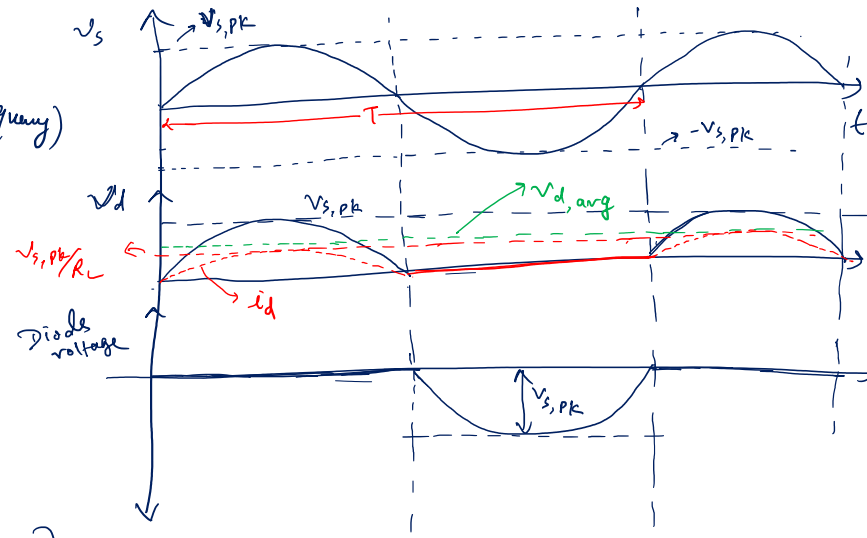

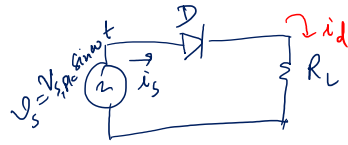


$$i_s = \begin{cases} i_d & ; v_s > 0 \\ 0 & ; v_s < 0 \end{cases}$$

Diode selection

v/g ratings

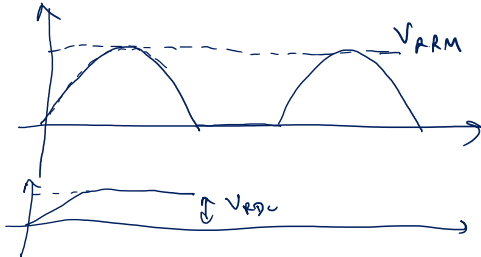- Peak repetitive reverse voltage (V_{RRM})
- Peak reverse voltage
- Reverse voltage or DC blocking voltage



Current ratings

- Average forward current, $I_{F(av)}$
- Average rectified forward current
- Repetitive peak forward current, I_{FRM}
- Non-Repetitive peak forward current, I_{FSM}
- I^2t rating

$I \rightarrow$ RMS value of forward current
 $t \rightarrow$ the time period of the pulse

Diode selection

voltage rating

$$\rightarrow \text{Peak repetitive reverse voltage } (V_{RRM}) = V_{s, pk}$$

$$\rightarrow I_{F, avg} = \frac{V_{s, pk}}{\pi R_L}$$

$$\rightarrow I_{F, rms} = \sqrt{\frac{1}{T} \int_0^{T/2} \left(\frac{V_{s, pk} \sin \omega t}{R_L} \right)^2 dt}$$

$$I_{F, rms} = \frac{V_{s, pk}}{2 R_L}$$

Thank You

