



IIT ROORKEE



NPTEL ONLINE
CERTIFICATION COURSE

Charging Infrastructure


Lecture-8

Revisiting Diode Bridge Rectifier with Capacitive Filter-II

Dr. Apurv Kumar Yadav

Department of Electrical Engineering



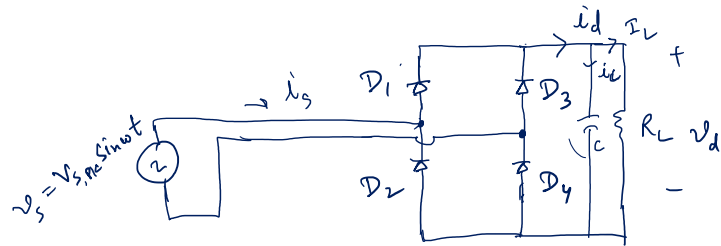


$$C = \left(1 - \frac{t_c}{T_{r2}}\right) \times \frac{P_L}{2V_o \cdot \Delta V_o} \times \frac{1}{f_s}$$

$$t_c = t_b - t_a$$

$$V_o = \frac{V_{dmax} + V_{dmin}}{2}$$

$$\Delta V_o = V_{dmax} - V_{dmin}$$

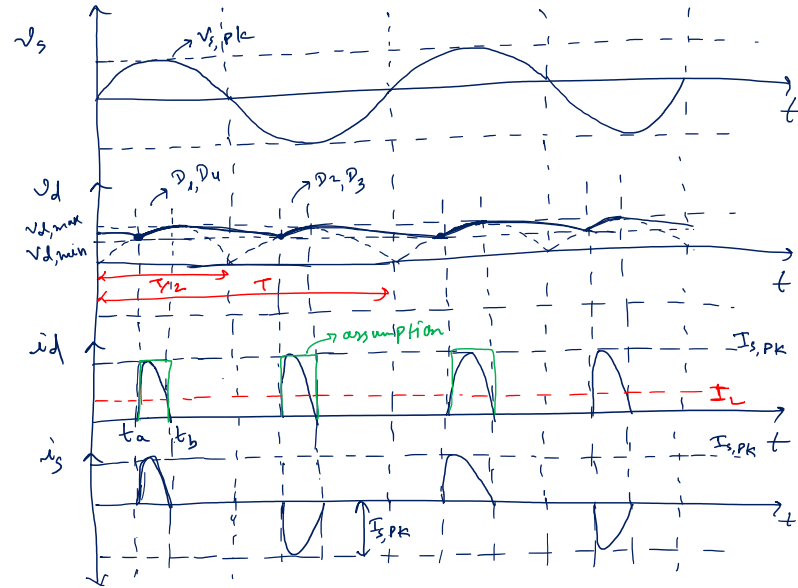

$$T = 1/f_s$$

$$\omega = 2\pi f_s$$

$$\Rightarrow \omega T = 2\pi$$

$$I_L = \frac{P_L}{V_0}$$

$$I_L = I_{S,PK} \frac{t_c}{T/2}$$

$$\Rightarrow I_{S,PK} = \frac{T/2}{t_c} \cdot \frac{P_L}{V_0}$$

$$\Rightarrow I_{S,PK} = \frac{T/2}{t_c} \cdot \frac{P_L \times 2}{V_{d,max} + V_{d,min}}$$

$$\Rightarrow \text{if } V_{d,max} \approx V_{d,min}$$

$$\Rightarrow t_c \rightarrow 0$$

$$\Rightarrow I_{S,PK} \rightarrow \infty \text{ (very high value)}$$

During t_c'
 $I_{C,rms} = (I_{s,pk} - I_L) \times \sqrt{\frac{t_c}{T/2}}$

During $t_c - T/2$
 $I_{C,rms} = I_L \times \sqrt{1 - \frac{t_c}{T/2}}$

$$\Rightarrow I_{C,rms} = \sqrt{(I_{s,pk} - I_L)^2 \frac{t_c}{T/2} + I_L^2 \left(1 - \frac{t_c}{T/2}\right)}$$


\Rightarrow for Capacitor selection

\rightarrow Voltage rating of Capacitor $= V_o + \frac{\Delta V_o}{2} = V_{s,pk}$

$\rightarrow C = \left(1 - \frac{t_c}{T/2}\right) \times \frac{P_L}{2V_o \cdot \Delta V_o} \cdot \frac{1}{f_s}$

\rightarrow RMS current rating $\Rightarrow I_{C,rms} = \sqrt{(I_{s,pk} - I_L)^2 \frac{t_c}{T/2} + I_L^2 \left(1 - \frac{t_c}{T/2}\right)}$

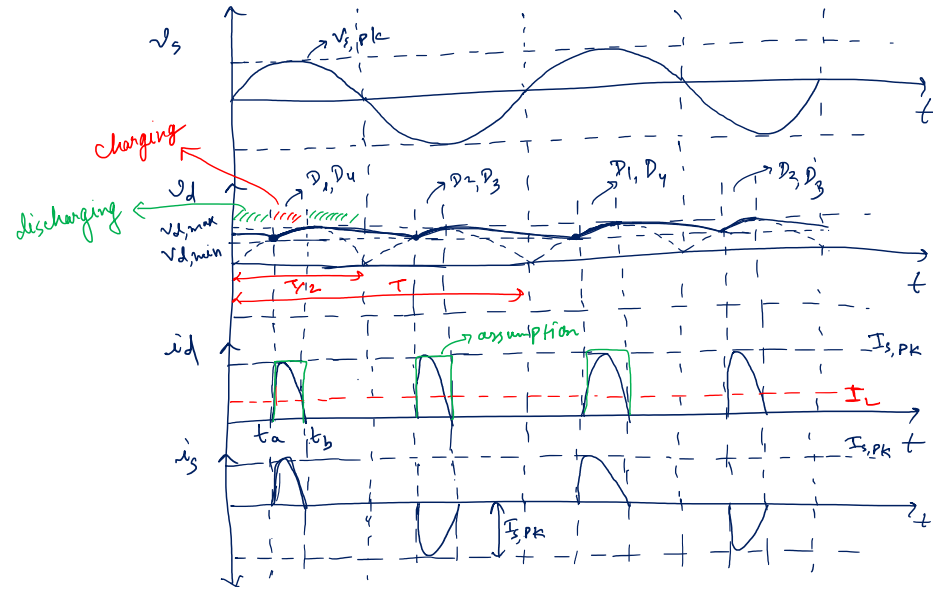\hookrightarrow determine the parallel-combination of capacitance



Diode Selection

$$V_{RAM} = V_{S, pk} = V_o + \frac{\Delta V_o}{2}$$

$$\text{Peak forward current} = I_{S, pk}$$

$$\text{Average forward current} = I_{S, pk} \times \frac{t_c}{T}$$

D_1, D_2, D_3, D_4

$$\text{RMS current} = I_{S, pk} \times \sqrt{\frac{t_c}{T}}$$

$$V_{d, max} \approx V_{d, min}$$

$$\Rightarrow \Delta V_o \rightarrow 0$$

$$\Rightarrow t_c \rightarrow 0$$

$$\Rightarrow C \uparrow$$

$$\Rightarrow I_{C, rms} \uparrow$$

$$\Rightarrow I_{S, pk} \uparrow$$

Disadvantage

- ① The peaky current drawn from the source, it includes a lot of harmonics.
- ② The current drawn is at non-unity.
- ③ The oversizing of the components

Advantage

The output voltage is nearly constant (varying within the permissible limit)




Learnings

- ① The unity power factor of the drawn current can be achieved when the load is purely resistive and the power is being delivered in both the +ve and -ve half cycle.
- ② The output voltage can be made nearly constant (within the permissible limit) by putting the output capacitive filter,
↳ the current drawn becomes non-sinusoidal.

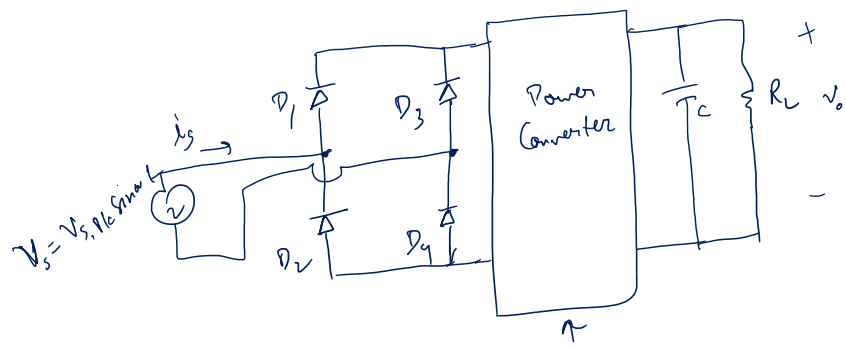Thus, to obtain unity power factor current drawn along with regulated voltage, the power factor correction converter is used.





Thank You

