



IIT ROORKEE



NPTEL ONLINE
CERTIFICATION COURSE

Charging Infrastructure

Lecture-17


Bridgeless PFC Converter

Dr. Apurv Kumar Yadav

Department of Electrical Engineering




Recap

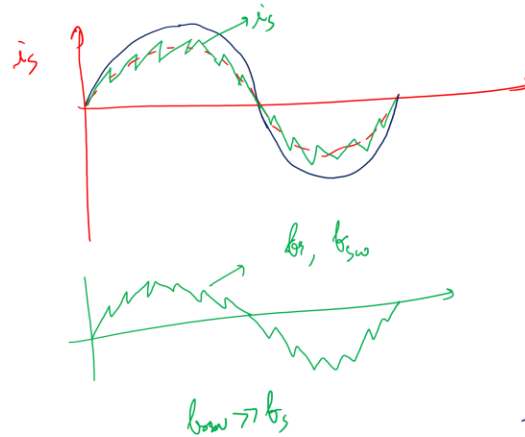

⇒ higher component count
⇒ 3 devices in conduction

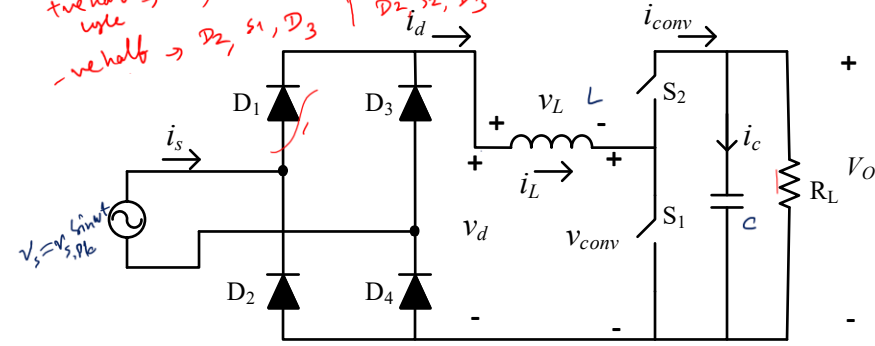
D_{TS}
 true half cycle $\rightarrow D_1, S_1, D_4$
 -ve half $\rightarrow D_2, S_1, D_3$
 $(1-D)T_s$
 D_1, S_2, D_4
 D_2, S_2, D_3




$$v_d = |v_{s,pk} \sin \omega t|$$

full-bridge
rectifier





Boost
converter

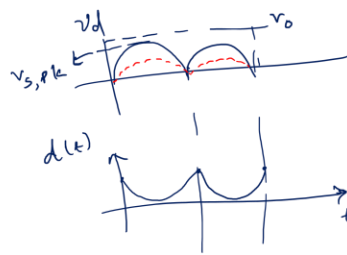

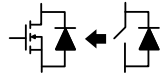

4 devices

Bridgeless PFC

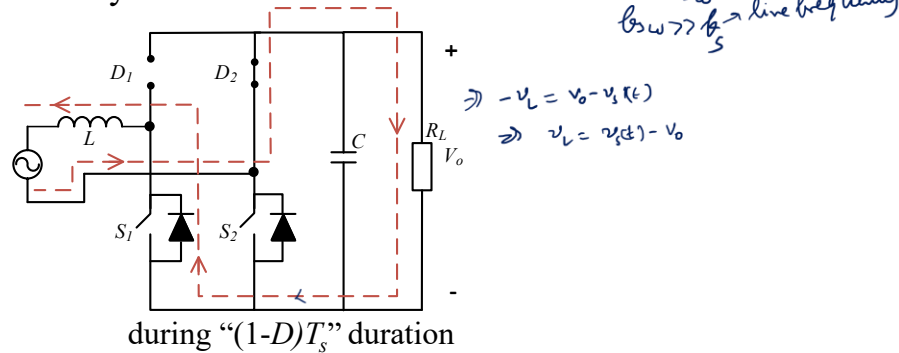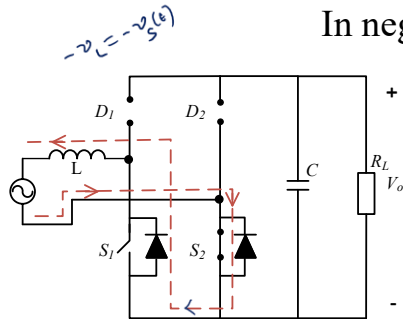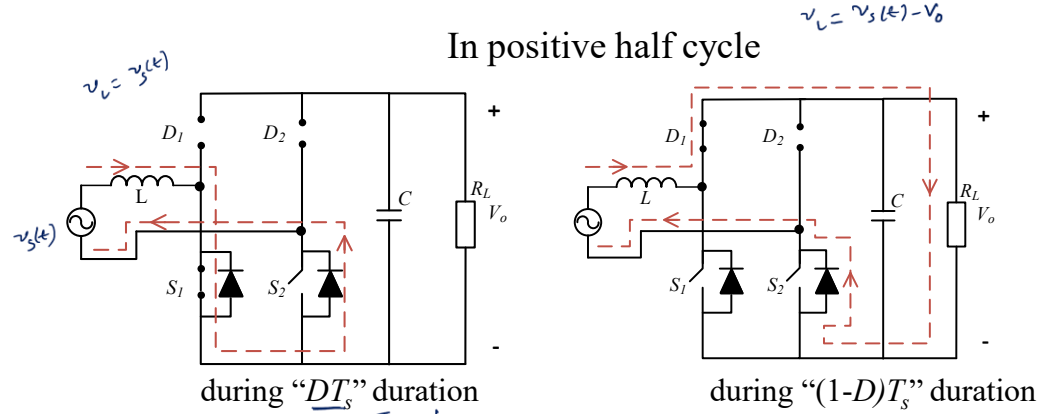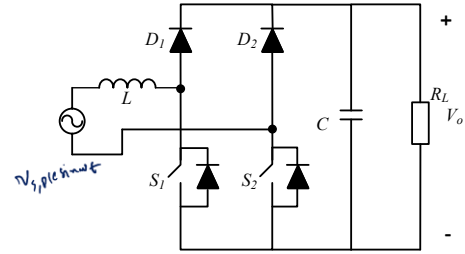

Bridgeless PFC

2nd +ve half cycle

$$\frac{DT_s}{V_L = V_s}$$

$$\frac{(1-D)T_s}{V_L = V_s - V_o}$$

2nd -ve half cycle

$$\frac{DT_s}{V_L = V_s}$$

$$\frac{(1-D)T_s}{V_L = V_s - V_o}$$

$$\Rightarrow \frac{DT_s}{V_L = |V_s|}$$

$$\frac{(1-D)T_s}{V_L = |V_s| - V_o}$$


$$\Rightarrow d(t) = 1 - \frac{|V_{s, \text{rms}} \sin \omega t|}{V_o}$$

$$\Rightarrow \begin{aligned} d_{S_1}(t) &= d(t), & V_s > 0 \\ &= 0, & V_s < 0 \end{aligned}$$

$$\Rightarrow \begin{aligned} d_{S_2}(t) &= 0, & V_s > 0 \\ &= d(t), & V_s < 0 \end{aligned}$$

\Rightarrow At any given instant, two devices are in conduction


Bridgeless PFC

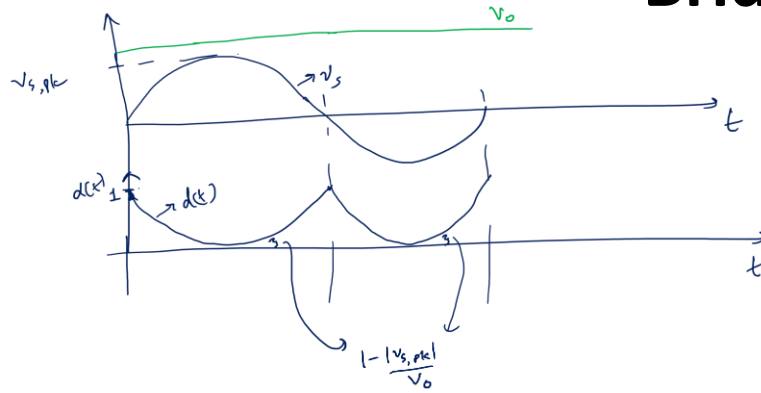


- ⇒ At any time instant, only 2 devices are in conduction
- ⇒ Only 4 devices need to be used

Disadvantage

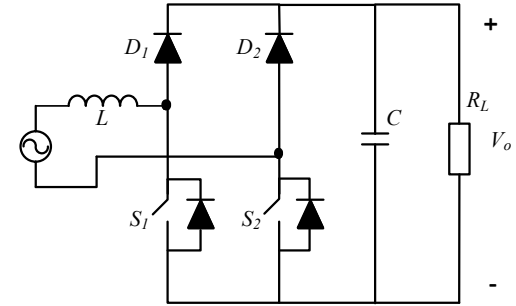- ① Diodes need to switch at t_{sw} ($t_{sw} \gg t_s$), thus fast recovery diode need to be used \Rightarrow higher losses associated with diode




Totem pole PFC

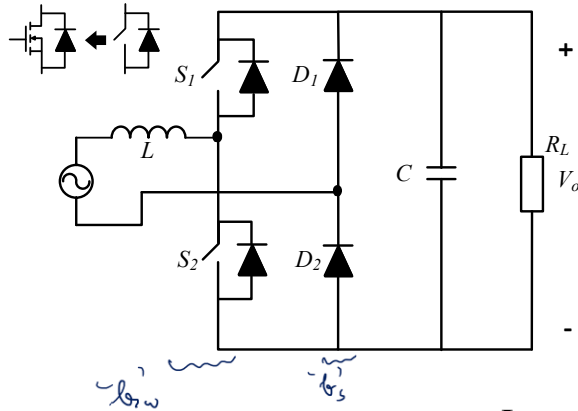


+ $t_{sw} \gg t_s$

- $\Rightarrow d(t) = 1 - \frac{|V_{s, \text{pk}} \sin \omega t|}{V_o}$

In positive half cycle ($v_s > 0$)

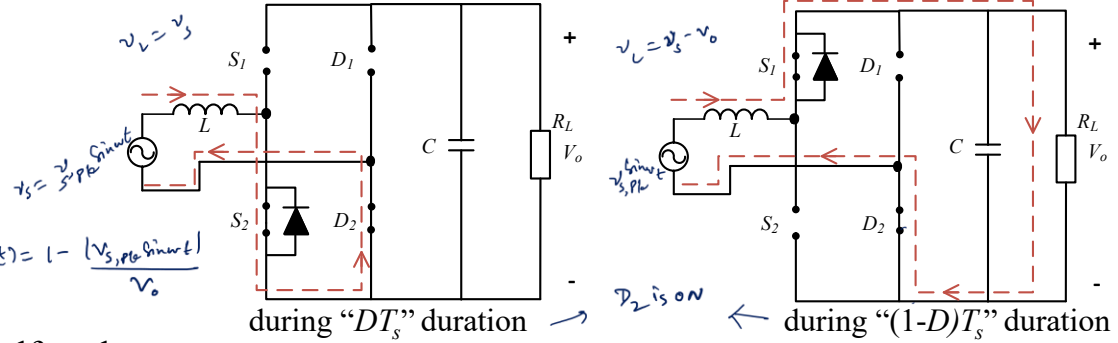

In negative half cycle

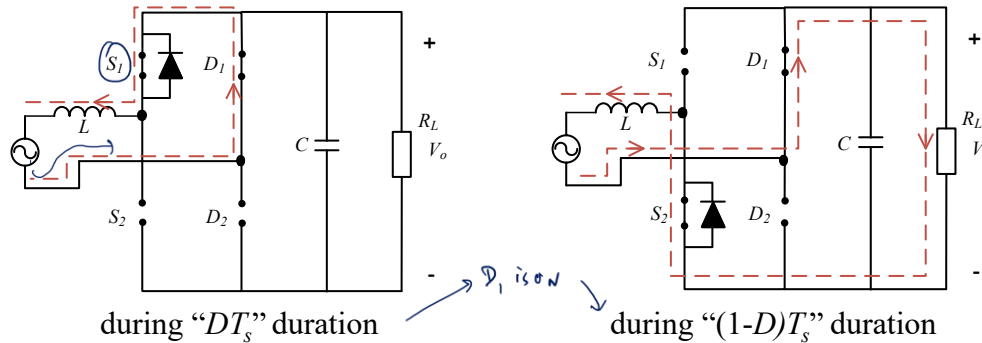

Totem pole PFC

→ It has two legs, where one of the legs are fast switching leg, while the other one is slow switching leg.

In positive half cycle, (always D_2 is on)

$$ds_1 = 1 - d(t)$$


$$ds_2 = d(t)$$

In negative half cycle, (always D_1 is on)

$$ds_1 = d(t)$$

$$ds_2 = 1 - d(t)$$

$$d(t) = 1 - \frac{|V_{s,ref} \sin \omega t|}{V_o}$$

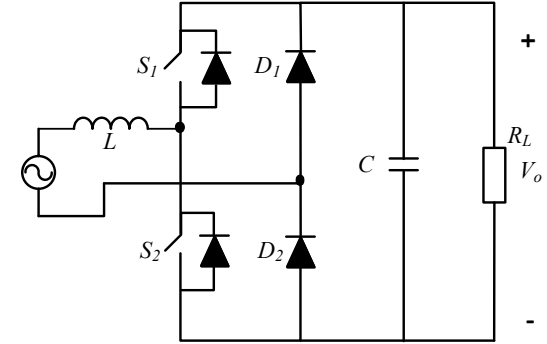

Thank You

