



IIT ROORKEE



NPTEL ONLINE
CERTIFICATION COURSE

Charging Infrastructure

Lecture-35


Modulation Strategies for PWM Full Bridge Converter

Dr. Apurv Kumar Yadav

Department of Electrical Engineering




turning on S_2 (Gate pulse to S_2)

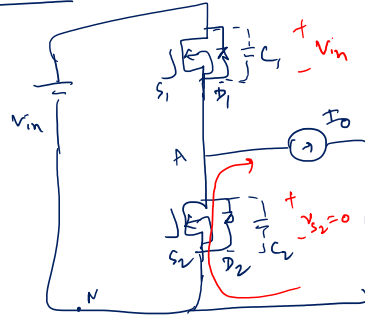

$$i_{S2} = I_0$$

Recap

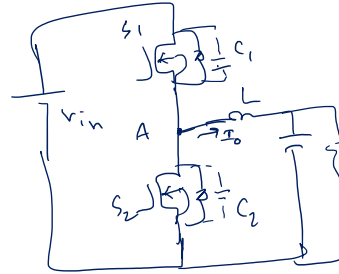

ZVS of Switch S_2
during turn-on of S_2


Soft-switching of S_2

$$\Rightarrow P_{sw(on)} = 0 ; \text{ limited } \frac{dv}{dt} = \frac{I_0}{C_1 C_2}$$

Sufficient deadtime is provided such that V_{C2} goes to 0, simultaneous V_{C1} goes to $V_{in} \Rightarrow$ required condition


The necessary condition is
 
$$L I_0^2 > C_1 V_{in}^2 + C_2 V_{in}^2$$



Recap

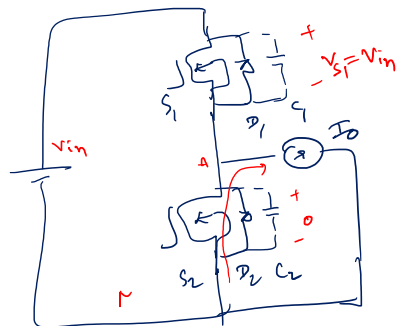When S_1 is turning on (going from off to on)




S_1 is off

S_2 is ON


$$I_o = i_{s2}$$

$$V_{AN} = 0$$

\Rightarrow

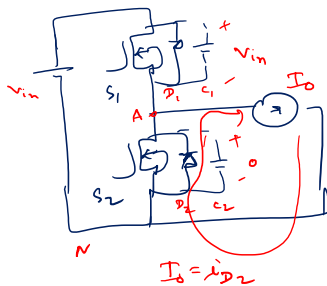

\Rightarrow

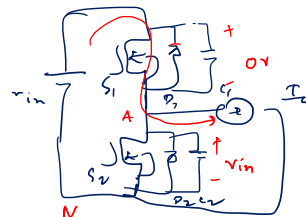

$$I_o = i_{s1}$$

Some non-zero $P_{sw(on)}$

S_1 is on

S_2 is OFF

$$\Rightarrow V_{AN} = V_{in}$$

S_1 is OFF

S_2 is OFF


deadtime

$$V_{AN} \approx 0$$


\Rightarrow Some non-zero $P_{sw(on)}$

\Rightarrow high $\frac{dv}{dt}$

\Rightarrow hard-switching of S_1


 


Full-bridge Converter

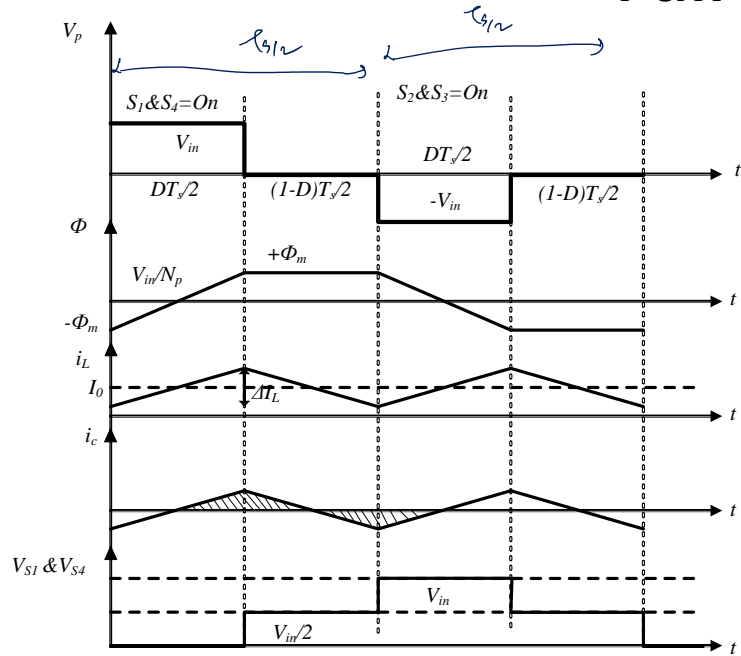


$$n = \frac{N_s}{N_p}$$


$$V_o = n V_{in}$$

 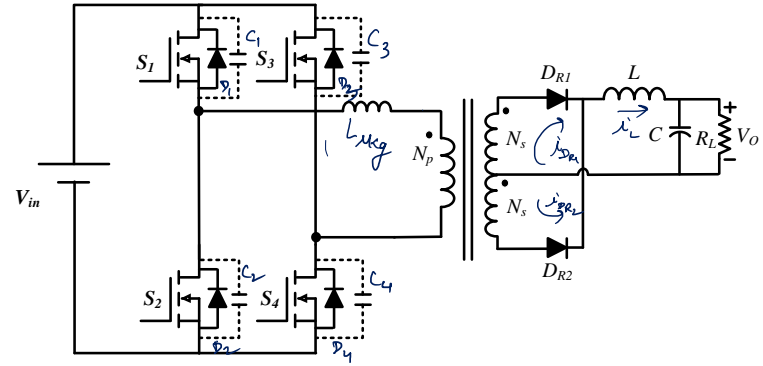

PWM Strategies


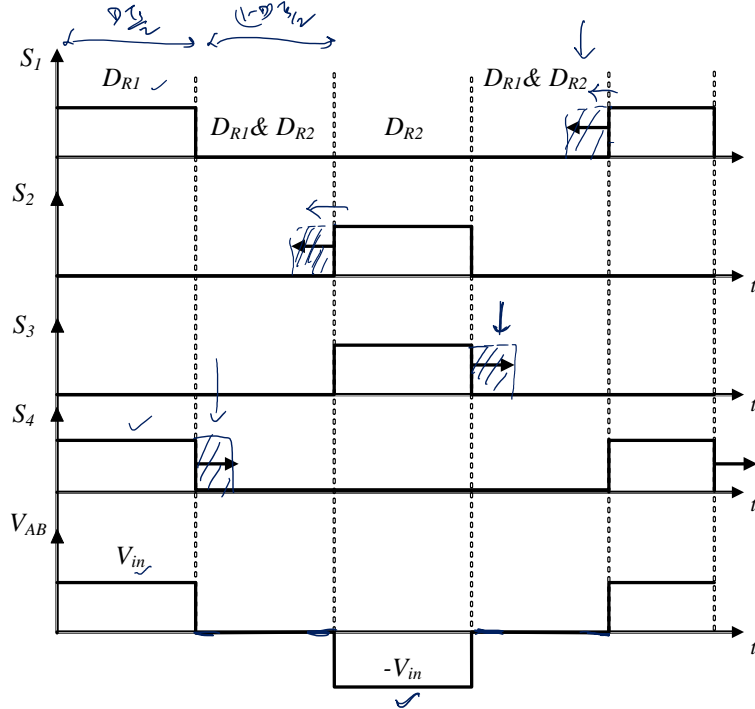


$$V_o = n V_{in} D$$

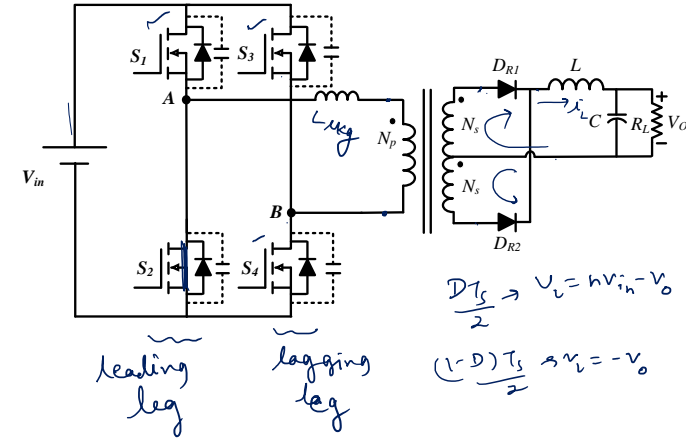

Source: Soft-Switching PWM Full-Bridge Converters: Topologies, Control, and Design by Xinbo Ruan

PWM Strategies

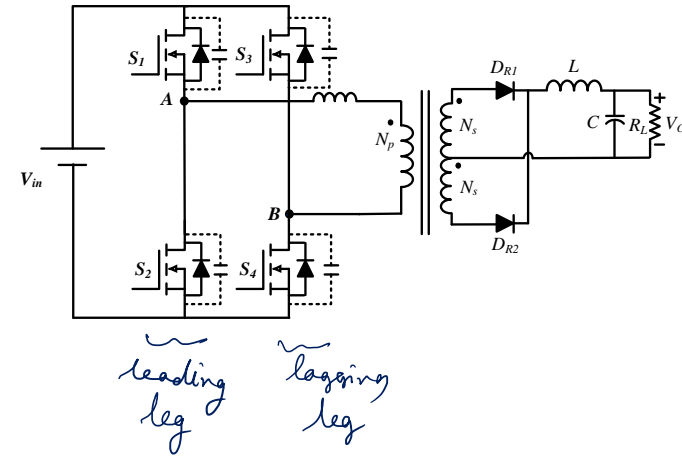
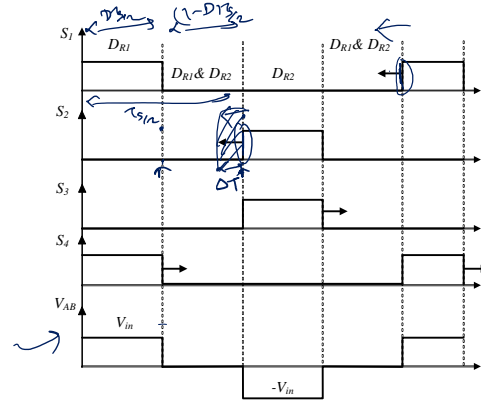


Leading leg

- 1: On-time is unchanged: $\frac{DT_S}{2}$ for S_1 & S_2
- 2: Turn-on time of S_1 and S_2 switches are adjusted forward, but the on-time is less than $\frac{T_S}{2}$ $\left(\frac{DT_S}{2} + \Delta T \right)$ $\Delta T < \frac{(1-D)T_S}{2}$
- 3: Turn-on time of S_1 and S_2 switches are adjusted forward to $\frac{T_S}{2}$ $\left(\frac{DT_S}{2} + \Delta T \right) \Rightarrow \Delta T = \frac{(1-D)T_S}{2} \Rightarrow t_{on}(S_1, S_2) = \frac{T_S}{2}$

Source: Soft-Switching PWM Full-Bridge Converters: Topologies, Control, and Design by Xinbo Ruan

PWM Strategies

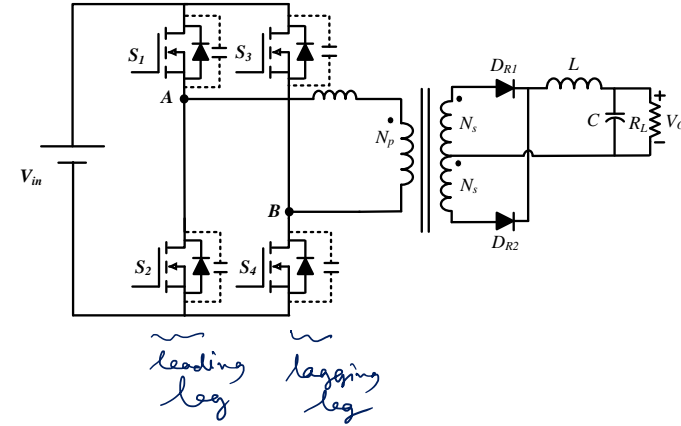
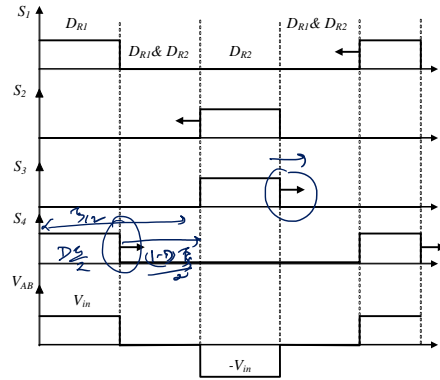


- Lagging leg

- ✓ A: On-time is unchanged: $\frac{DT_s}{2}$ S_3, S_4
- B: Turn-on time of S_3 and S_4 switches are adjusted backward, but the on-time is less than $\frac{T_s}{2}$ $\left(\frac{DT_s}{2} + \Delta t\right) \rightarrow \Delta t < \frac{(1-D)T_s}{2}$
- C: Turn-on time of S_3 and S_4 switches are adjusted backward to $\frac{T_s}{2}$ $\rightarrow \left(\frac{DT_s}{2} + \Delta t\right)$ such that $\Delta t = \frac{(1-D)T_s}{2}$

Source: Soft-Switching PWM Full-Bridge Converters: Topologies, Control, and Design by Xinbo Ruan


Modulation Method -1

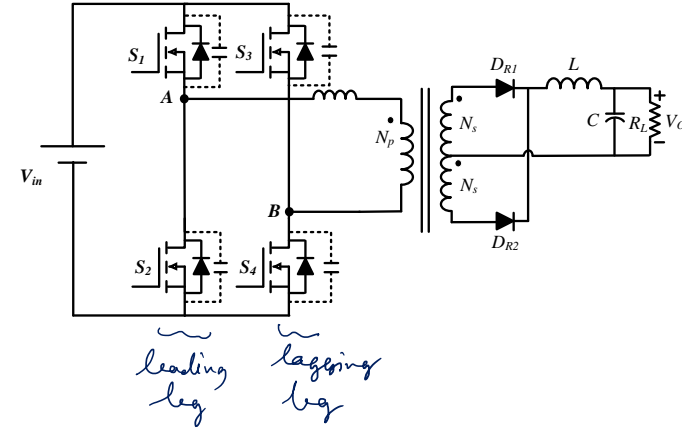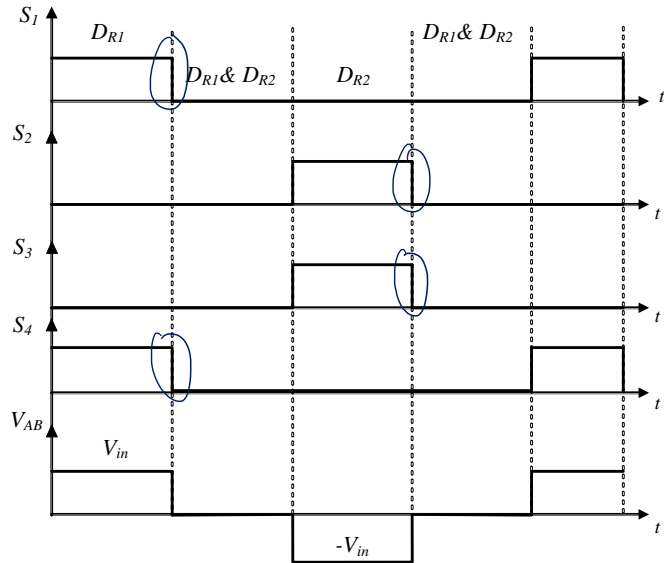

- ✓✓
1A
- Diagonal switches turn-off at the same time ⇐

Source: Soft-Switching PWM Full-Bridge Converters: Topologies, Control, and Design by Xinbo Ruan


Modulation Method -2

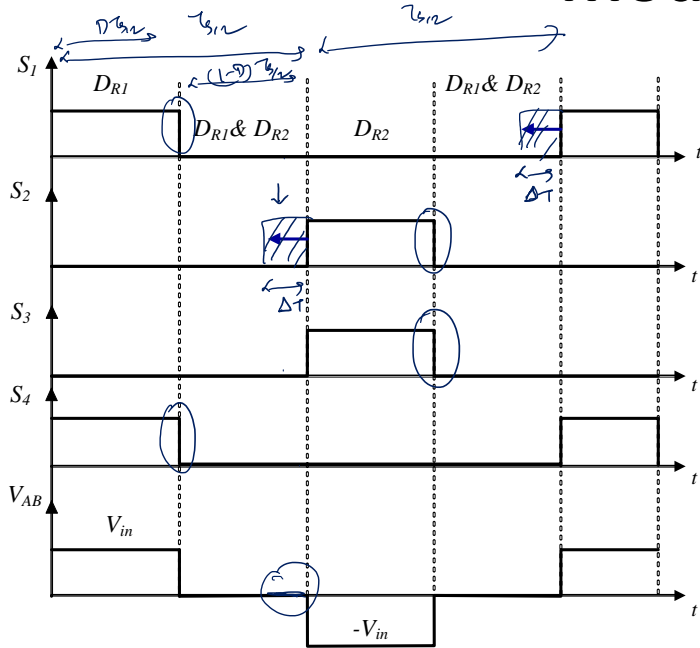

$$\Delta \tau < \frac{(1-D)T_s}{2}$$

$$\Rightarrow t_{on(s_2)} = \frac{DT_s}{2} + \Delta \tau$$


$$V_o = nV_{in}D$$

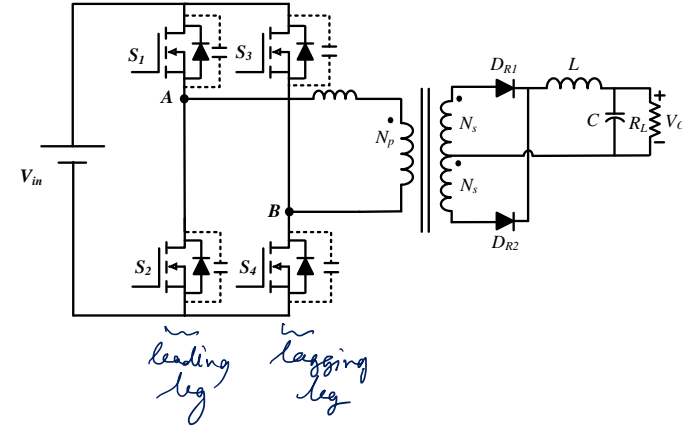

- $2A$
- Diagonal switches turn-off at the same time

Source: Soft-Switching PWM Full-Bridge Converters: Topologies, Control, and Design by Xinbo Ruan

Modulation Method -3

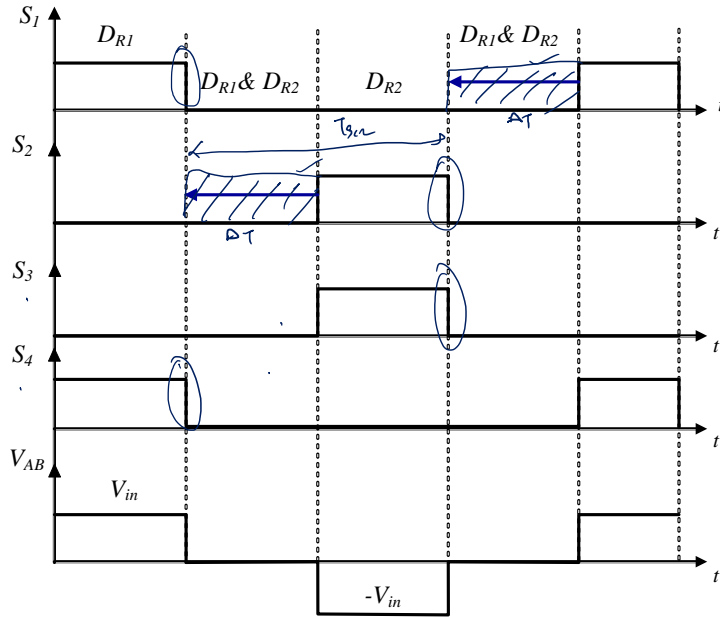


$$\Delta T = \frac{(1-D)T_s}{2}$$

$$t_{on}(s_1, s_2) = \frac{DT_s}{2} + \frac{(1-D)T_s}{2}$$

$$= T_s/2$$


$$v_o = n v_{in}$$

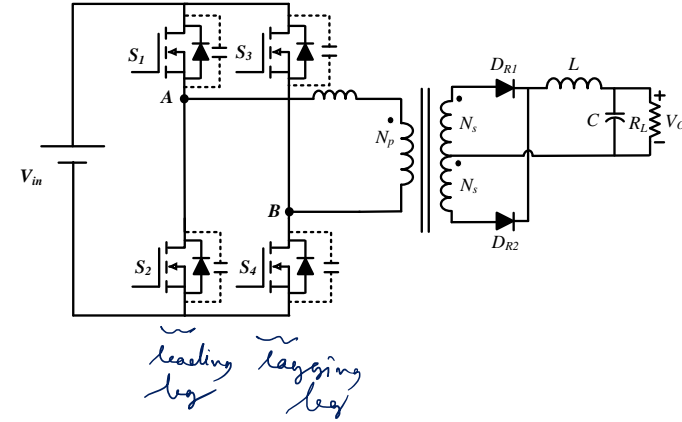

- 3A
- Diagonal switches turn-off at the same time

Source: Soft-Switching PWM Full-Bridge Converters: Topologies, Control, and Design by Xinbo Ruan


Modulation Method -4

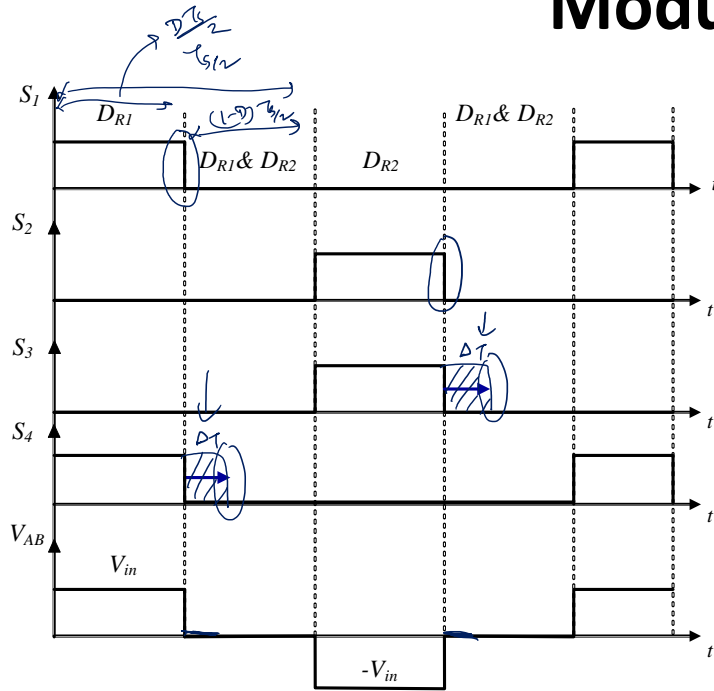

$$\Delta T < \frac{(1-D)T}{2}$$

$$\Rightarrow t_{on}(s_2, s_u) = \frac{DT_1}{2} + \Delta T$$

$$V_o = nV_{in}D$$

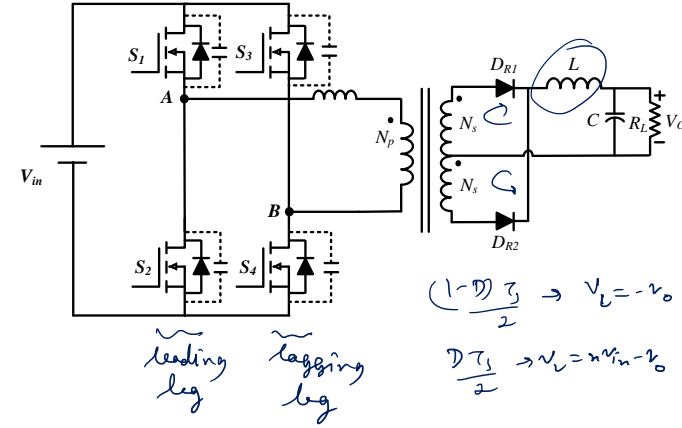


$$\frac{(1-D)T}{2} \rightarrow V_L = -v_o$$

$$\frac{DT_1}{2} \rightarrow V_L = nV_{in} - v_o$$

- ✓ 1B
- Diagonal switches turn-off at different time

Source: Soft-Switching PWM Full-Bridge Converters: Topologies, Control, and Design by Xinbo Ruan

Modulation Method -5

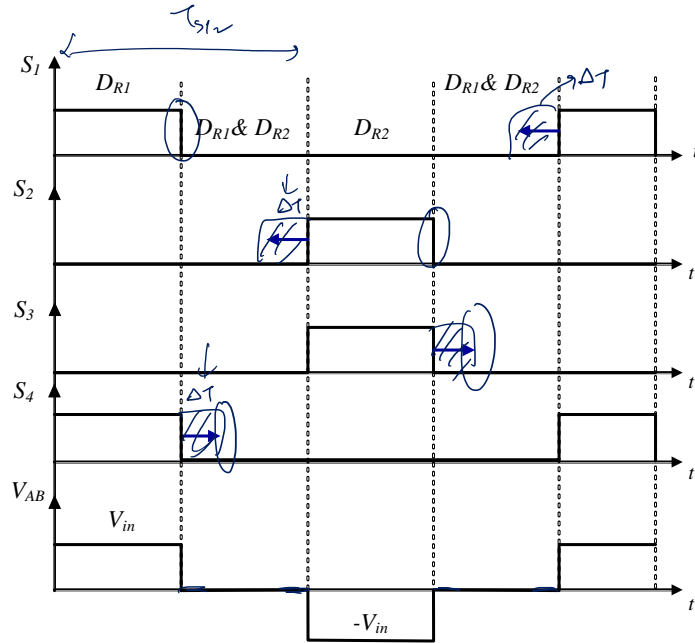


- 2B
- Diagonal switches turn-off at different time

$$\Delta T < \frac{(1-D)T_s}{2}$$

$$\Rightarrow t_{on} = \frac{DT_s}{2} + \Delta T$$


(S₁, S₂, S₃, S₄)

$$V_o = n V_{in} D$$

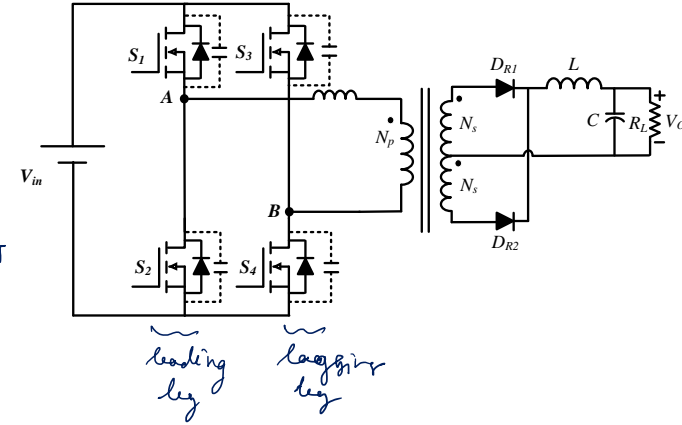

Source: Soft-Switching PWM Full-Bridge Converters: Topologies, Control, and Design by Xinbo Ruan

Modulation Method -6

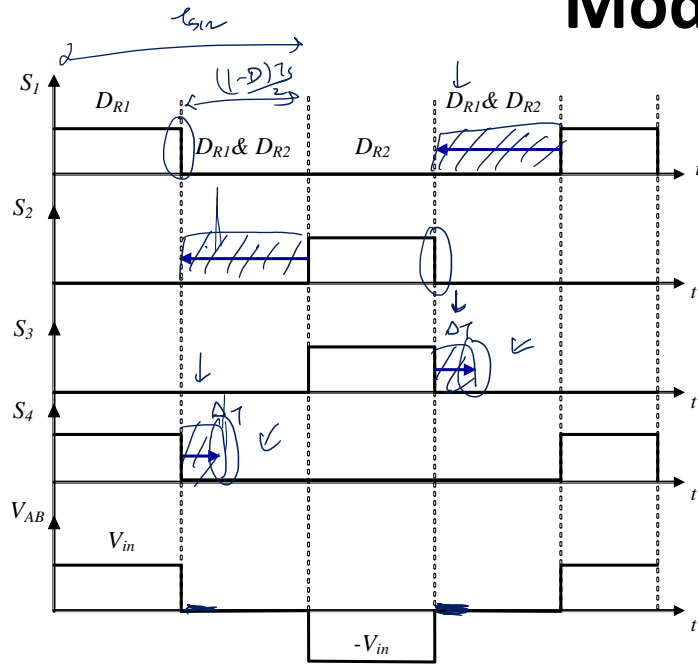


$$t_{on}(s_1, s_2) = \frac{T_s}{2}$$

$$t_{on}(s_3, s_4) = \frac{DT_s}{2} + \Delta T$$

$$\Rightarrow \Delta T < \frac{(1-D)T_s}{2}$$


$$\Rightarrow v_o \approx n v_{in}$$

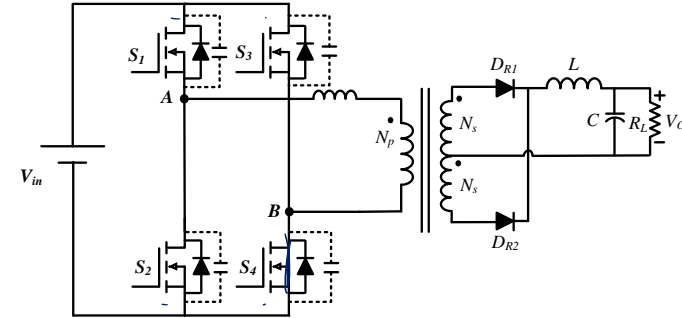

- 3B
- Diagonal switches turn-off at different time


Source: Soft-Switching PWM Full-Bridge Converters: Topologies, Control, and Design by Xinbo Ruan

Modulation Method -7

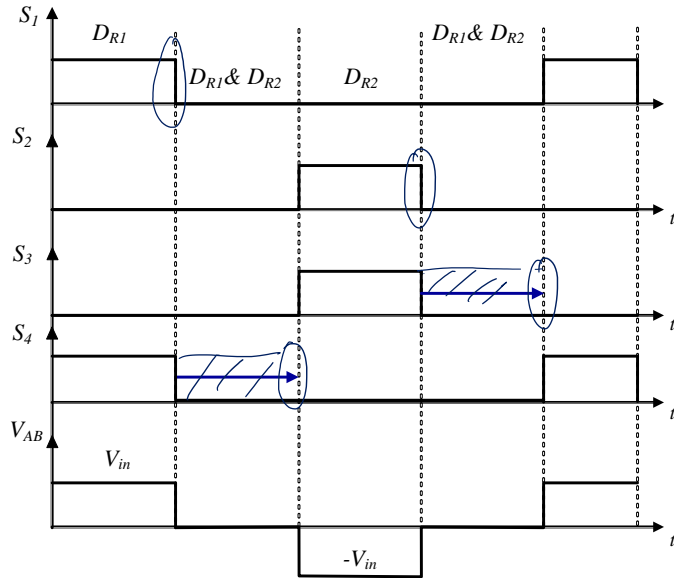


$$\Rightarrow t_{on}(s_3, s_4) = \frac{T_s}{2}$$


$$\Rightarrow v_o = n v_{in} D$$

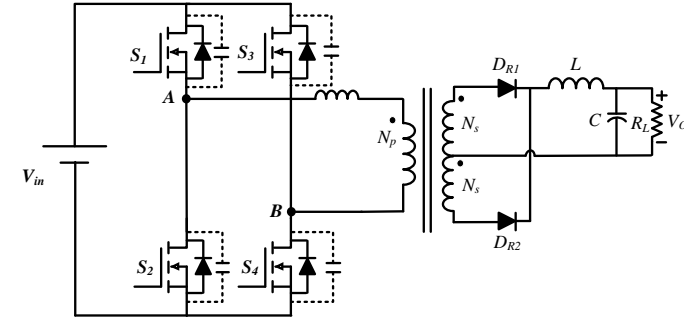

 - \checkmark 1C
- Diagonal switches turn-off at different time



Modulation Method -8

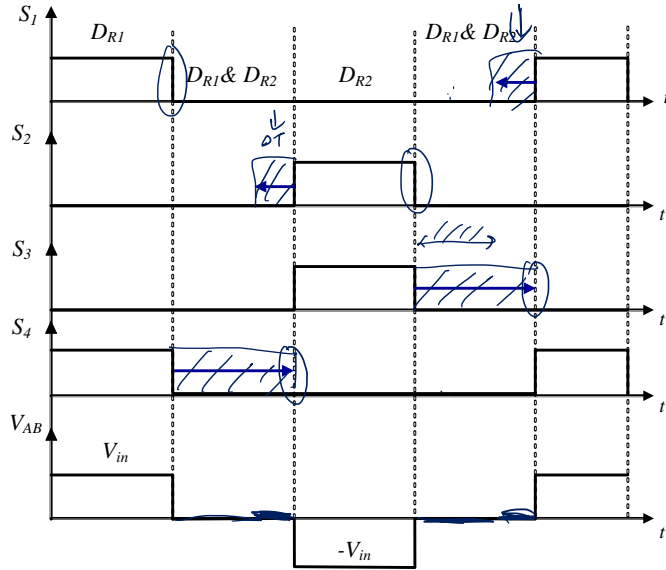


$$t_{on}(S_1, S_4) = \frac{T_s}{2}$$

$$t_{on}(S_1, S_2) = \frac{D T_s}{2} + \Delta T$$

$$\Delta T < \frac{(1-D) T_s}{2}$$


$$V_o = n V_{in} D$$

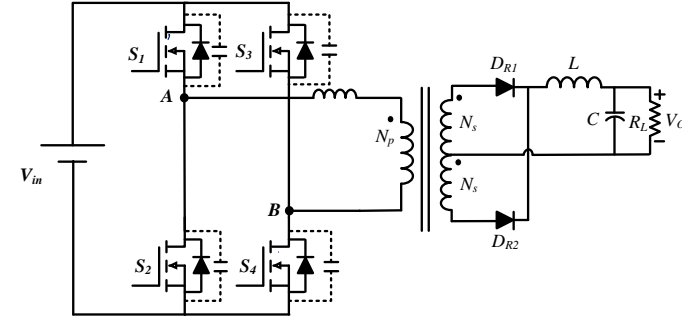

- $2C$
- Diagonal switches turn-off at different time

Source: Soft-Switching PWM Full-Bridge Converters: Topologies, Control, and Design by Xinbo Ruan


Modulation Method -9

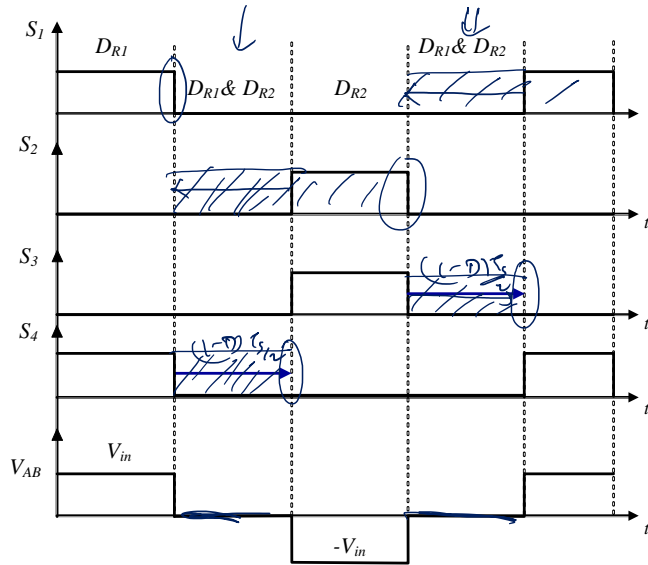

$$t_{on}(S_1, S_2, S_3, S_4) = \frac{T_s}{2}$$

$$\Delta T = \frac{(1-D)T_s}{2}$$

$$V_o = n V_{in} D$$

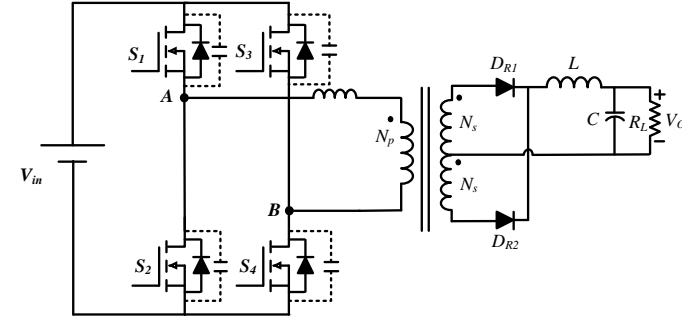


- $\sim 3C$
- Diagonal switches turn-off at different time

Source: Soft-Switching PWM Full-Bridge Converters: Topologies, Control, and Design by Xinbo Ruan

Two Types of PWM Strategies

- Type-1: Diagonal switches turns-off at the same time: Modulation method 1 to 3
- Type-2: Diagonal switches turns-off at different time: Modulation method 4 to 9

$$V_o = n V_{in}$$

 

Source: Soft-Switching PWM Full-Bridge Converters: Topologies, Control, and Design by Xinbo Ruan

Thank You

