



IIT ROORKEE



NPTEL ONLINE  
CERTIFICATION COURSE

# Charging Infrastructure

## Lecture-27

### Closed loop control of three-phase AC-DC converter-II

Dr. Apurv Kumar Yadav

Department of Electrical Engineering




# Recap
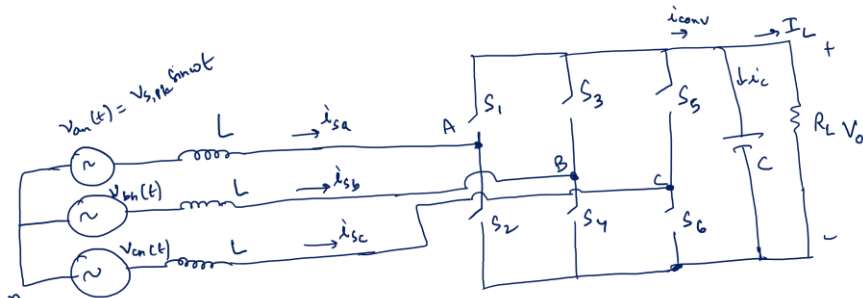
## Control objectives


① To regulate the output voltage to a desired value. ( $> \sqrt{2} V_{LL}$ )

② The current drawn should have unity power factor (upf) operation




$$i_{sa} + i_{sb} + i_{sc} = 0 \quad (\text{for balanced 3-}\phi \text{ operation})$$

# Recap

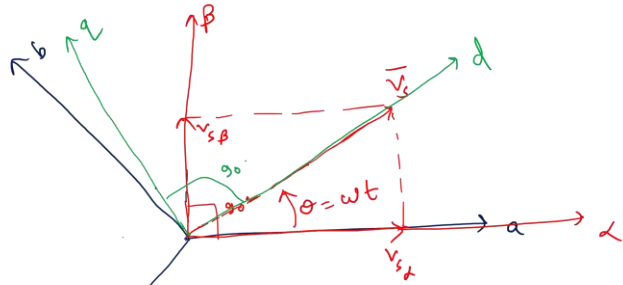

$\alpha$ - $\beta$   $\rightarrow$  stationary reference frame

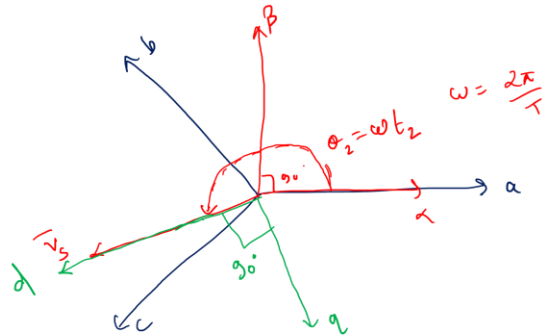$d$ - $q$   $\rightarrow$  rotating reference frame



at one instant 't'

$a, b, c \rightarrow$  sampled quantity ( $v_s, i_s, v_{sw}$ )

$$\alpha = a - b/2 - c/2 \Rightarrow \alpha = \frac{3a}{2}$$

$$\beta = a \cos 90^\circ + b \cos 30^\circ - c \cos 30^\circ \Rightarrow \beta = \frac{\sqrt{3}}{2} b - \frac{\sqrt{3}}{2} c$$

$$d = \alpha \cos \theta + \beta \sin \theta$$

$$q = -\alpha \sin \theta + \beta \cos \theta$$

$$V_{s\alpha} = \frac{3}{2} V_{sa}$$

$$V_{s\beta} = \frac{\sqrt{3}}{2} V_{sb} - \frac{\sqrt{3}}{2} V_{sc}$$

( $V_{sa}, V_{sb}, V_{sc} \rightarrow$  sampled  $v_{au}(t), v_{bu}(t), v_{cu}(t)$ )

$$\Rightarrow V_{sd} = V_{s\alpha} \cos \theta + V_{s\beta} \sin \theta$$



$$V_{sq} = -V_{s\alpha} \sin \theta + V_{s\beta} \cos \theta$$

$$I_{s\alpha} = \frac{3}{2} I_{sa} \quad (I_{sa}, I_{sb}, I_{sc} \rightarrow \text{sampled } i_{sa}, i_{sb}, i_{sc})$$

$$I_{s\beta} = \frac{\sqrt{3}}{2} I_{sb} - \frac{\sqrt{3}}{2} I_{sc}$$

$$I_{sd} = I_{s\alpha} \cos \theta + I_{s\beta} \sin \theta$$
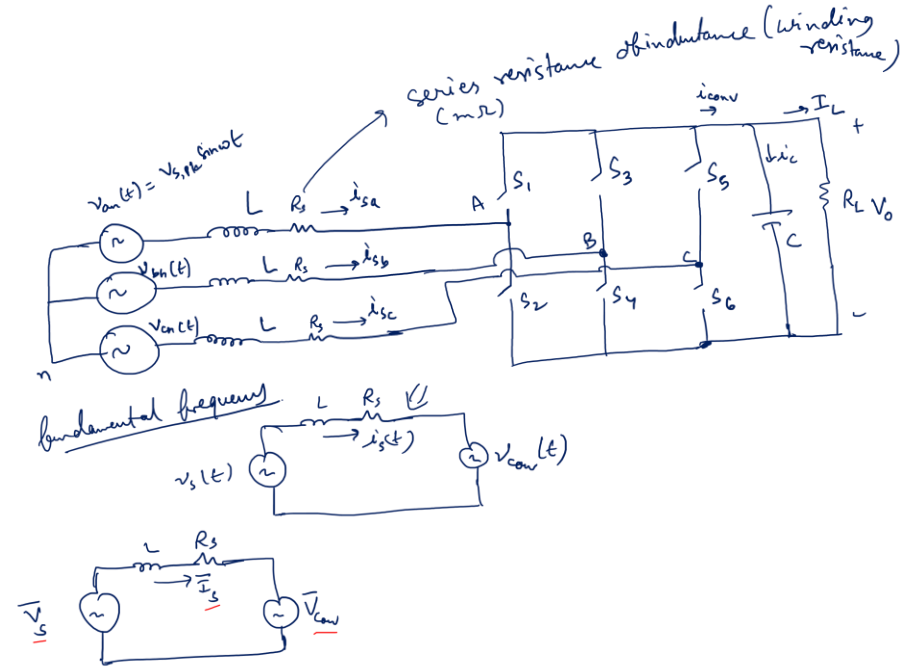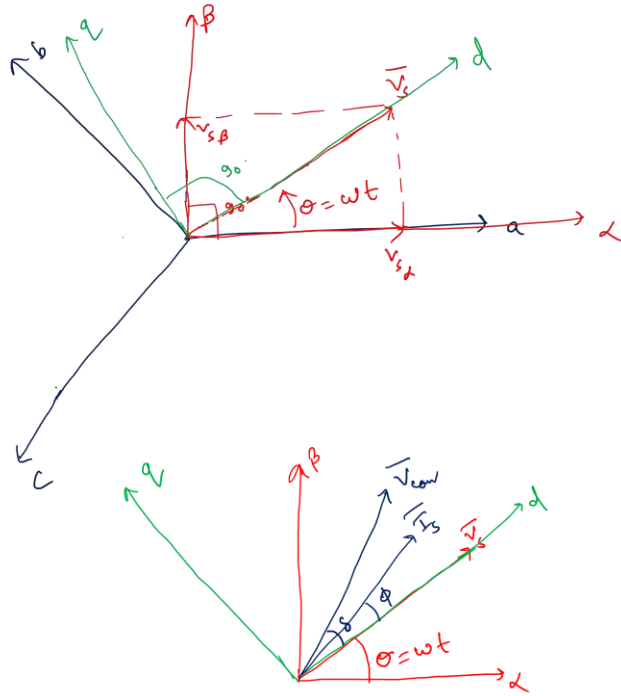
$$I_{sq} = -I_{s\alpha} \sin \theta + I_{s\beta} \cos \theta$$



d-q frame

$$\bar{V}_s = V_{sd} + j0$$

$$\Rightarrow \bar{V}_s = |V_s| \cdot e^{j0}$$

$$\bar{I}_s = |I_s| \cdot e^{j\phi}$$

$$\bar{V}_{\text{caw}} = |V_{\text{caw}}| \cdot e^{j\delta}$$

α-β frame

$$\bar{V}_s = |V_s| e^{j\theta}$$


$$\bar{I}_s = |I_s| \cdot e^{j(\theta+\phi)}$$

$$\bar{V}_{\text{caw}} = |V_{\text{caw}}| e^{j(\theta+\delta)}$$

( $V_{sq} = 0$ , as the  $\bar{V}_s$  is aligned along d-axis)

$$(|V_s| = \sqrt{V_{sd}^2 + 0^2})$$

$$\Rightarrow I_{sd} = |I_s| \cdot \cos(\theta + \phi); \quad I_{sq} = |I_s| \sin(\theta + \phi)$$

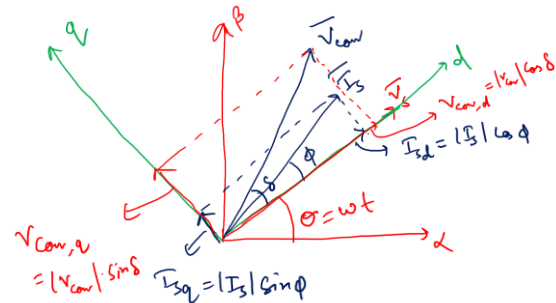

d-B stationary frame

$$\bar{V}_s = L \frac{d\bar{I}_s}{dt} + R_s \bar{I}_s + \bar{V}_{cmv}$$

$$|V_s| e^{j\theta} = L \frac{d}{dt} (|I_s| e^{j(\theta+\phi)}) + R_s (|I_s| e^{j(\theta+\phi)}) + |V_{cmv}| e^{j(\theta+\delta)} \longrightarrow (1)$$


d-q (synchronous rotating) frame

By multiplying eq. (1) by  $e^{-j\theta}$


$$\Rightarrow |V_s| \cdot e^{j\theta} \cdot e^{-j\theta} = L \frac{d}{dt} (|I_s| e^{j(\theta+\phi)}) \cdot e^{-j\theta} + R_s (|I_s| e^{j(\theta+\phi)}) \cdot e^{-j\theta} + |V_{cmv}| \cdot e^{j(\theta+\delta)} \cdot e^{-j\theta}$$

$$\Rightarrow |V_s| \cdot e^{j0} = L \frac{d}{dt} (|I_s| e^{j(\theta+\phi)}) \cdot e^{-j\theta} + R_s (|I_s| e^{j\phi}) + |V_{cmv}| \cdot e^{j\delta} \longrightarrow (2)$$

$$L \frac{d}{dt} \left( \underbrace{|I_s| e^{j(\theta+\phi)}}_u \cdot \underbrace{e^{-j\theta}}_v \right) = L \left[ \frac{d}{dt} (|I_s| e^{j(\theta+\phi)}) \cdot e^{-j\theta} + |I_s| e^{j(\theta+\phi)} \cdot \frac{d}{dt} (e^{-j\theta}) \right]$$

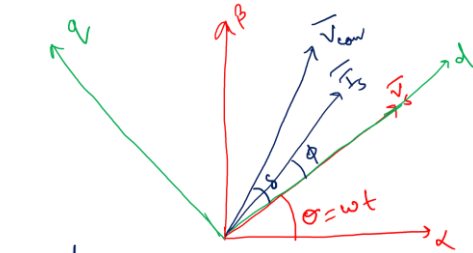
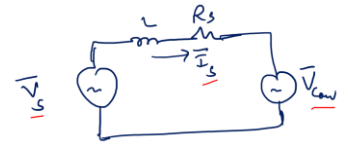
$$\Rightarrow \frac{d\theta}{dt} = \omega$$



$$L \frac{d}{dt} \left( I_3 e^{j(\omega t + \phi)} \cdot e^{-j\omega t} \right) = L \left[ \frac{d}{dt} \left( I_3 \cdot e^{j(\omega t + \phi)} \right) \cdot e^{-j\omega t} + I_3 \cdot e^{j(\omega t + \phi)} \cdot \frac{d}{dt} e^{-j\omega t} \right] \quad \cdot \quad \frac{d}{dt} (e^{-j\omega t}) = e^{-j\omega t} \left( -\frac{d\omega}{dt} \right) = j e^{-j\omega t} (-\omega)$$

$$= L \frac{d}{dt} \left( I_3 \cdot e^{j(\omega t + \phi)} \right) \cdot e^{-j\omega t} - j L I_3 \cdot e^{j(\omega t + \phi)} \cdot e^{-j\omega t} \omega$$

$$\Rightarrow L \frac{d}{dt} \left( I_3 e^{j(\omega t + \phi)} \right) \cdot e^{-j\omega t} = L \frac{d}{dt} \left( I_3 e^{j(\omega t + \phi - \omega t)} \right) + j L \left( I_3 \cdot e^{j(\omega t + \phi - \omega t)} \right) \cdot \omega$$

$$L \frac{d}{dt} \left( I_3 \cdot e^{j(\omega t + \phi)} \right) \cdot e^{-j\omega t} = L \frac{d}{dt} \left( I_3 \cdot e^{j\phi} \right) + j L \omega \cdot I_3 \cdot e^{j\phi} \longrightarrow \textcircled{3}$$

put eq.  $\textcircled{3}$  in  $\textcircled{2}$

$$I_{s1} \cdot e^{j\omega t} = L \frac{d}{dt} \left( I_3 \cdot e^{j\phi} \right) + j L \omega I_3 \cdot e^{j\phi} + R_s (I_3 \cdot e^{j\phi}) + (V_{L\omega}) e^{j\omega t} \longrightarrow \textcircled{4}$$

$$I_3 \cdot e^{j\phi} = I_3 \cdot \cos \phi + j I_3 \cdot \sin \phi$$

$$= I_{s1} + j I_{s2}$$

$$I_{s1} \cdot e^{j\omega t} = V_{s1} + j\omega L I_3 \quad (V_{s1} = I_{s1} \cdot \cos \phi)$$

$$|V_{can}| \cdot e^{j\delta} = |V_{can}| \cdot \cos \delta + j |V_{can}| \cdot \sin \delta \\ = V_{can,d} + j V_{can,q}$$

$$V_{sd} + j0 = L \frac{d}{dt} (I_{sd} + j I_{sq}) + R_s (I_{sd} + j I_{sq}) + j \omega L (I_{sd} + j I_{sq}) + (V_{can,d} + j V_{can,q})$$

$$\Rightarrow V_{sd} + j0 = L \frac{d}{dt} I_{sd} + j L \frac{d}{dt} I_{sq} + R_s I_{sd} + j R_s I_{sq} + V_{can,d} + j V_{can,q} + j \omega L I_{sd} - \omega L I_{sq}$$

Separate out Real & Imaginary part

Real part,  $V_{sd} = L \frac{d}{dt} I_{sd} + R_s I_{sd} + V_{can,d} - \omega L I_{sq}$

Imaginary, 0 =  $L \frac{d}{dt} I_{sq} + R_s I_{sq} + V_{can,q} + \omega L I_{sd}$

Rearrange the term

d-axis model,  $L \frac{d}{dt} I_{sd} + R_s I_{sd} = -V_{can,d} + \omega L I_{sq} + V_{sd}$

q-axis model,  $L \frac{d}{dt} I_{sq} + R_s I_{sq} = -V_{can,q} - \omega L I_{sd}$

cross-coupling term

cross-coupling term



# Thank You

