



IIT ROORKEE



NPTEL ONLINE  
CERTIFICATION COURSE

# Charging Infrastructure

## Lecture-28

### Closed loop control of three-phase AC-DC converter-III

Dr. Apurv Kumar Yadav


Department of Electrical Engineering




# Recap
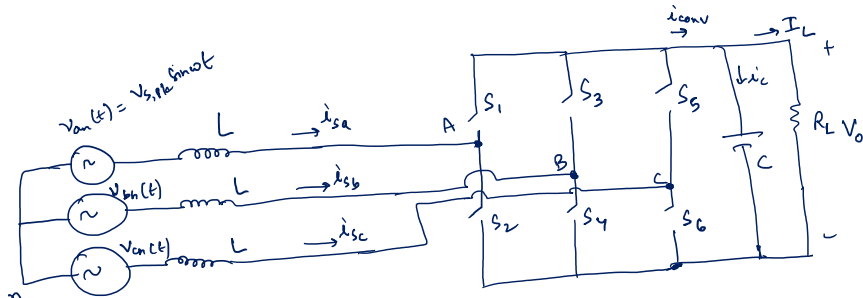
## Control objectives

- ① To regulate the output voltage to a desired value. ( $> \sqrt{2} V_{L-L}$ )
- ② The current drawn should have unity power factor (upf) operation



# Recap

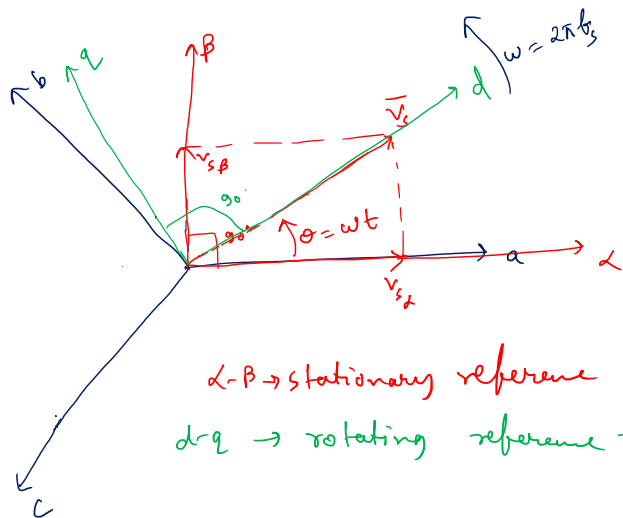


$\alpha$ - $\beta$   $\rightarrow$  stationary reference frame

$d$ - $q$   $\rightarrow$  rotating reference frame

$$i_{sa} + i_{sb} + i_{sc} = 0$$

3ph  $\rightarrow$  2-phase  $\rightarrow$   $d$ - $q$   
 $\alpha$ - $\beta$

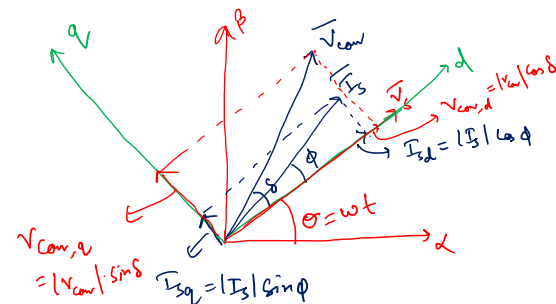$v_{sq} = 0$   
 $\rightarrow$   $d$ -axis is aligned along the  $\bar{\Psi}_s$



$\rightarrow$  cross-coupling

$d$ -axis model, 
$$L \frac{d}{dt} I_{sd} + R_s I_{sd} = -V_{\text{cross},d} + \omega L I_{sq} + V_{sd}$$


$q$ -axis model, 
$$L \frac{d}{dt} I_{sq} + R_s I_{sq} = -V_{\text{cross},q} - \omega L I_{sd} \rightarrow \text{cross-coupling}$$



d-axis model, 
$$L \frac{d}{dt} I_{sd} + R_s I_{sd} = -V_{can,d} + \omega L I_{sq} + V_{sd}$$

q-axis model, 
$$L \frac{d}{dt} I_{sq} + R_s I_{sq} = -V_{can,q} - \omega L I_{sd}$$

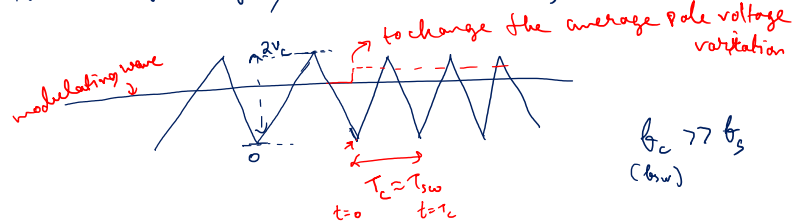Assume the three half-bridges, are modulated using SPWM




$$T_c \gg T_s$$
  
(b.w)

Average time delay in response towards change in modulating wave,  $T_d = \frac{0 \times T_{sw}}{2}$

$$\Rightarrow T_d = \frac{T_{sw}}{2}$$

$$\Rightarrow \text{The Transfer function of 3-}\phi \text{ half bridge} = \frac{G_n}{1+sT_d}$$

Gain,  $G_n = \frac{V_o}{2V_c}$

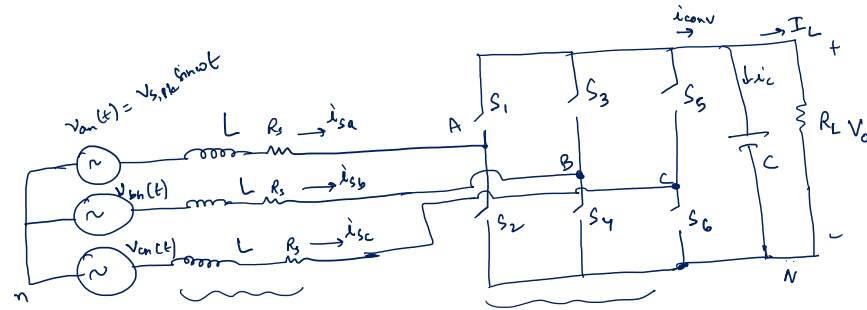

$$(T_{sw} = T_c = \frac{1}{f_{bc}} = \frac{1}{b_{sw}})$$

Source: Siva Prasad, J.S., Bhavsar, T., Ghosh, R. et al. Vector control of three-phase AC/DC front-end converter. *Sadhana* **33**, 591-613 (2008)

d-axis model, 
$$L \frac{d}{dt} I_{sd} + R_s I_{sd} = -V_{com,d} + \omega L I_{sq} + \underline{V_{sd}}$$


q-axis model, 
$$L \frac{d}{dt} I_{sq} + R_s I_{sq} = -V_{com,q} - \omega L I_{sd}$$

$$\Rightarrow (sL + R_s) I_{sd}(s) = -V_{com,d} + \omega L I_{sq} + \underline{V_{sd}}$$

$$\Rightarrow (sL + R_s) I_{sq}(s) = -V_{com,q} + \omega L I_{sd} - \underline{\omega L I_{sd}}$$


$$V_{fb,d} = \frac{-\omega L I_{sq}}{G} - \frac{V_{sd}}{G}$$

$$V_{fb,q} = \frac{\omega L I_{sd}}{G}$$

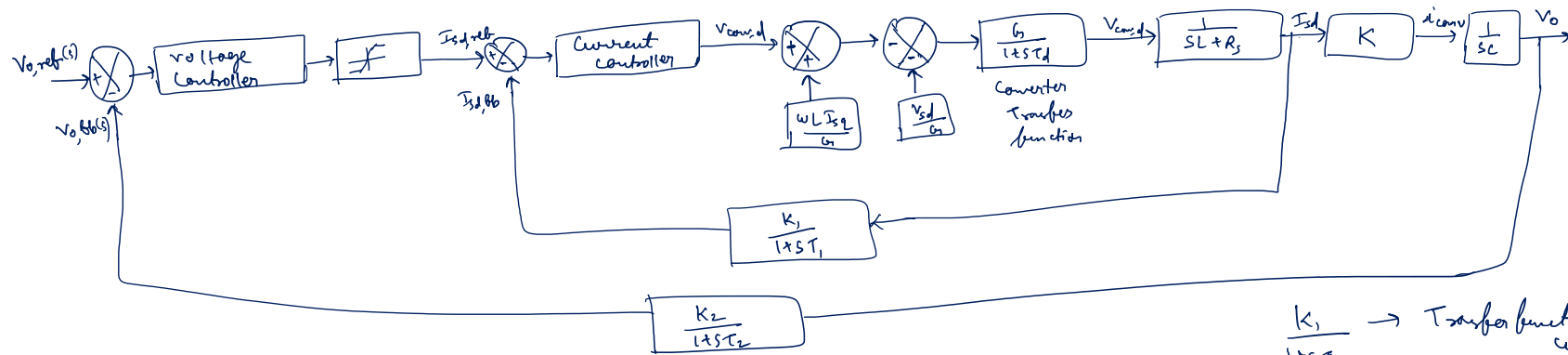

$\frac{K_1}{1+sT_1} \rightarrow$  Transfer function of current sensor

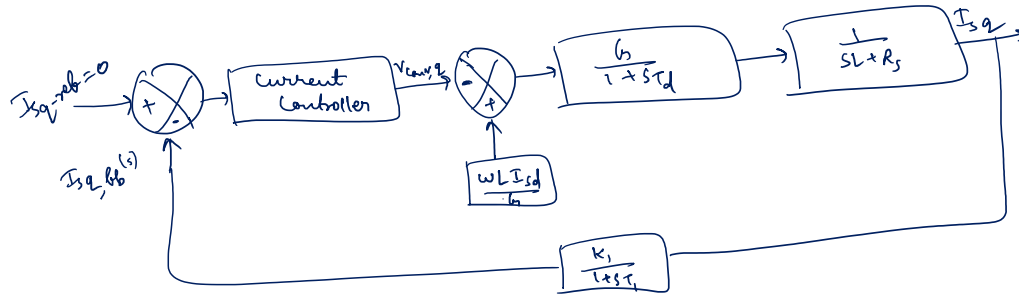$\frac{K_2}{1+sT_2} \rightarrow$  Transfer function of output voltage sensor



Source: Siva Prasad, J.S., Bhavsar, T., Ghosh, R. et al. Vector control of three-phase AC/DC front-end converter. *Sadhana* **33**, 591–613 (2008)

# Thank You

