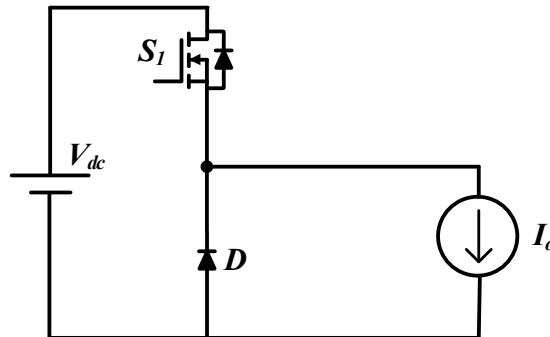




WEEK 3: ASSIGNMENT

1. For the circuit shown below what will be the RMS current (in A) of the switch S_1 , if the switch S_1 is turned-on for $20 \mu\text{s}$ and diode D is turned-on for $5 \mu\text{s}$. The switching frequency of the switch is kept at 40kHz , $V_{dc} = 400\text{V}$, $I_o = 25\text{A}$. The answer should be rounded up to 3 decimal places.



Answer: 22-23

2. If a single-phase PFC converter operating with unity power factor, then output capacitor voltage ripple has following dominant frequency component:

- A. line frequency component
- B. 2nd line harmonic component
- C. switching frequency component
- D. 2nd harmonic of switching frequency component

Answer: B

3. The transfer function $\left. \frac{\widetilde{i_l(s)}}{\widetilde{d(s)}} \right|_{\widetilde{v_s(s)}=0}$ is obtained from state space representation by following equations:


- A. $(SI - A)^{-1}Q$
- B. $(SI - A)^{-1}K$
- C. $C(SI - A)^{-1}Q$
- D. $C(SI - A)^{-1}K$

Answer: B

4. A boost PFC converter fed from 220V , 50Hz input is supply the 1000W load. The converter is operated with the switching frequency of 10 kHz and regulates the output voltage at 400V . The allowable peak to peak output voltage ripple is 5% of the nominal. Calculate the smallest capacitance is required to meet the specification in μF . (Note: The answer should be rounded up to 2 decimal places; use $\pi = 3.14$; $1\text{ radian} = 57.3\text{ degrees}$).

Answer: 397.00 – 400.00

5. For the Boost PFC as shown below.

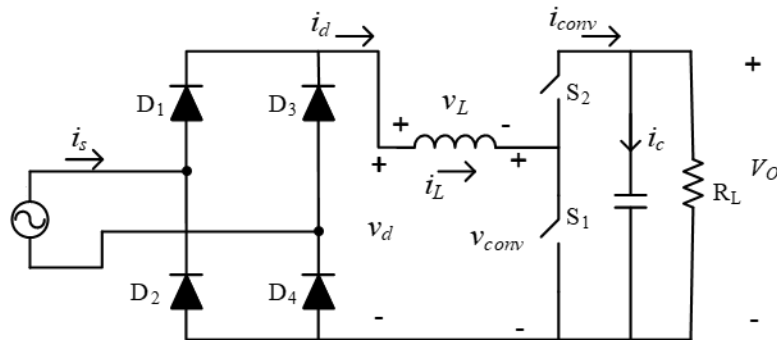

Match the following:

Switches	RMS current stress
I. S_1	a. $\sqrt{\frac{2}{T} \int_0^{\frac{T}{2}} d(t)(i_s^2(t)) dt}$
II. S_2	b. $\sqrt{\frac{2}{T} \int_0^{\frac{T}{2}} (1 - d(t))(i_s^2(t)) dt}$
III. D_1	c. $\frac{I_{s,pk}}{2}$
IV. D_2	d. $\frac{I_{s,pk}}{\sqrt{2}}$

- A. I -a, II-b, III-c, IV-c
- B. I -b, II-a, III-c, IV-c
- C. I -b, II-a, III-d, IV-d
- D. I -a, II-b, III-d, IV-d

Answer: A

6. If, while doing small signal modelling to obtain the transfer function, following are the steps involved:

- I. Average large signal model
- II. Linearization around the operating point
- III. Perturbations
- IV. Conversion from time domain to s-domain

Then what will be the correct order in which the above mentioned steps need to be arranged to obtain the transfer function.

- A. I, II, III, IV
- B. IV, III, II, I
- C. I, III, II, IV
- D. IV, III, II, I

Answer: C

7. For the table shown below:

Matrices	parameters
I. A_1	a. $\begin{bmatrix} 0 & -\frac{1}{L} \\ \frac{1}{C} & -\frac{1}{R_L C} \end{bmatrix}$
II. A_2	b. $\begin{bmatrix} 1 \\ L \\ 0 \end{bmatrix}$
III. B_1, B_2	c. $\begin{bmatrix} 0 & 0 \\ 0 & -\frac{1}{R_L C} \end{bmatrix}$
IV. C_1, C_2	d. $[0 \quad 1]$

Match the correct combination (Symbols have obvious meanings):

- A. I -a, II-c, III-b, IV-d
- B. I -c, II-a, III-b, IV-d
- C. I -a, II-c, III-d, IV-b
- D. I -c, II-a, III-d, IV-b

Answer: B

8. For dual loop closed control of PFC converter, which of the following statements is/are true:

- A. The outer loop is the output DC voltage control loop
- B. The inner loop is the supply current control loop
- C. The outer loop is the supply current control loop
- D. The inner loop is the output DC voltage control loop

Answer: A, B

9. Which of the following quantities is/are the state variable in the boost PFC converter?

- A. Inductor current
- B. Duty ratio
- C. Input AC voltage
- D. Output capacitor voltage

Answer: A, D

10. Which of the following is/are the correct assumptions which have been taken while obtaining the small signal modelling of the boost PFC converter to obtain the average current control?

- A. $f_{sw} \gg f_s$
- B. $f_s \gg f_{sw}$
- C. Duty ratio at one switching period remains constant
- D. magnitude of perturbations \gg operating point values
- E. magnitude of perturbations \ll operating point values

Answer: A, C, D

Answer Keys:

1. 22-23	2. B	3. B	4. 397.00-400.00	5. A
6. C	7. B	8. A, B	9. A, D	10. A, C, D

Assignment #3

Q.1. for the circuit, 'S₁' is on for 20μs, and switching frequency of 40kHz

$$\Rightarrow T_s = \frac{1}{40 \times 1000} = 25 \mu s$$

$$\therefore \text{Duty ratio of } S_1, D = \frac{20 \mu s}{25 \mu s}$$

$$= 0.8$$

$$\therefore \text{The RMS current of } S_1 = \sqrt{D} \cdot I_o$$
$$= \sqrt{0.8} \cdot 25$$

(as it carries constant current)

$$\boxed{I_{\text{rms}, S_1} = 22.36 \text{ A}}$$

Assignment #3

Q.4.

$$C = \frac{P_L}{2\pi f_s \Delta V_o \cdot V_o}$$

$$\begin{aligned} P_L &= 1000W \\ V_o &= 400V \\ f_s &= 50 \text{ Hz} \end{aligned}$$

$$\begin{aligned} \Delta V_o &= \frac{5}{100} \times 400 \\ &= 20V \end{aligned}$$

(5% of nominal)

$$\Rightarrow C = \frac{1000}{2\pi \times 3.14 \times 50 \times 20 \times 400}$$

$$C = 3.98089 \times 10^{-4}$$

$$\Rightarrow \boxed{C = 398.09 \mu F}$$

(this is the smallest capacitor as if you increase the capacitor the ΔV_o will be smaller than 5% of nominal, which is o.k.)