



IIT ROORKEE



NPTEL ONLINE
CERTIFICATION COURSE

Charging Infrastructure



Lecture-11

Single-phase Boost PFC Converter-III

Dr. Apurv Kumar Yadav
Department of Electrical Engineering



Recap

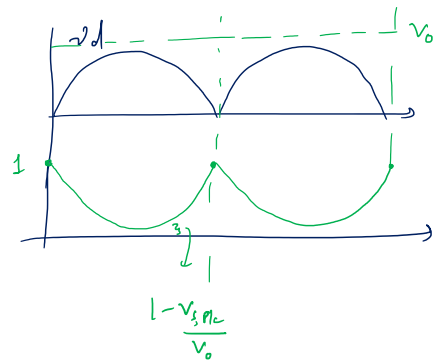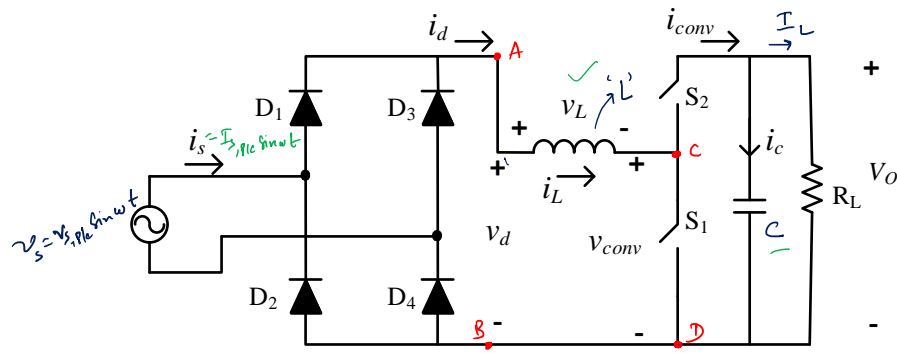

$$v_d = |v_s(t)|$$

$$v_d = V_{s,PK} |\sin \omega t| \Rightarrow t_{sw} \gg t_s$$

full-bridge
diode rectifier

Boost converter

for $S_2 \rightarrow d(t)_{s2} = 1 - d(t)$

$$= \frac{V_{s,PK} \sin \omega t}{V_o}$$

for $S_1 \rightarrow d(t)_{s1} = d(t)$

$$d(t) = 1 - \frac{V_{s,PK} \sin \omega t}{V_o}$$

$$\Rightarrow 0 < d(t) < 1$$

$$\Rightarrow V_o > V_{s,PK} \rightarrow$$

$$230V \rightarrow 325V$$

$$\Rightarrow V_o > 325V$$

$$\approx V_o \approx 400V$$

$$L = \frac{V_o}{4 \Delta i_{L,max} f_{sw}} \rightarrow$$

$\Delta i_{L,max} \rightarrow$ allowable ripple current $\rightarrow 10\% \text{ of } I_{s,PK}$



Sizing of 'c'

Assumption, the converter is operated in such a manner that the upf current is drawn from the grid

$$\begin{aligned} \rightarrow i_s &= I_{s, \text{pk}} \sin \omega t \\ v_s &= V_{s, \text{pk}} \sin \omega t \end{aligned}$$

$$P_{in}(t) = (V_{s,plc} \sin \omega t) (I_{s,plc} \sin \omega t)$$

$$= V_{s,plc} I_{s,plc} \sin^2 \omega t$$


$$= V_{s,plc} I_{s,plc} \sin^2 \omega t$$

$$= V_{s,rlc} I_{s,rlc} \frac{(1 - \cos 2\omega t)}{2}$$

$$P_{in}(t) = \frac{V_{s,pk} I_{s,pk}}{2} - \frac{V_{s,pk} I_{s,pk} \cos 2\omega t}{2} \rightarrow (1)$$

Power at the
output of
half bridge
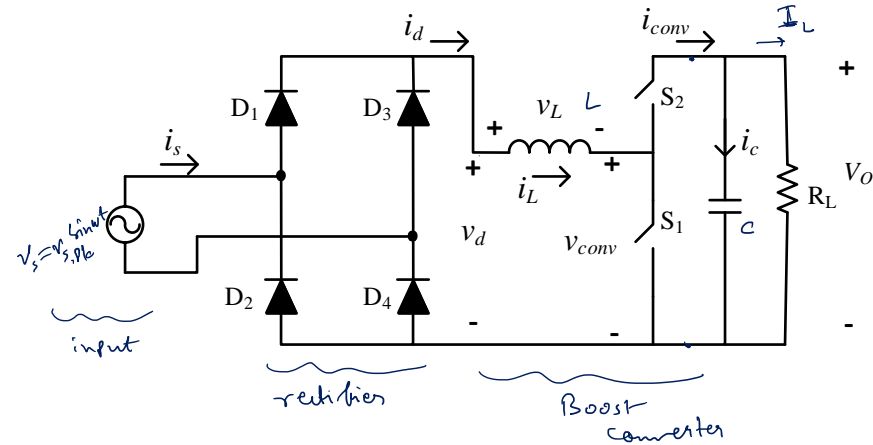
$$P_d(t) = i_{conv}(t) \cdot V_o \longrightarrow (2)$$



Assume, the losses in rectifier & boost converter is negligible

$$\Rightarrow \text{Eq (1)} = \text{Eq (2)}$$

$$\Rightarrow P_{in}(t) = P_d(t) \quad (\text{By doing the power balance})$$


$$\Rightarrow i_{conv}(t) \cdot V_o = \frac{V_{s,pk} I_{s,pk}}{2} - \frac{V_{s,pk} I_{s,pk} \cos 2\omega t}{2}$$

$$\Rightarrow i_{conv}(t) = \frac{V_{s,pk} I_{s,pk}}{2 V_o} - \frac{V_{s,pk} I_{s,pk} \cos 2\omega t}{2 V_o}$$

will be flowing 'p' to the load P_o
 \Downarrow
 DC quantity

$$i_{conv}(t) = i_c(t) + I_L$$

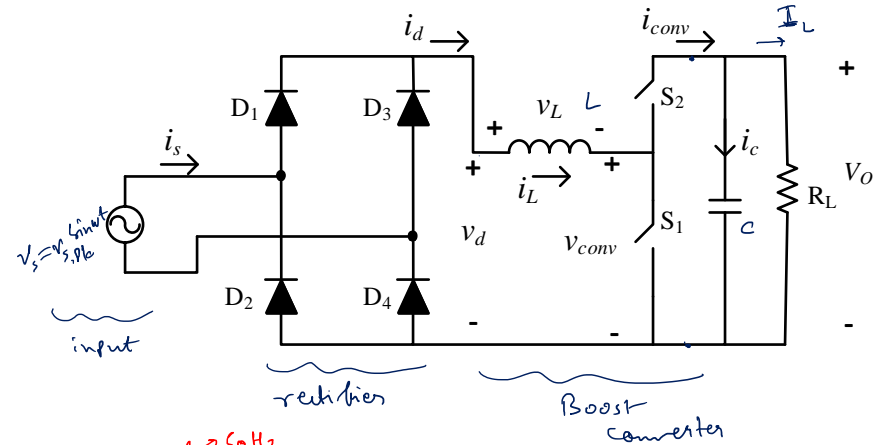\Downarrow
 2nd harmonic current \rightarrow will be flowing through the capacitor
 \Rightarrow 2nd line harmonic current



$$\omega = 2\pi f_s \rightarrow 50 \text{ Hz}$$

$$i_c(t) = \frac{-V_{s,pk} I_{s,pk} \cos 2\omega t}{2 V_o}$$

the ripple generated by the $i_c(t)$

$$\Rightarrow V_{o,ripple} = \frac{1}{C} \int i_c(t) dt$$

$$V_{o,ripple} = \frac{1}{C} \int \frac{-V_{s,pk} I_{s,pk}}{2 V_o} \cos 2\omega t dt \rightarrow (3)$$


we can write,

$$\frac{V_{s,pk} I_{s,pk}}{2 V_o} = I_L \rightarrow (4)$$


Eq. (4) in (3)

$$\Rightarrow V_{o,ripple} = \frac{-I_L}{C} \int \cos 2\omega t dt$$
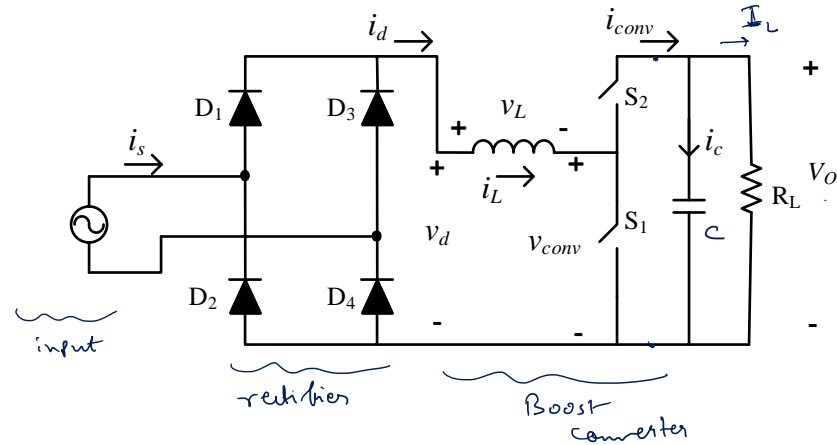
$$V_{o,ripple} = \frac{-I_L}{2C\omega} \sin 2\omega t \rightarrow (5)$$



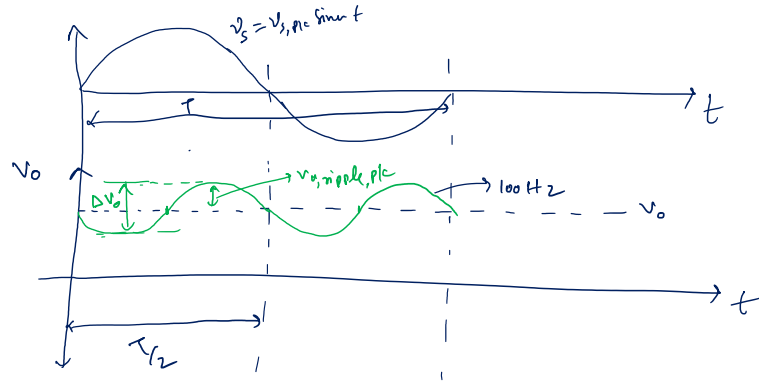
$$V_{o, ripple, plc} = \frac{I_L}{2\omega C} \longrightarrow (6)$$



$$C = \frac{I_L}{2\omega V_{o, ripple, plc}}$$

$$C = \frac{I_L}{\omega \Delta V_o}$$

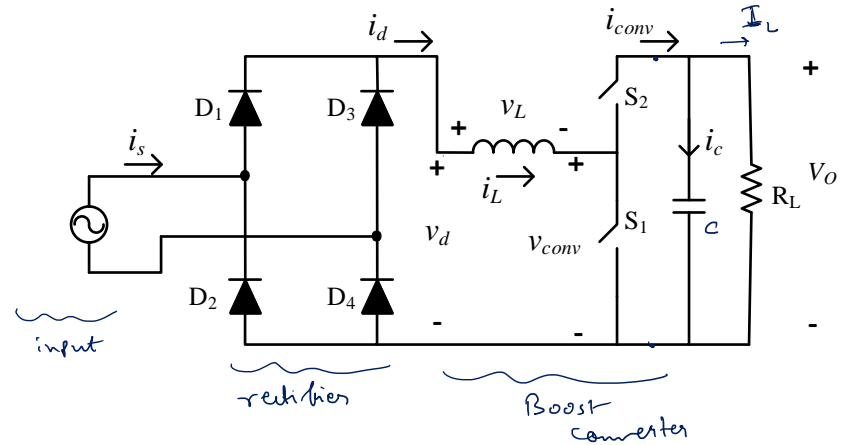


$$\Rightarrow C = \frac{P_L}{\omega \Delta V_o \cdot V_o}$$

$$\Rightarrow C = \frac{P_L}{2\pi f_s \Delta V_o \cdot V_o}$$

$\xrightarrow{\text{specification}}$
 $\xrightarrow{\text{specification}}$
 $\xrightarrow{\text{allowable voltage ripple}}$
 $\xleftarrow{\text{the line freq.}}$

\Rightarrow Capacitor 'C' sees the 2nd line harmonic current & has ripple which is of 2nd line harmonic freq.

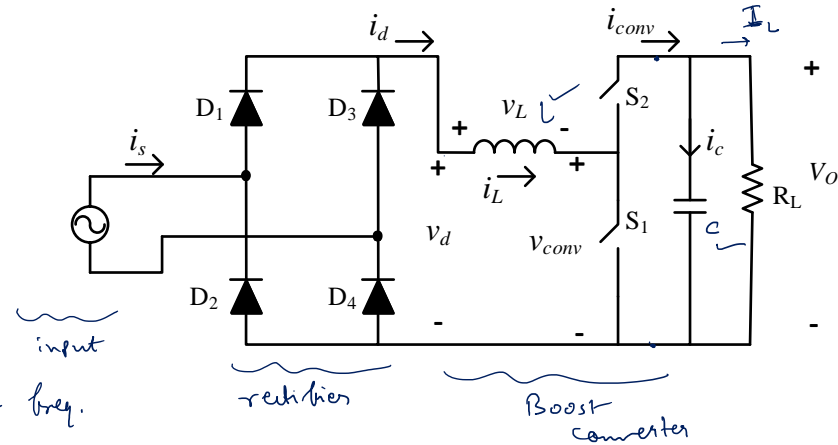\Rightarrow C is of large size because of 2nd line harmonic freq. component



Switch ratings

for S_1

The voltage rating of S_1 , $V_{S1} = V_o$

$$\Rightarrow V_{S1} = 1.4 V_o \quad (40\% - 60\%)$$

$$V_o = 400 \text{ V}$$

$$V_{S1} \approx 650 \text{ V} - 700 \text{ V}$$


$$\hookrightarrow 600 \text{ V}$$

RMS current of S_1

$$\text{The } I_{\text{RMS}, S1} = \sqrt{\frac{1}{T_s} \int_0^{T_s} (i_{S1})^2 dt}$$

$$= \sqrt{\frac{1}{T_s} \left[\int_0^{DT_s} I_o^2 + \int_{DT_s}^{T_s} 0 \right] dt}$$

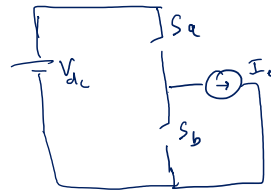
$$= \sqrt{\frac{1}{T_s} I_o^2 \int_0^{DT_s} dt}$$



\Rightarrow when S_a is ON \rightarrow $\frac{\text{Duty ratio}}{\text{Switching period}} = \frac{DT_s}{T_s} = \frac{V_o}{V_{dc}}$

The current through $S_a = I_o$

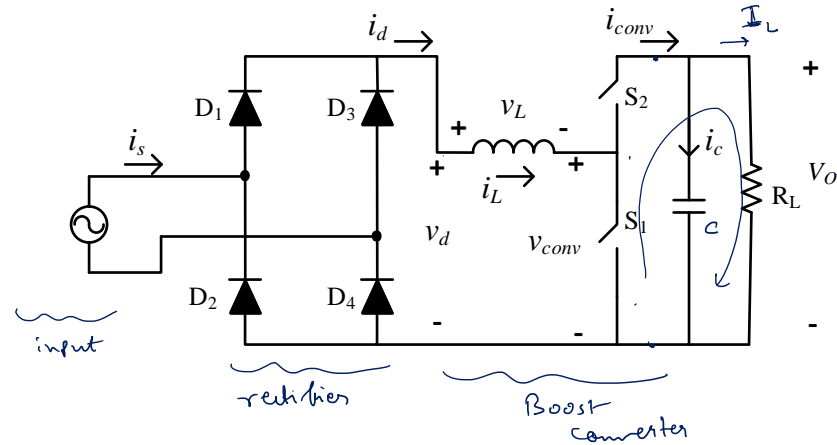\Rightarrow when S_a is off, $(1-D) T_s$
The current through $S_a = 0$



$$\Rightarrow I_{rms,sa} = \sqrt{\frac{1}{T_s} \int_0^{DT_s} I_s^2 dt}$$

$$= \sqrt{\frac{1}{T_s} \int_0^{DT_s} I_o^2 dt}$$

$$I_{rms,sa} = I_o \sqrt{D}$$

Rms current of switch 'S₁'

$$i_s(t) = I_{s,plc} \sin \omega t$$

$$i_{L1}(t) = i_d(t) = I_{s,plc} \sin \omega t \rightarrow \text{in the half cycle}$$

$$\Rightarrow I_{S1,rms} = \sqrt{\frac{1}{T_s} \int_0^{DT_s} (i_s(t))^2 dt}$$

$$I_{S1,rms} = \sqrt{\frac{2}{T} \int_0^{T/2} I_{s,plc}^2 \sin^2 \omega t \left(1 - \frac{|V_{s,plc} \sin \omega t|}{V_o}\right) dt}$$


$P_L =$

$\Rightarrow P_{in} = 3.3 \text{ kW}$

$\Rightarrow \frac{V_{s,plc} I_{s,plc}}{2} = 3.3 \text{ kW}$

$\Rightarrow I_{s,plc} = \frac{3.3 \text{ kW} \times 2}{V_{s,plc}}$

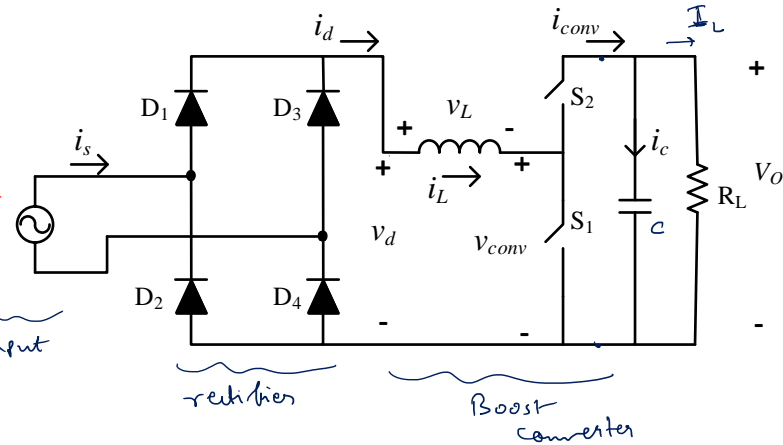$\Rightarrow I_{s,plc} = \frac{P_L \times 2}{V_{s,plc} \text{ input}}$



Thank You

