



IIT ROORKEE



NPTEL ONLINE  
CERTIFICATION COURSE

# Charging Infrastructure


## Lecture-24

### Three-phase AC-DC Converter-II

Dr. Apurv Kumar Yadav  
Department of Electrical Engineering



# Recap

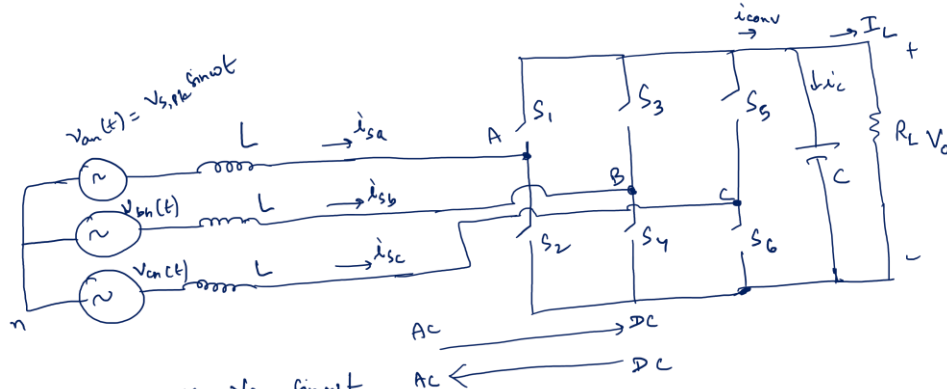

$$\begin{aligned} V_{an}(t) &= V_{s,PK} \sin \omega t \\ V_{bn}(t) &= V_{s,PK} \sin(\omega t - 120^\circ) \\ V_{cn}(t) &= V_{s,PK} \sin(\omega t - 240^\circ) \end{aligned}$$

$$\Rightarrow (\omega L \cdot I_{s,PK}) < 10\% \text{ of } V_{s,PK}$$

↑ required

$$L = \sqrt{\frac{\left(\frac{m V_o}{2}\right)^2 - V_{s,PK}^2}{(2\pi f_s \cdot I_{s,PK})^2}}$$

⇒ the voltage drop across inductor (corresponding to fundamental) must be less than 10% of the  $V_{s,PK}$


⇒ m-modulation index  $\rightarrow$  designer's choice (0.8 to 0.9)

$V_{s,PK} \rightarrow$  specification

$V_o \rightarrow$  specification

$f_s \rightarrow$  line frequency given in specification
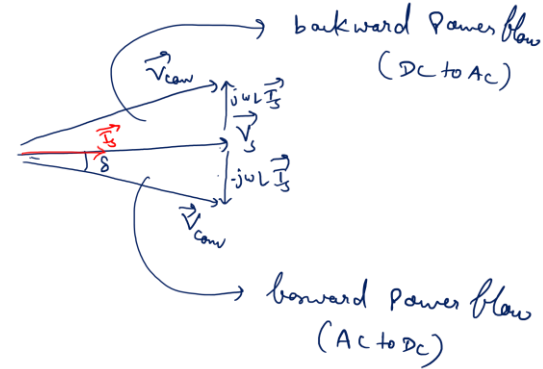
$$I_{s,PK} \rightarrow \frac{P_L \times \sqrt{2}}{3V_{ph,ns}} \leftarrow \text{assuming no loss in the power converter}$$



## Sizing of switches

$$D = \frac{1}{2} + \frac{v_m}{2V_c} \rightarrow \text{carrier signal} \quad \text{(from discussions in lec-22)}$$

$\nearrow$  modulating signal  
 $\searrow$  carrier signal

$\Rightarrow$  In case of SPWM (Sinusoidal PWM)  $\rightarrow v_m = V_m \sin \omega t$

$$\Rightarrow D = \frac{1}{2} + \frac{V_m \sin \omega t}{2V_c}$$

$$\Rightarrow D = \frac{1}{2} + \frac{m}{2} \sin \omega t \quad \left(m = \frac{V_m}{V_c}\right) \rightarrow \text{for } S_1 \text{ switch}$$


$$\Rightarrow \text{for } S_2 \text{ switch} \Rightarrow 1-D \Rightarrow \frac{1}{2} - \frac{m}{2} \sin \omega t$$

gls. Magnet with body diode is used to realize  $S_1$  &  $S_2$  switch

$$I_{rms, S_1} = \sqrt{\frac{1}{T} \int_0^T D \cdot (I_{s, PK} \sin \omega t)^2 dt}$$

$$I_{rms, S_2} = \sqrt{\frac{1}{T} \int_0^T \left(\frac{1}{2} - \frac{m}{2} \sin \omega t\right) (I_{s, PK} \sin \omega t)^2 dt}$$
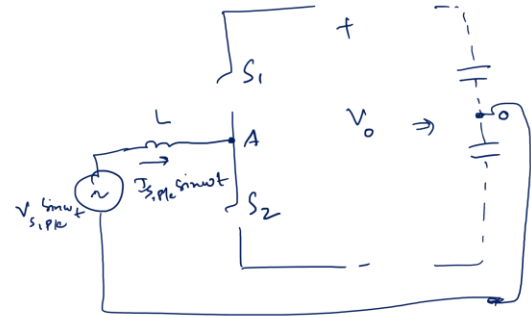
$$I_{rms, S_1} = \sqrt{\frac{1}{T} \int_0^T \left(\frac{1}{2} + \frac{m}{2} \sin \omega t\right) (I_{s, PK} \sin \omega t)^2 dt}$$



$$T = \frac{1}{f_s}$$

$$\Rightarrow \omega T = 2\pi$$


2b  $S_1$  &  $S_2$  switch is realized using IGBT with free wheeling diode

$S_1$  switch is in conduction for  $DT_s$ , during the positive half cycle  
 $D \rightarrow \frac{1}{2} + \frac{m}{2} \sin \omega t$

$D_2$  diode is in conduction for  $(1-D)T_s$  duration  $\rightarrow$  during positive half cycle  
 $1-D \rightarrow \frac{1}{2} - \frac{m}{2} \sin \omega t$

$$\begin{aligned} I_{ave, switch, S_1} &= \frac{1}{T} \int_0^{T/2} \left( \frac{1}{2} + \frac{m}{2} \sin \omega t \right) I_{s, pk} \sin \omega t \cdot dt \\ &= \frac{1}{T} I_{s, pk} \left[ \int_0^{T/2} \left( \frac{1}{2} \sin \omega t \cdot dt \right) + \int_0^{T/2} \left( \frac{m}{2} \sin^2 \omega t \cdot dt \right) \right] \\ &= \frac{I_{s, pk}}{2\pi} \left[ 1 + \frac{\pi m}{4} \right] \end{aligned}$$

UPF operation

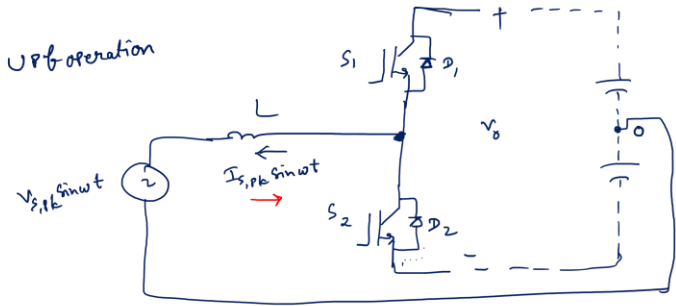

In positive half cycle,  $V_s > 0$   $T_s = 1/f_{sw}$

$\Rightarrow S_1 \rightarrow DT_s$  } in conduction  
 $D_2 \rightarrow (1-D)T_s$

In negative half cycle,  $V_s < 0$   
 $S_2 \rightarrow (1-D)T_s$  } in conduction  
 $D_1 \rightarrow DT_s$

$$I_{rms, \text{ switch, } s_1} = \sqrt{I_T \int_0^{T/2} D(I_{s, pk} \sin \omega t)^2 dt} = \sqrt{I_T \int_0^{T/2} \left(\frac{1}{2} + \frac{m}{2} \sin \omega t\right) (I_{s, pk} \sin \omega t)^2 dt} = \frac{I_{s, pk}}{2\sqrt{2}} \sqrt{1 + \frac{8m}{3\pi}}$$


$$\begin{aligned} \Rightarrow I_{avg, \text{ diode, } D_1} &= I_T \int_0^{T/2} (1-D) I_{s, pk} \sin \omega t \cdot dt \\ &= I_T \int_0^{T/2} \left(\frac{1}{2} - \frac{m}{2} \sin \omega t\right) I_{s, pk} \sin \omega t \cdot dt \\ &= \frac{I_{s, pk}}{2\pi} \left[1 - \frac{m\pi}{4}\right] \end{aligned}$$

$$\begin{aligned} I_{rms, \text{ diode, } D_1} &= \sqrt{I_T \int_0^{T/2} (1-D) (I_{s, pk} \sin \omega t)^2 \cdot dt} \\ &= \sqrt{I_T \int_0^{T/2} \left(\frac{1}{2} - \frac{m}{2} \sin \omega t\right) (I_{s, pk} \sin \omega t)^2 \cdot dt} \end{aligned}$$

$$I_{rms, \text{ diode, } D_1} = \frac{I_{s, pk}}{2\sqrt{2}} \sqrt{1 - \frac{8m}{3\pi}}$$

voltage stress across  $S_1$  &  $S_2 = V_o$

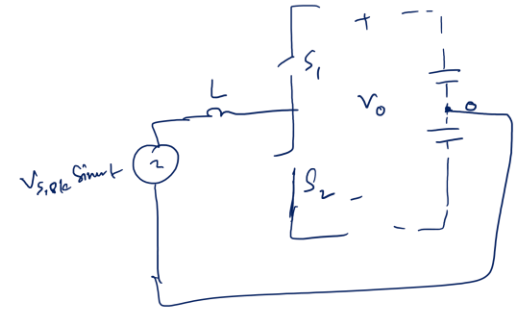The voltage rating of  $S_1$  &  $S_2 = 1.4V_o$  (40%  $\rightarrow$  safety margin)




$\rightarrow$  due to parasitic inductances of the loop  $= L_{\text{parasitic}} \frac{di}{dt}$   
 $V_o$   
 $\rightarrow$  voltage across switches  $S_1$  &  $S_2$

## Sizing of Capacitors

⇒ The output power (at AB terminal)

$$= V_o \cdot i_{conv}$$

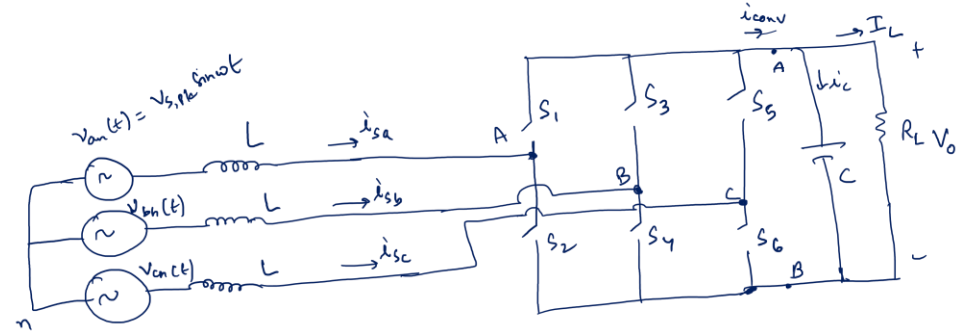Input power =  $V_{s, pk} \sin \omega t \cdot I_{s, pk} \sin \omega t$  → assuming upf operation  
 $+ V_{s, pk} \sin(\omega t - 120^\circ) \cdot I_{s, pk} \sin(\omega t - 120^\circ)$   
 $+ V_{s, pk} \sin(\omega t - 240^\circ) \cdot I_{s, pk} \sin(\omega t - 240^\circ)$



If there is loss-less converter

Apply power balance

⇒ Input power = Output power

$$\Rightarrow V_o \cdot i_{conv} = V_{s, pk} \sin \omega t \cdot I_{s, pk} \sin \omega t + V_{s, pk} \sin(\omega t - 120^\circ) \cdot I_{s, pk} \sin(\omega t - 120^\circ) + V_{s, pk} \sin(\omega t - 240^\circ) \cdot I_{s, pk} \sin(\omega t - 240^\circ)$$

$$= V_{s, pk} I_{s, pk} \left( \sin^2 \omega t + \sin^2(\omega t - 120^\circ) + \sin^2(\omega t - 240^\circ) \right)$$


$$= V_{s, pk} I_{s, pk} \left( \frac{1 - \cos 2\omega t}{2} + \frac{1 - \cos(2\omega t - 240^\circ)}{2} + \frac{1 - \cos(2\omega t - 480^\circ)}{2} \right)$$

$$= V_{s, pk} I_{s, pk} \left( \frac{3}{2} - \underbrace{\left( \cos 2\omega t + \cos(2\omega t - 240^\circ) + \cos(2\omega t - 480^\circ) \right)}_{= 0} \right)$$

$$\Rightarrow V_0, i_{con} = \frac{3}{2} V_{s,pk} \cdot I_{s,pk}$$

$$\Rightarrow i_{con} = \frac{3}{2V_0} V_{s,pk} \cdot I_{s,pk} \longrightarrow \text{there is absence of 2nd line freq. component (only DC-component exist)}$$


fundamental frequency

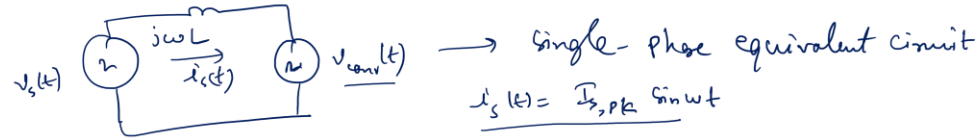

$v_{con}(t) \rightarrow$  fundamental component along with harmonic frequency component at side band of  $m_f (m_f = \frac{b_c}{b_m}) \approx$  carrier frequency

harmonic frequency component

The single phase equivalent circuit

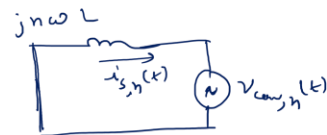

$$\Rightarrow i_{s,n}(t) = \frac{v_{con,n}(t)}{jn\omega L}$$

$$\begin{aligned} \omega &= 2\pi f_m \\ b_m &= b_s \\ \omega &= 2\pi b_s \end{aligned}$$



# Thank You

