



IIT ROORKEE



NPTEL ONLINE
CERTIFICATION COURSE

Charging Infrastructure



Lecture-20

DCM operation of Boost PFC Converter

Dr. Apurv Kumar Yadav
Department of Electrical Engineering




Recap

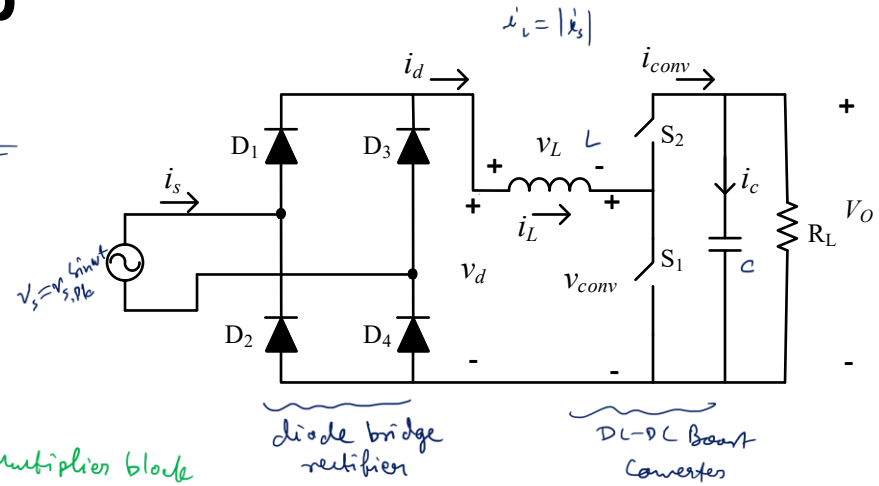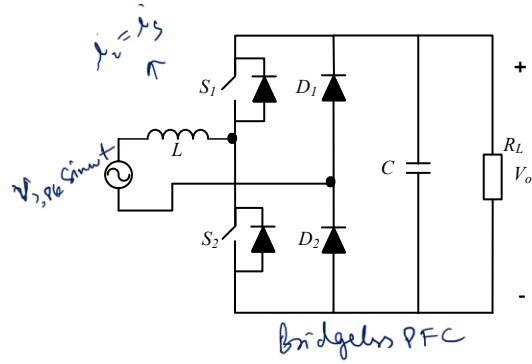


→ Multiplier block

↳ Multiplier control approach

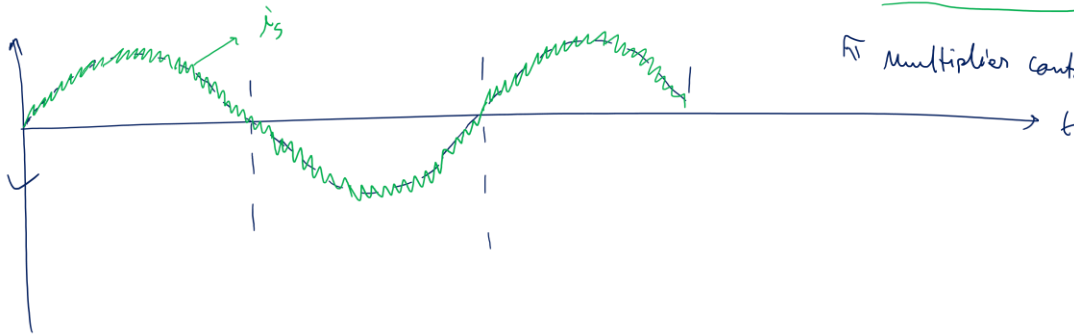

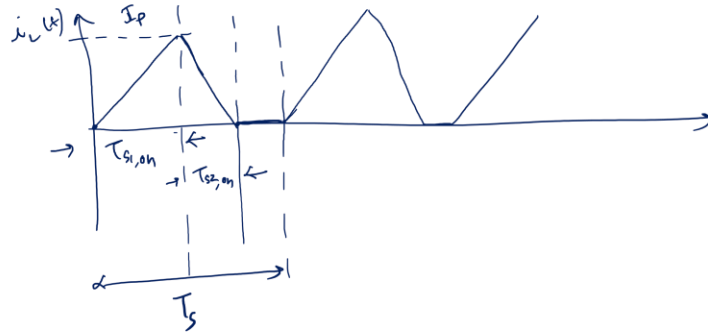DCM of Boost PFC, in one of the switching cycle ' T_s '



$$V_L = L \frac{di}{dt} = |V_s|$$


$$|V_s| = \frac{L I_p}{T_{s1,on}}$$

$$\Rightarrow I_p = \frac{|V_s| T_{s1,on}}{L}$$

if $T_{s1,on}$ is constant, then the I_p (pk of inductor current) follows the $|V_s|$ variation \Rightarrow AC voltage

I_p is varying in sinusoidal manner.

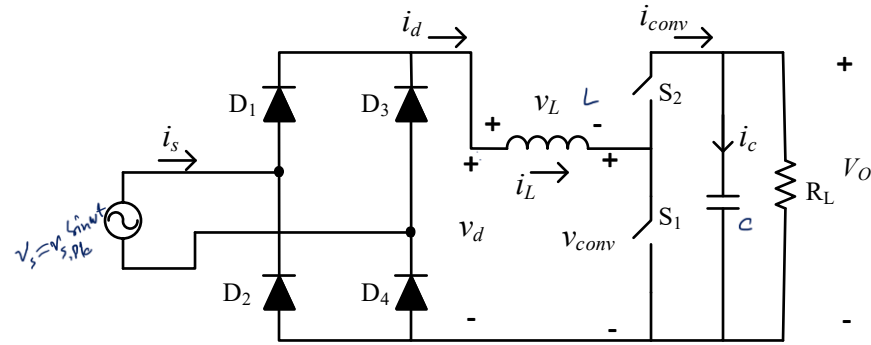$T_{s1,on} \rightarrow$ switch ' S_1 ' is ON



$$V_d = |V_s|$$

$$\Rightarrow i_s = i_L, V_s > 0 \\ = -i_L, V_s < 0$$

$$\langle \dot{i}_L(t) \rangle_{T_s} = \frac{1}{2} \times \frac{|v_s| \cdot T_{s1, on}}{L} \times \frac{(T_{s1, on} + T_{s2, on})}{T_s}$$

$$\text{let, } D_1 = \frac{T_{s1, on}}{T_s} ; D_2 = \frac{T_{s2, on}}{T_s}$$

$$\Rightarrow \langle \dot{i}_L(t) \rangle_{T_s} = \frac{1}{2} \left[\frac{|v_s(t)| T_{s1, on}}{L} (D_1 + D_2) \right]$$

$$\langle \dot{i}_L(t) \rangle_{T_s} = \frac{1}{2} \left[\frac{|v_s(t)| D_1 T_s}{L} (D_1 + D_2) \right] \rightarrow (1)$$


volt-sec

$$|v_s(t)| D_1 T_s + (|v_s(t)| - V_o) D_2 T_s = 0$$

$$\Rightarrow D_2 = \frac{|v_s(t)|}{V_o - |v_s(t)|} \cdot D_1 \rightarrow (2)$$

Substitute (2) in (1)

$$\langle \dot{i}_L(t) \rangle_{T_s} = \frac{1}{2} |v_s(t)| \cdot D_1 T_s \cdot \left[D_1 + \frac{|v_s(t)|}{V_o - |v_s(t)|} \cdot D_1 \right]$$

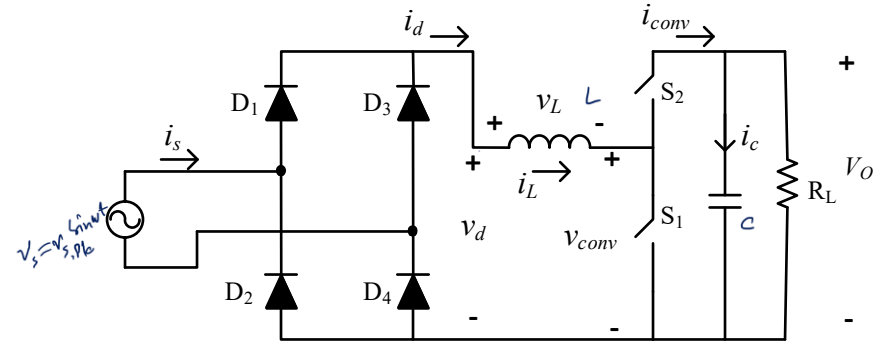



$$\Rightarrow \langle i_L(t) \rangle_{T_s} = \frac{1}{2} \cdot |v_s(t)| \cdot D_1^2 T_s \left[\frac{V_o}{V_o - |v_s(t)|} \right]$$

$$i_s(t) = i_L(t), v_s > 0$$

$$= -i_L(t), v_s < 0$$

$$\Rightarrow \langle i_s(t) \rangle_{T_s} = \frac{1}{2} |V_{s,pk} \sin \omega t| D_1^2 T_s \left[\frac{V_o}{V_o - |V_{s,pk} \sin \omega t|} \right]$$

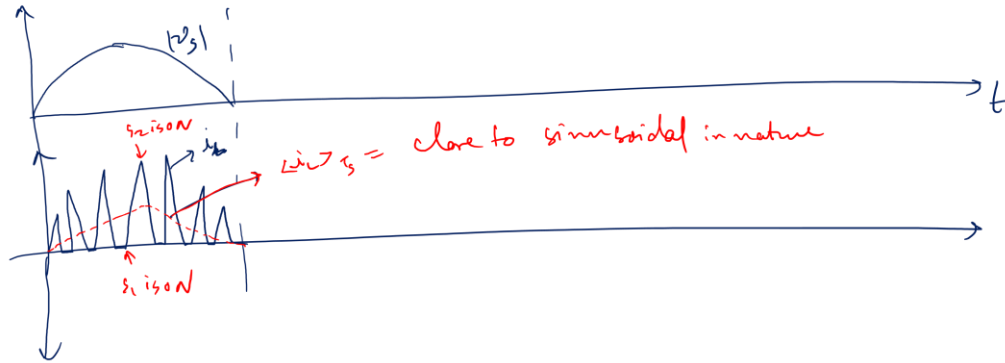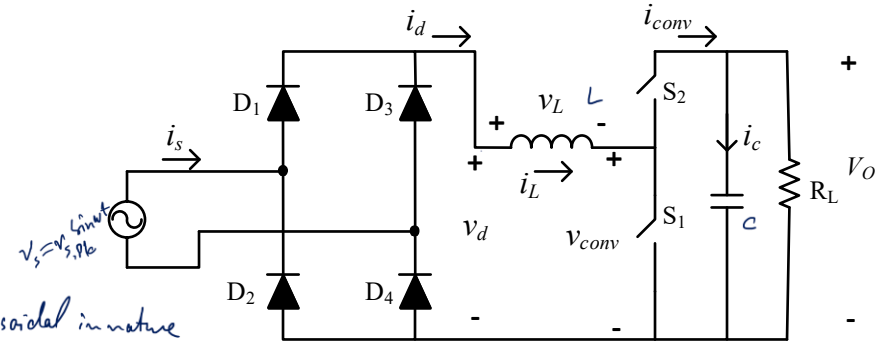if we keep D_1 & T_s constant i.e., $T_{s,on}$ is kept constant, we can ensure that $\langle i_L(t) \rangle_{T_s}$ is sinusoidal in nature




Advantages

- ① The current drawn from the source, follows the AC voltage.
- ② The use of multiplier, dual loop, unit sinewave waveform is provided.
- ③ Reduced switching loss as if diode is used in place of S_2 , the reverse recovery loss of diode is nearly zero.

Disadvantage

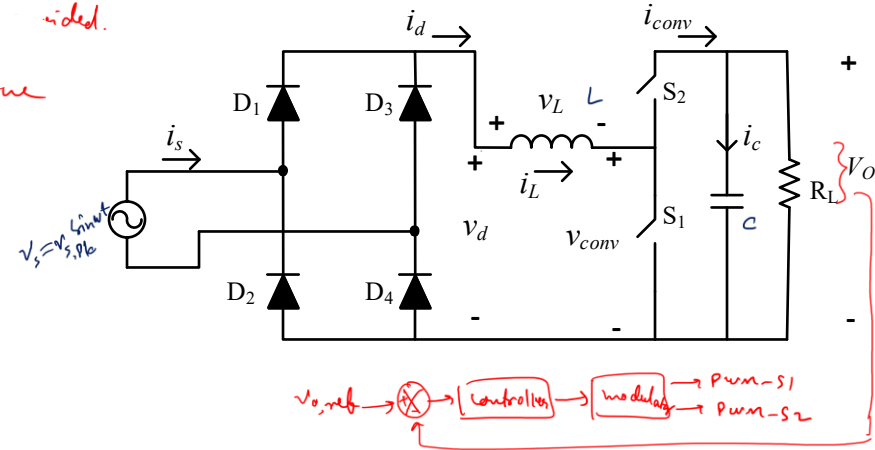- ① ^{average} Input current is close to sinewave, THD is more
- ② Ripple is more
- ③ RMS currents of $S_1, S_2, L, D_1, D_2, D_3, D_4$ are more
- ④ S_1 turns off with higher current.



Thank You

