



IIT ROORKEE



NPTEL ONLINE  
CERTIFICATION COURSE

# Charging Infrastructure

## Lecture-31

### Revisiting Isolated DC-DC Converters-II


**Dr. Apurv Kumar Yadav**  
Department of Electrical Engineering



# Recap
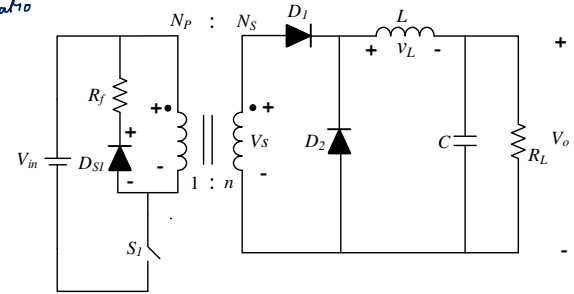
## Disadvantage

- ① Sufficient  $(1-D)T_S \rightarrow$  limits the switching freq. } - limited duty ratio  
as flux in the transformer core must get reset to 0.
- ② The reverse recovery losses of the diode
- ③ Long reset of the flux in the transformer
- ④ Core utilization is limited  $\approx$  half
- ⑤ The switch ' $S_1$ ' voltage rating is higher than  $V_{in}$ .




$$V = N \Delta B \cdot A \cdot f$$

$$A_c = \frac{V}{N B_{max} f}$$

if the  $\Delta B \rightarrow +B_{max}$  to  $-B_{max}$

$$A_c = \frac{V}{2N B_{max} f}$$

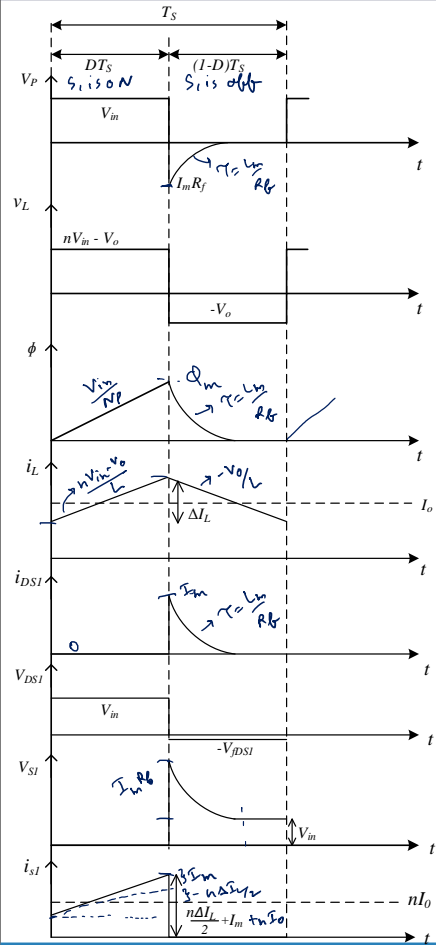


## Forward Converter with Demagnetizing winding

$I_m \rightarrow$  magnetizing component of current, which led to  $\phi_m$
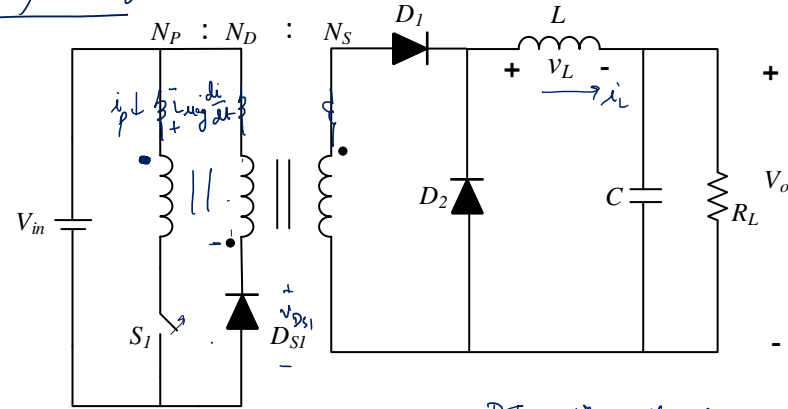
### Disadvantage

- ① Multi winding transformer
- ② limited switching freq.
- ③  $V_{DS1}$  rating is greater than  $V_{in}$
- ④ Transformer is under utilization
- ⑤ The voltage kick on switch  $S_1$  due to leakage inductance



$$DT_s \rightarrow v_L = nV_{in} - v_o$$



$$(-D)T_s \rightarrow v_L = -v_o$$

$$\Rightarrow v_o = nV_{in}D$$



$$V_{S1} = V_{in} + \frac{N_p}{N_D} V_{in}$$

$$I_m \rightarrow \phi_m$$

$$N_p \cdot I_m = I_{D1} \cdot N_D$$

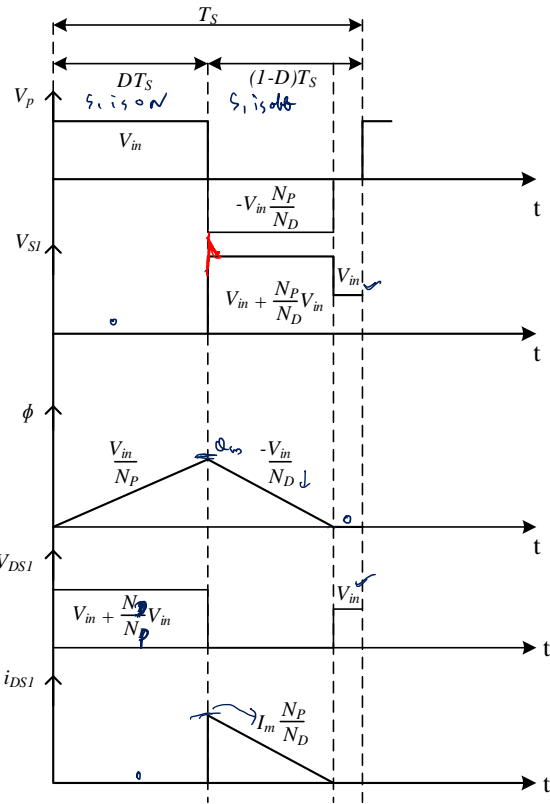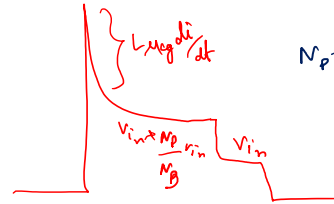

## Dual Switch Forward converters

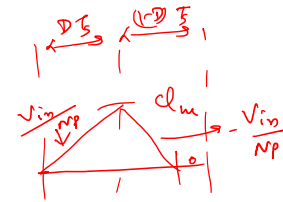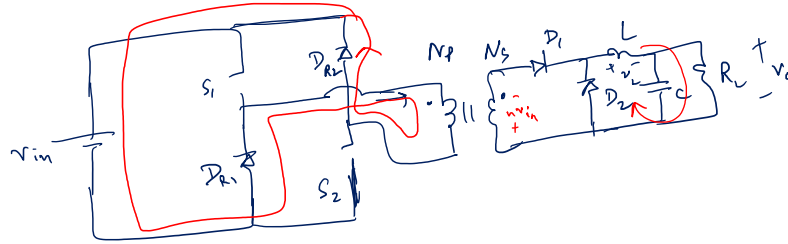


$T_s$  period  $\rightarrow S_1 \& S_2$  is ON  
 $\Rightarrow V_L = nV_{in} - V_o$

$\Rightarrow (1-D) T_s$  period  $\rightarrow S_1 \& S_2$  is off  
 $\Rightarrow V_L = -V_o$


voltage sec across 'L'  
 $\Rightarrow V_o = nV_{in}D$

- $\Rightarrow S_1 \& S_2 \rightarrow$  voltage rating =  $V_{in}$
- $\Rightarrow$  but it uses two switch & two diodes in primary side.
- $\Rightarrow$  limited switching freq.
- $\Rightarrow$  reverse recovery losses ( $D_1 \& D_2$ )
- $\Rightarrow$  core utilization is half

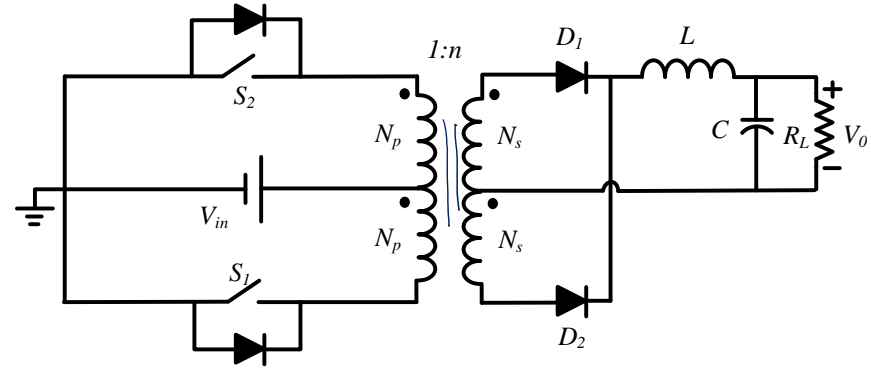
Push-pull based DC-DC Converter  
→ 4 sets of transformer winding




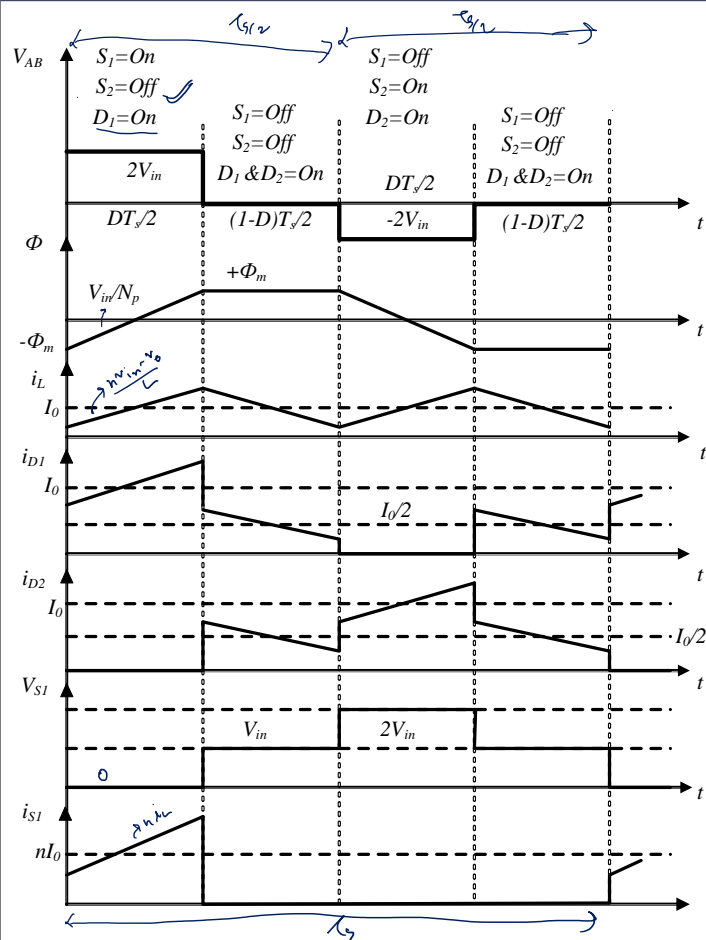
Source: Power Electronics: Essentials & Applications by L Umanand



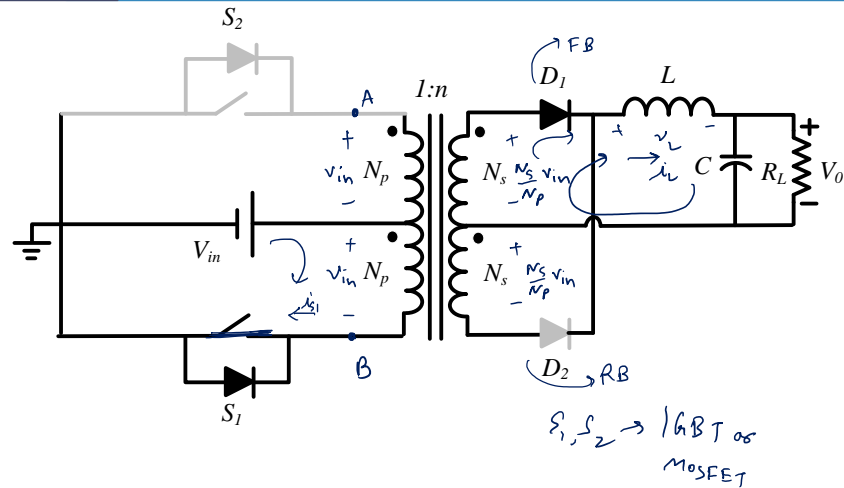
$\frac{N_s}{N_p} = n$   
 $(DT_s/2 \text{ period})$   
 $(V_L = nV_{in} - V_o)$   
 $nV_{in} > V_o$   
 $\Rightarrow$



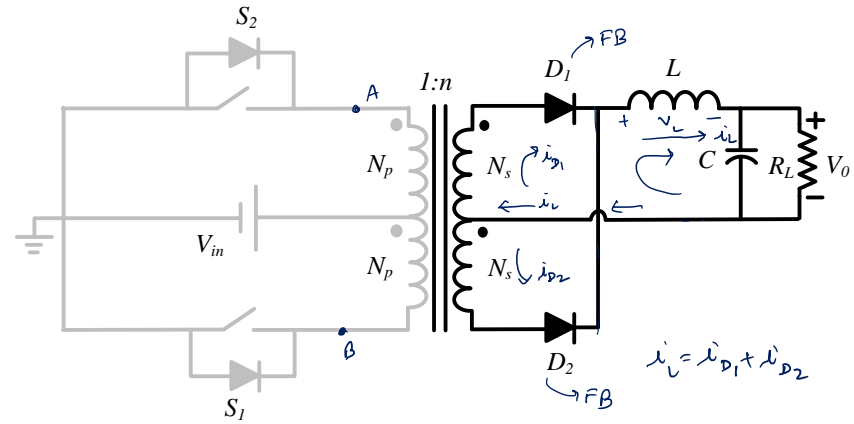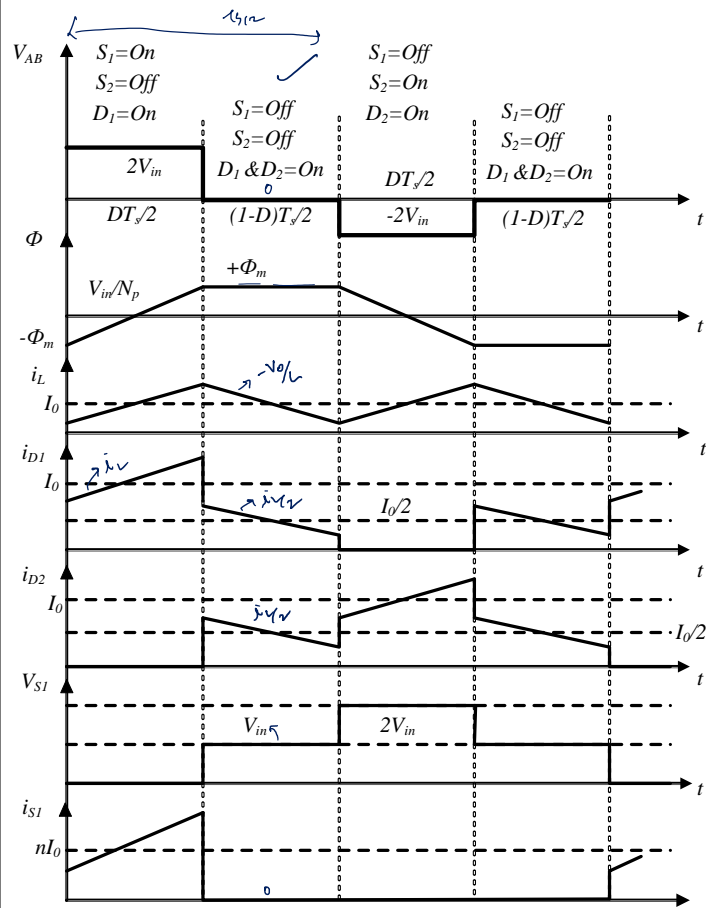Source: Power Electronics: Essentials & Applications by L Umanand



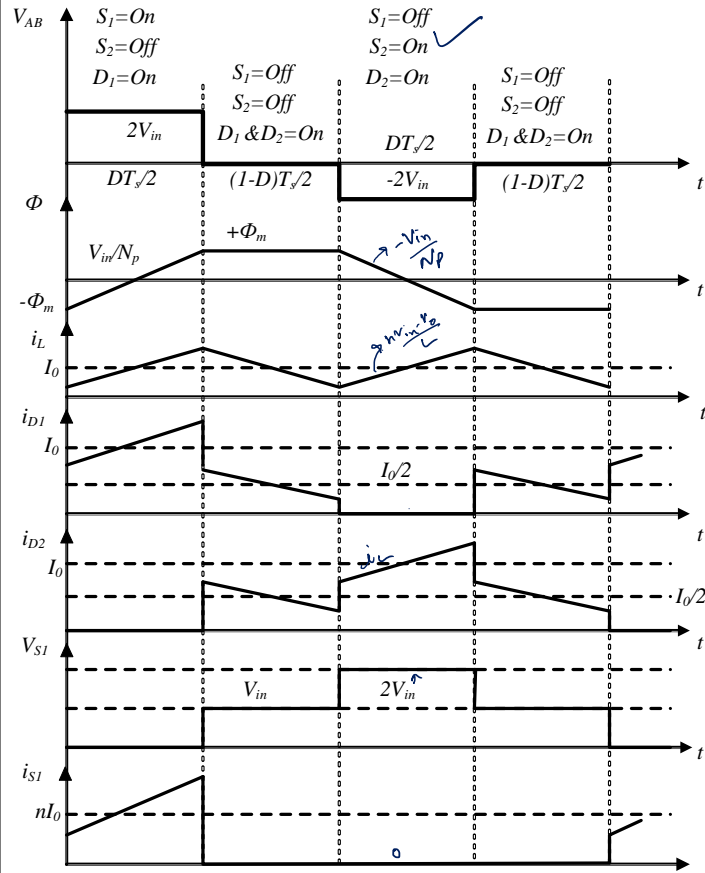
$$\begin{aligned} \frac{d\phi}{dt} &= V \\ \frac{d\phi}{dt} &= 0 \end{aligned}$$



Next,  $\frac{DT_s}{2}$ , period


$$V_L = nV_{in} \sim \frac{V_0}{2}$$

$$nV_{in} > V_0$$

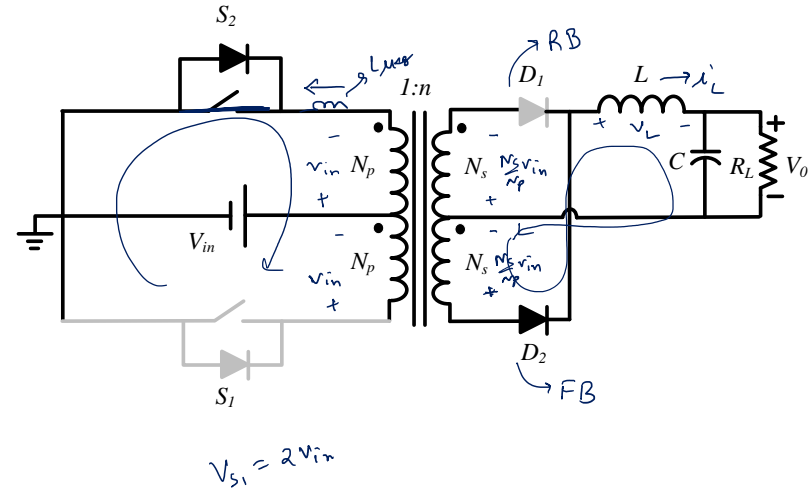

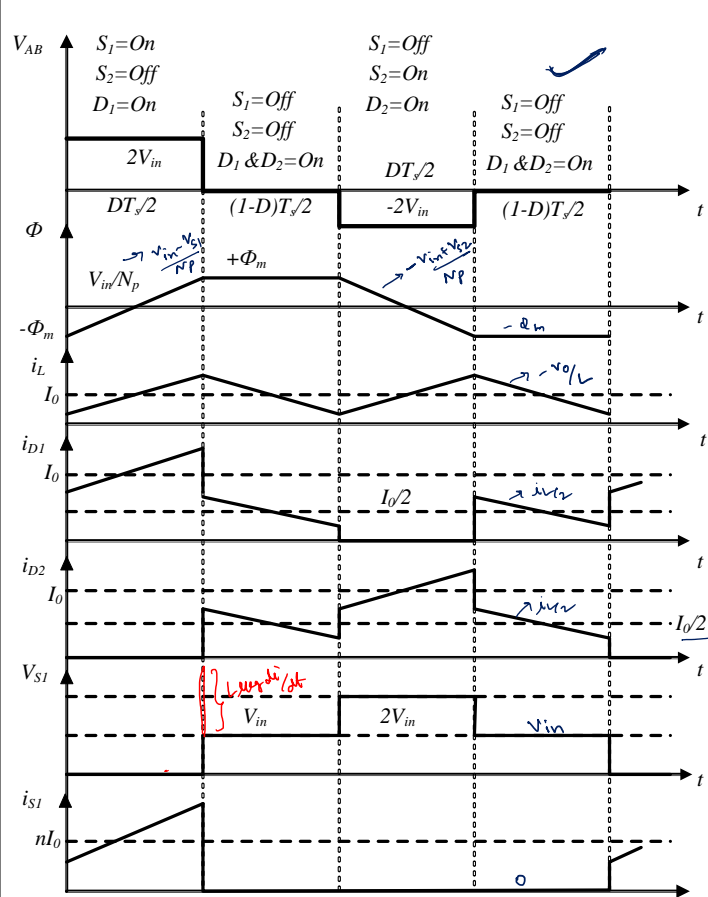Source: Power Electronics: Essentials & Applications by L Umanand





$$V_{L_{avg}} = \frac{(1-D)T_s}{2}$$

$$V_L = -V_0$$


$$\text{volt-sec ab } \int V_L dt$$

$$(nV_{in} - V_0) \frac{DT_s}{2} + (-V_0) \frac{(1-D)T_s}{2} = 0$$

$$\Rightarrow V_0 = nDV_{in}$$

$$V = NAB \cdot A_c \cdot f$$
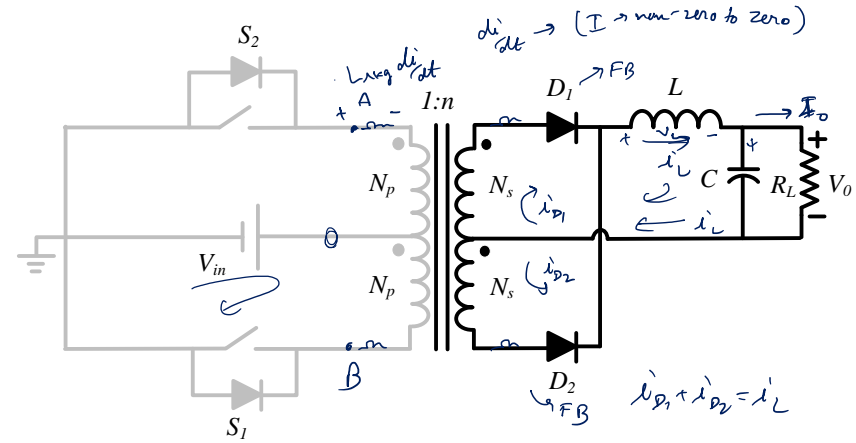
$$\Rightarrow A_c = \frac{V}{2N B_{max} f}$$




### Advantage

- ① Core is fully utilized
- ② The cut-off frequency is  $2 \times f_{sw}$  (of L & C)
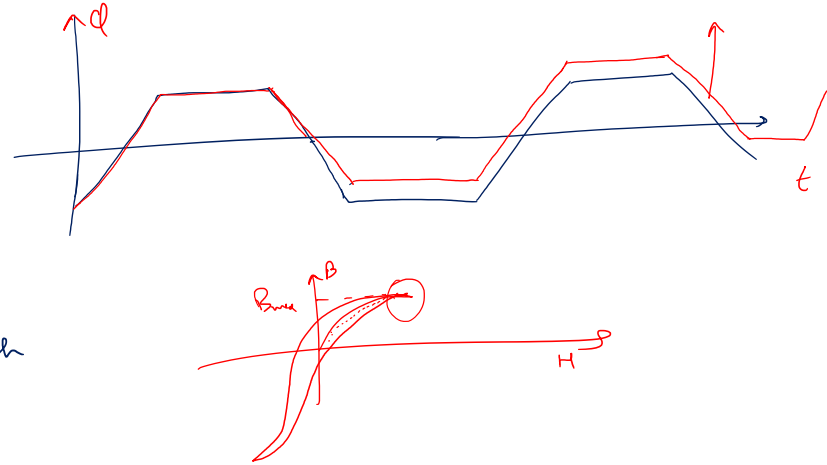
### Disadvantage

- ①  $S_1, S_2$  rating are doubled ( $2V_{in}$ )
- ② flux walking phenomenon which lead to core saturation
- ③ The voltage kick <sup>(on  $S_1$  &  $S_2$  switch)</sup> due to the sudden breaking of current through leakage inductance  $\rightarrow V_{S1}$  &  $V_{S2}$
- ④ L winding transformer need to be wound.



# Thank You

