



IIT ROORKEE



NPTEL ONLINE
CERTIFICATION COURSE

Charging Infrastructure

Lecture-14


Closed Loop Control of Single-phase Boost PFC Converter-II

Dr. Apurv Kumar Yadav

Department of Electrical Engineering



Recap

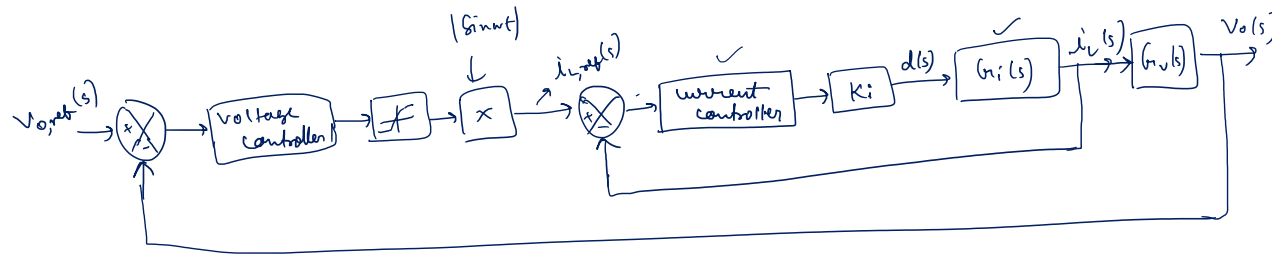

$$G_i(s) = \frac{i_L(s)}{d(s)}$$

$$G_v(s) = \frac{V_o(s)}{i_L(s)} \approx \frac{V_L(s)}{i_L(s)}$$

Small Signal Model

Average large signal model using state equations

↓
perturbation

↓
linearize the state equation around the operating point

↓
time-domain to s-domain

State variables: i_L, v_C

Input : d, v_s

output : V_0

in one of the switching period,
the duty ratio of $S_1 = D$

the $v_d = |v_s|$


In the positive half-cycle

During DT₂ period,

$$\Rightarrow L \frac{di_L}{dt} = |v_s| \Rightarrow \frac{di_L}{dt} = \frac{|v_s|}{L}$$

$$v_c = -i_c R_L$$
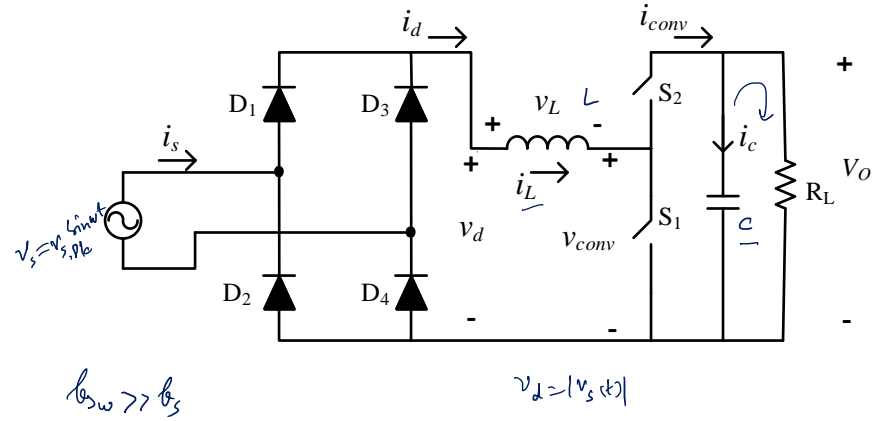
$$\Rightarrow C \frac{dv_c}{dt} = -\frac{v_c}{R_L}$$



$$\frac{dv_c}{dt} = -\frac{v_c}{R_L C}$$

$$\text{input} = |v_s|$$

$$V_o = v_c$$

$\Rightarrow i_L, v_c$ are the state variable $\Rightarrow x = \begin{bmatrix} i_L \\ v_c \end{bmatrix}$

$$\dot{x} = \begin{bmatrix} \frac{di_L}{dt} \\ \frac{dv_c}{dt} \end{bmatrix} = \begin{bmatrix} 0 & 0 \\ 0 & -\frac{1}{R_L C} \end{bmatrix} x + \begin{bmatrix} V_L \\ 0 \end{bmatrix} \frac{|v_s|}{V_s}$$

$$v_o = \begin{bmatrix} 0 & 1 \end{bmatrix} \begin{bmatrix} i_L \\ v_c \end{bmatrix} + \begin{bmatrix} 0 \\ 1 \end{bmatrix} \frac{|v_s|}{V_s}$$


(1-5) T₁,

$$\frac{di_L}{dt} = \frac{1}{L} (|v_s| - v_c)$$

$$i_{conv} = i_L$$

$$\Rightarrow i_L = i_c + I_L$$
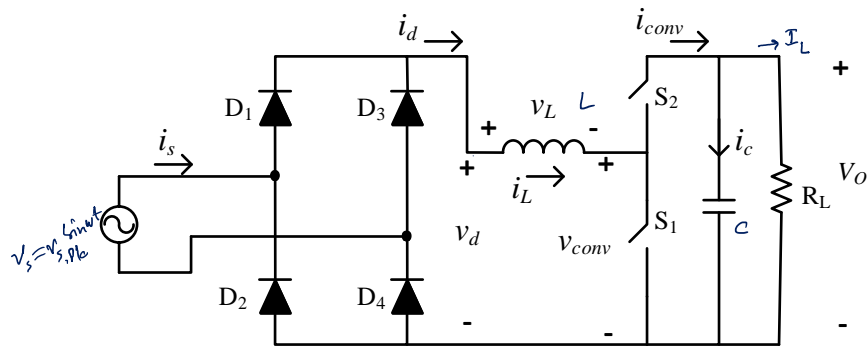
$$\Rightarrow i_c = i_L - \frac{v_c}{R_L}$$



$$\Rightarrow \dot{i}_c = \dot{i}_L - \frac{v_c}{R_L}$$

$$\Rightarrow \frac{dv_c}{dt} = \frac{1}{C} \dot{i}_c$$


$$= \frac{1}{C} \left[\dot{i}_L - \frac{v_c}{R_L} \right]$$

$$\Rightarrow \frac{dv_c}{dt} = \frac{1}{C} \dot{i}_L - \frac{1}{R_L C} v_c$$

$$\Rightarrow V_o = v_c$$

$$\begin{bmatrix} \dot{\overset{x}{i_L}} \\ \dot{\overset{x}{v_c}} \end{bmatrix} = \overset{A_L}{\begin{bmatrix} 0 & -\frac{1}{L} \\ \frac{1}{C} & -\frac{1}{R_L C} \end{bmatrix}} \begin{bmatrix} \overset{x}{i_L} \\ \overset{x}{v_c} \end{bmatrix} + \overset{B_L}{\begin{bmatrix} \frac{1}{L} \\ 0 \end{bmatrix}} \overset{V_s}{v_s}$$
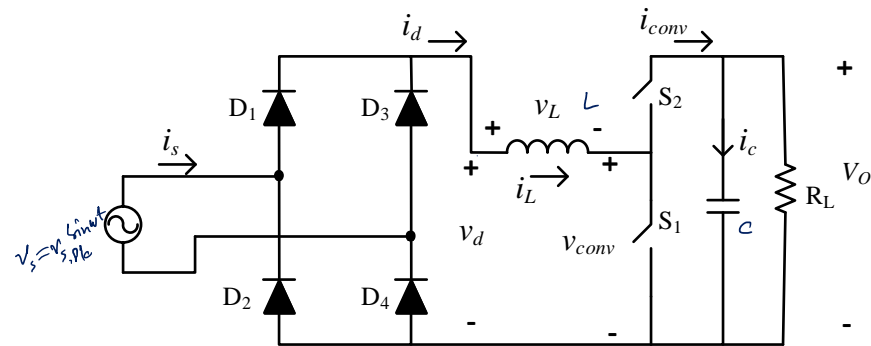
$$V_o = \overset{C_L}{\begin{bmatrix} 0 & 1 \end{bmatrix}} \begin{bmatrix} \overset{x}{i_L} \\ \overset{x}{v_c} \end{bmatrix} + \overset{D_L}{\begin{bmatrix} 0 \end{bmatrix}} \overset{V_s}{v_s}$$



$$\dot{x} = \frac{(A_1 x + B_1 |v_s|)D T_s + (A_2 x + B_2 |v_s|)(1-D) T_s}{T_s}$$

$$\Rightarrow \dot{x} = (A_1 x + B_1 |v_s|)D + (A_2 x + B_2 |v_s|)(1-D) \rightarrow \textcircled{1}$$


$$v_o = [C_1 x]D + [C_2 x](1-D) \rightarrow \textcircled{2}$$

Rearranging eq. $\textcircled{1}$ & $\textcircled{2}$

$$\Rightarrow \dot{x} = \underbrace{[A_1 D + A_2 (1-D)]}_A x + \underbrace{[B_1 D + B_2 (1-D)]}_B |v_s|$$

$$\Rightarrow v_o = \underbrace{[C_1 D + C_2 (1-D)]}_C x$$

$$\Rightarrow \left. \begin{aligned} \dot{x} &= A x + B |v_s| \\ v_o &= C x \end{aligned} \right\} \rightarrow \text{Average large signal model using state space representation}$$

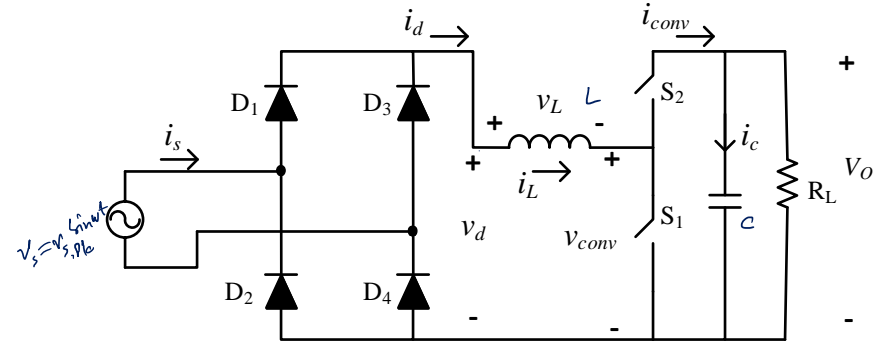


$$A = \begin{bmatrix} 0 & -\frac{(1-D)}{L} \\ \frac{1-D}{C} & -\frac{1}{R_L C} \end{bmatrix}; \quad B = \begin{bmatrix} \frac{V_L}{L} \\ 0 \end{bmatrix}$$

$$C = \begin{bmatrix} 0 & 1 \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} \frac{di_L}{dt} \\ \frac{dv_C}{dt} \end{bmatrix} = \begin{bmatrix} 0 & -\frac{(1-D)}{L} \\ \frac{1-D}{C} & -\frac{1}{R_L C} \end{bmatrix} \begin{bmatrix} i_L \\ v_C \end{bmatrix} + \begin{bmatrix} \frac{V_L}{L} \\ 0 \end{bmatrix} |v_s|$$
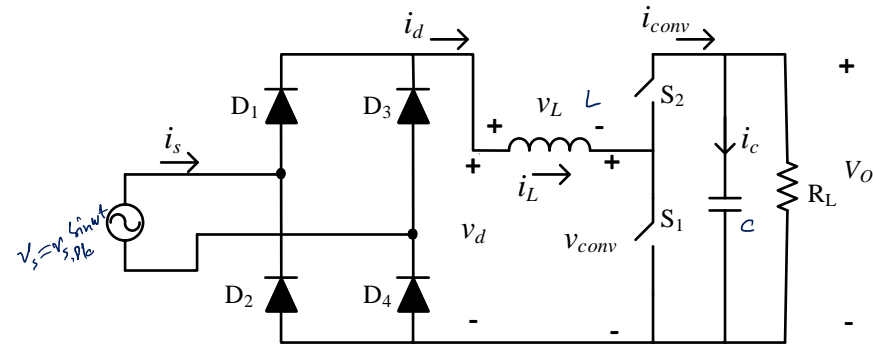
$$V_o = \begin{bmatrix} 0 & 1 \end{bmatrix} \begin{bmatrix} i_L \\ v_C \end{bmatrix}$$



Thank You

