



IIT ROORKEE



NPTEL ONLINE
CERTIFICATION COURSE

Charging Infrastructure

Lecture-7


Revisiting Diode Bridge Rectifier with Capacitive Filter

Dr. Apurv Kumar Yadav

Department of Electrical Engineering



Recap

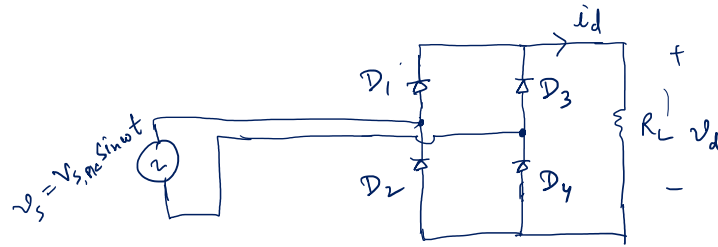


→ full-bridge uncontrolled rectifier

Inference


- The output voltage is uncontrolled, it only depends on input AC voltage (V_s, ω)
- The input current is sinusoidal in nature
- Power is delivered in both the cycle (+ve & -ve) to R_L .
- The output voltage is not constant, it is rectified DC voltage
 $\Rightarrow v_d(t) = |v_s(t)|$
 it is continuously varying

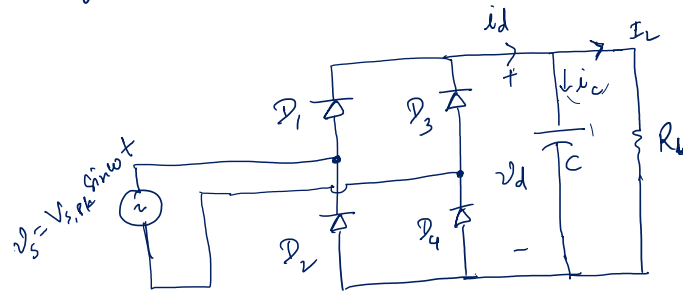1- ϕ full-bridge rectifier with Capacitive filter



→ from t_a to t_b , the Capacitor 'C' is charging, while in the remaining portion of $T/2$, the Capacitor is discharging

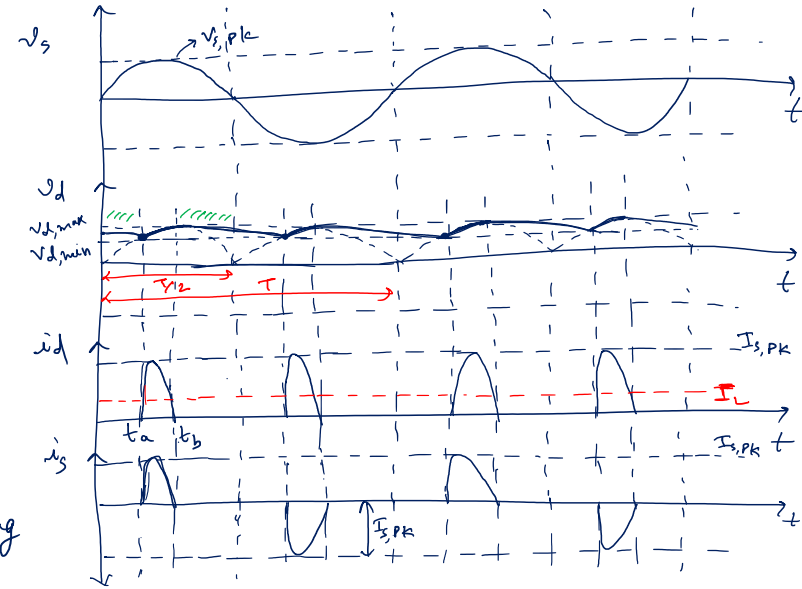→ To maintain the voltage between $V_{d,max}$ & $V_{d,min}$ the energy ^{gained} during charging is equal to Energy lost during discharging



$$T = 1/f_s$$

$$\omega = 2\pi f_s$$

$$\Rightarrow \omega T = 2\pi$$

$$\text{Energy gained during charging} \Rightarrow E_c = \frac{1}{2} C (v_{d,\max}^2 - v_{d,\min}^2) \longrightarrow (1)$$

Let, P_L be the load power (power delivered to load)

\Rightarrow Energy delivered to load from Capacitor during T_2

$$E_d = P_L \times \frac{T}{2} \times \left[\frac{T_2 - t_c}{T_2} \right] \quad [t_c = t_b - t_a]$$

$$E_d = P_L \times \frac{T}{2} \times \left[1 - \frac{t_c}{T_2} \right] \longrightarrow (2)$$

$$\Rightarrow E_d = E_c \quad (\text{to ensure the capacitor voltage is between } v_{d,\max} \text{ \& } v_{d,\min})$$

$$\Rightarrow \frac{1}{2} C (v_{d,\max}^2 - v_{d,\min}^2) = P_L \times \frac{T}{2} \times \left[1 - \frac{t_c}{T_2} \right]$$

$$C = \left(1 - \frac{t_c}{T_s}\right) \times \frac{P_L}{(V_{d,max}^2 - V_{d,min}^2)} \times T \longrightarrow (3)$$

$$V_{d,max}^2 - V_{d,min}^2 = (V_{d,max} + V_{d,min}) (V_{d,max} - V_{d,min}) \longrightarrow (4)$$

$$\Rightarrow \Delta V_o = V_{d,max} - V_{d,min} \quad (\text{output voltage ripple})$$

$$\Rightarrow \frac{V_{d,max} + V_{d,min}}{2} = V_o \quad (V_o \rightarrow \text{nominal output DC voltage})$$

$$\Rightarrow V_{d,max}^2 - V_{d,min}^2 = 2 V_o \cdot \Delta V_o \longrightarrow (5)$$

Substitute (5) in (3)

$$\Rightarrow C = \left(1 - \frac{t_c}{T_s}\right) \times \frac{P_L}{2 V_o \cdot \Delta V_o} \times \frac{1}{f_s} \longrightarrow 50 \mu\text{s}$$

In order to select the Capacitor

✓ → Capacitance value

✓ → voltage rating → $V_{d,max} = V_o + \frac{\Delta V_o}{2}$

→ RMS current through the Capacitor → will determine the parallel connection in the Capacitor bank



Thank You

