



IIT ROORKEE



NPTEL ONLINE
CERTIFICATION COURSE

Charging Infrastructure


Lecture-9

Single-phase Boost PFC Converter


Dr. Apurv Kumar Yadav
Department of Electrical Engineering



Recap


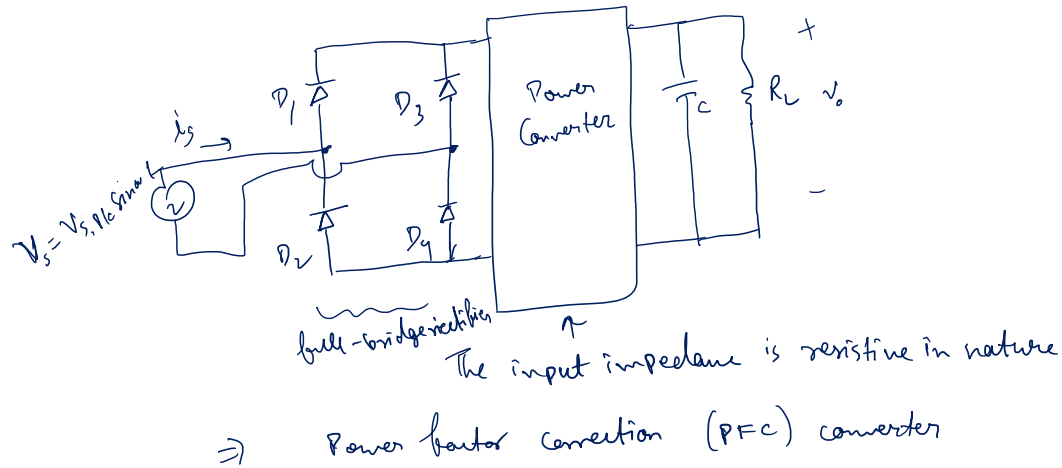


Boost PFC

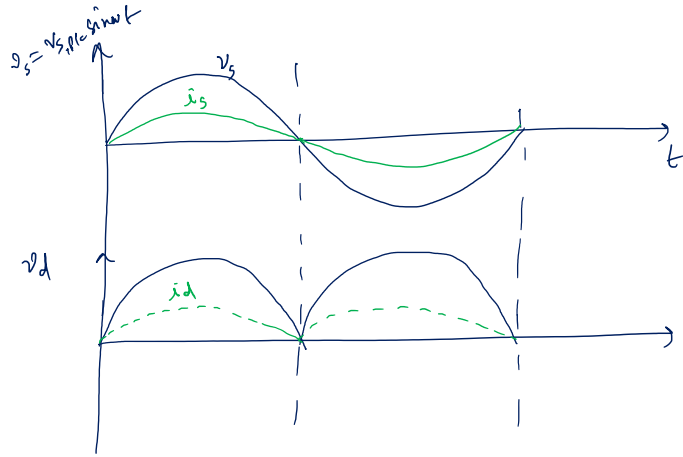

$$v_d = |v_s(t)|$$

$$v_d = |v_{s,rms} \sin \omega t|$$

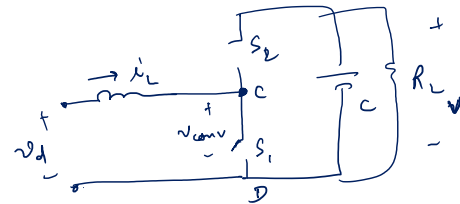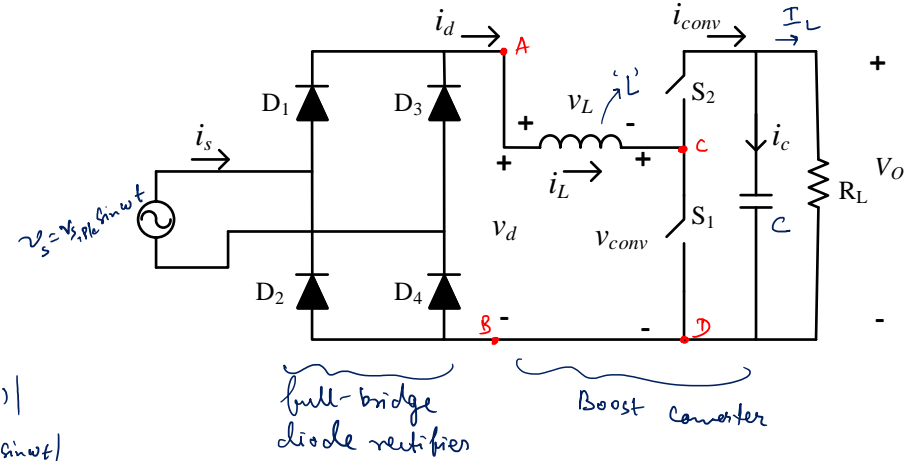


full-bridge
diode rectifier

Boost converter

Boost PFC

Consideration

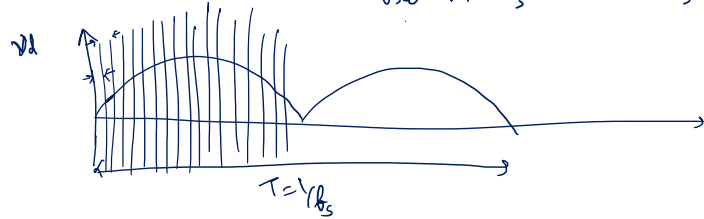
The switching freq. of S_1, S_2 switches \gg the supply frequency
 $f_{sw} \gg f_s \Rightarrow T_s \ll T$




$$(T_s = 1/f_{sw}) \quad v_s = V_s \sin \omega t$$


\Rightarrow the $v_d = |v_s(t)|$ is nearly constant during one switching period

Let us take, ' D ' is the duty ratio of switch ' S_1 ' at one of the switching period
 $|v_s| \rightarrow$ is the v_d voltage at one of the switching period

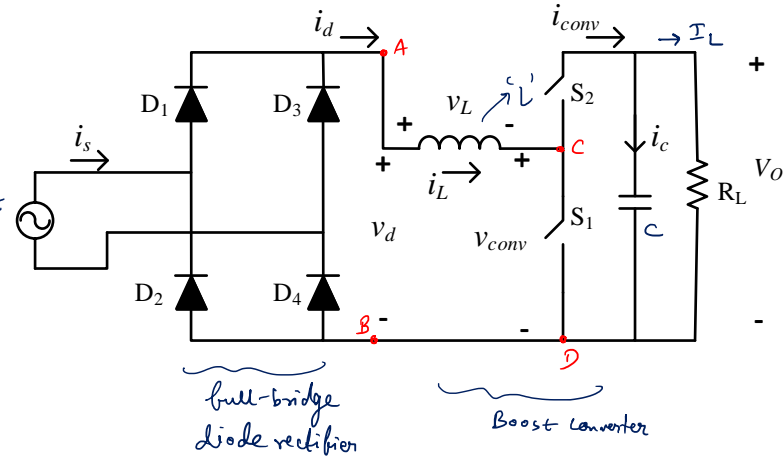

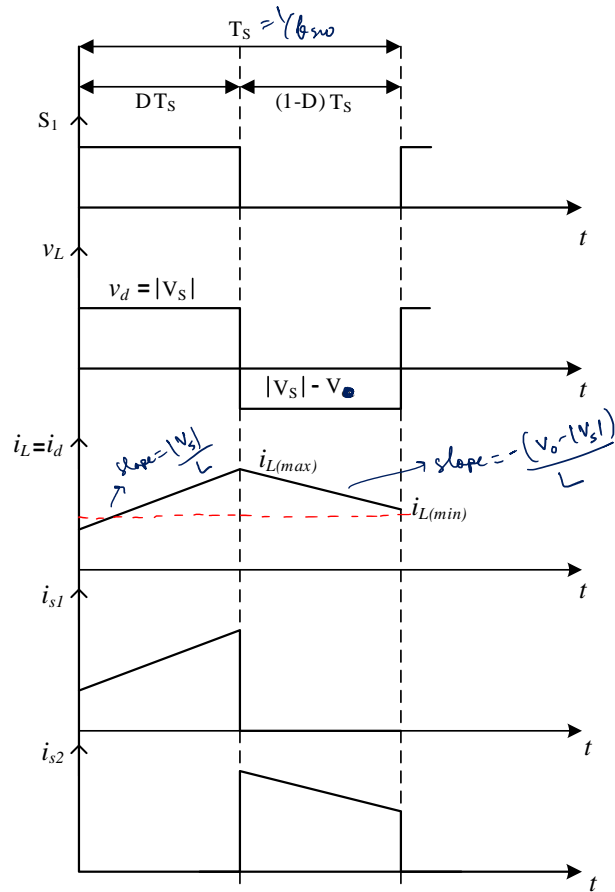


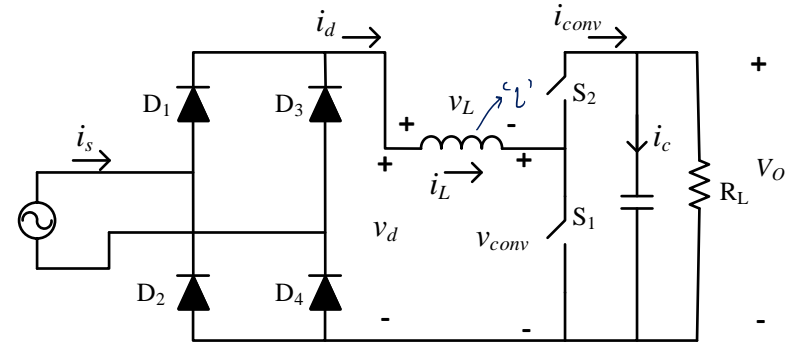During $\mathcal{D}T_s \rightarrow S_1$ conducts current in 1 direction, S_2 blocks voltage of one polarity $\rightarrow V_{s2} = -V_o$




in the half cycle, D_1 & D_4 are forward biased


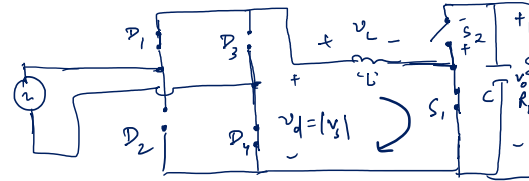
During $\mathcal{D}T_s$, S_1 is ON $\rightarrow S_2$ is off $\rightarrow V_{s2} = -V_o$




$$v_L = L \frac{di}{dt} \Rightarrow \frac{di}{dt} = \frac{|V_s|}{L}$$

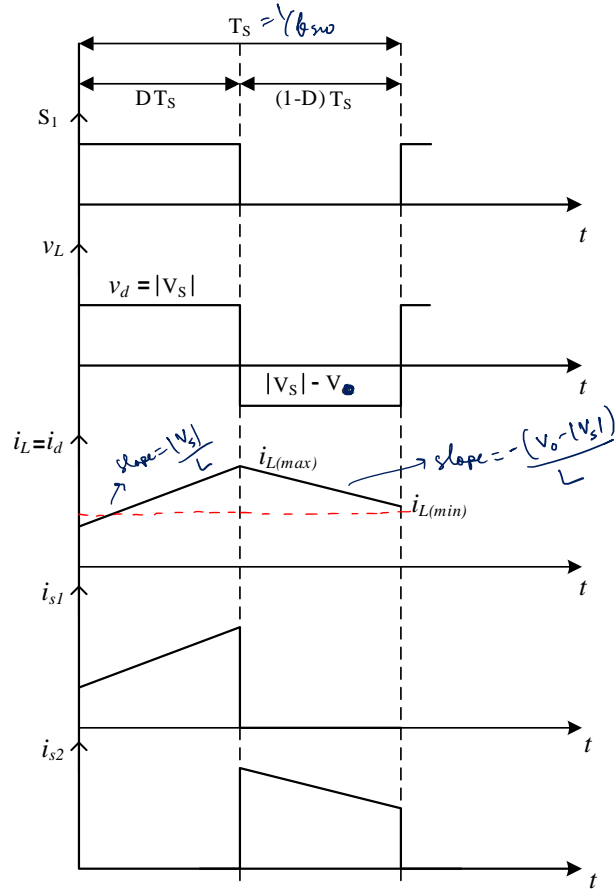

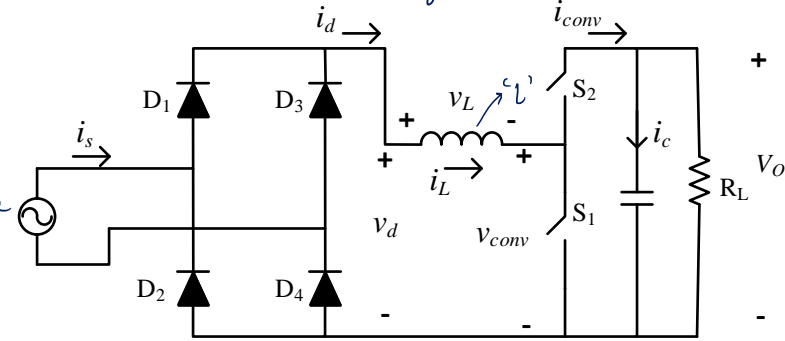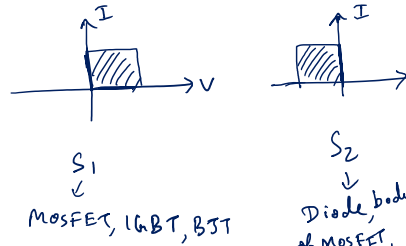During $DT_s \rightarrow S_1$ conducts current in 1 direction, S_2 blocks voltage of one polarity $\rightarrow V_{s2} = -V_o$
 During $(1-D)T_s \rightarrow S_2$ conducts current in 1 direction, S_1 blocks voltage of one polarity $\rightarrow V_{s1} = V_o$



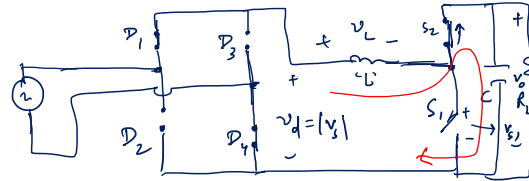in the half cycle, D_1 & D_4 are forward biased
 During $(1-D)T_s$, S_2 is ON $\rightarrow S_1$ is off $\rightarrow V_{s1} = V_o$



$$V_L = |V_s| - V_o$$

$$V_o > |V_s| \Rightarrow V_L \text{ is -ve} \Rightarrow \frac{di}{dt} = \frac{|V_s| - V_o}{L}$$



Thank You

