



IIT ROORKEE



NPTEL ONLINE  
CERTIFICATION COURSE

# Charging Infrastructure


## Lecture-32

### Revisiting Isolated DC-DC Converters-III


Dr. Apurv Kumar Yadav  
Department of Electrical Engineering



# Recap

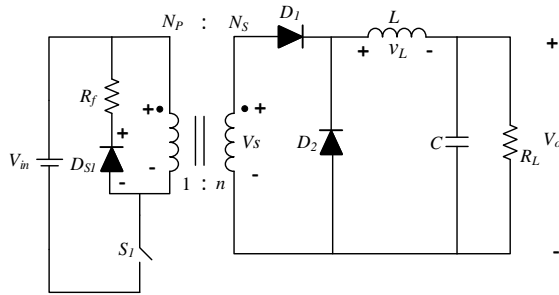

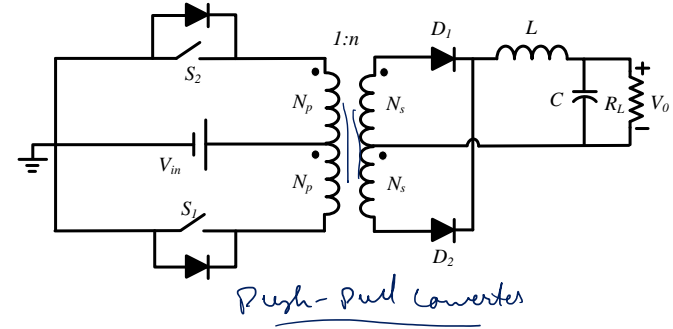- forward converter with demagnetizing winding
- dual switch forward converter
- 0 to  $B_{max}$



-  $B_{max}$  to +  $B_{max}$

→ Area of core gets reduced by half

# Full-bridge based isolated DC-DC converter

$$\frac{N_s}{N_p} = n$$

$$\frac{DT_s}{2} \text{ period,}$$

$$v_L = nV_{in} - v_o$$

$$\frac{(1-D)T_s}{2} \text{ period,}$$

$$v_L = -v_o$$

$$\frac{DT_s}{2} \text{ period}$$


$$v_L = nV_{in} - v_o$$

$$\frac{(1-D)T_s}{2} \text{ period}$$

$$v_L = -v_o$$


$$\Rightarrow (nV_{in} - v_o) \frac{DT_s}{2} + (-v_o) \frac{(1-D)T_s}{2} = 0$$

$$\Rightarrow v_o = nV_{in}D$$

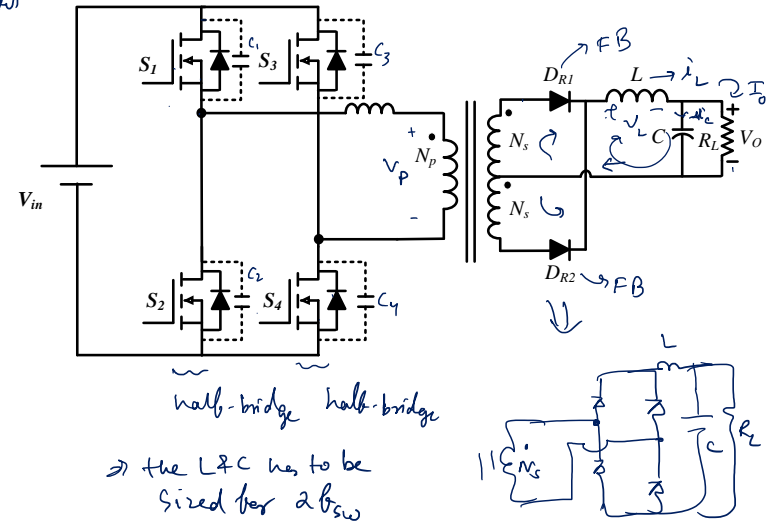

half-bridge half-bridge

the L & C has to be sized for  $2f_{sw}$

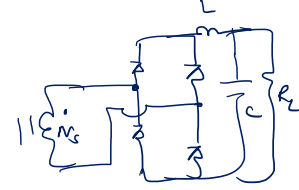

Sizing of  $C$

$$C \cdot \Delta V_o = \Delta Q = \frac{1}{2} \times \frac{\Delta I_L}{2} \times \frac{T_s}{4}$$

$$\Rightarrow C_{\text{cri}} = \frac{\Delta I_L}{8(2f_{sw}) \cdot \Delta V_o}$$

$$f_{sw} = \frac{1}{T_s}$$

$$C > C_{\text{cri}}$$

$\Delta V_o \rightarrow$  specification  
 $f_{sw} \rightarrow$  designer choice  
 $\Delta I_L \rightarrow$  5 to 10% of  $I_o$

Sizing of  $L$

$$|-v_o| = \frac{L \Delta i_L}{\left(\frac{(1-D)T_s}{2}\right)}$$

$$\left(\frac{(1-D)T_s}{2}\right) \rightarrow v_L = -v_o$$

$$\Rightarrow L = \frac{v_o(1-D)}{2f_{sw} \Delta i_L}$$


$$\Rightarrow L = \frac{nV_{in}D(1-D)}{2f_{sw} \Delta i_L}$$


designer choice

designer choice

specification depends on output voltage & 'n'

5 to 10% of  $I_o$

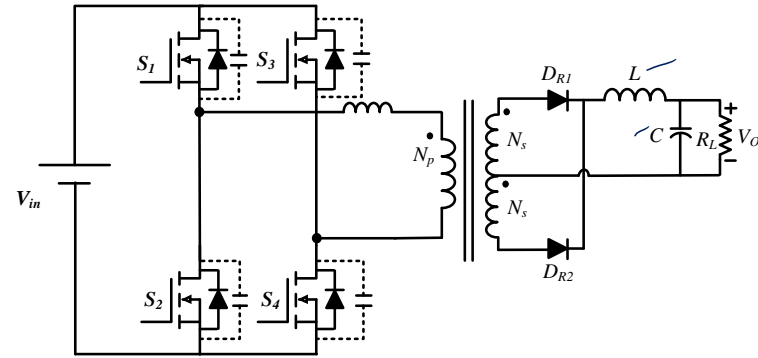

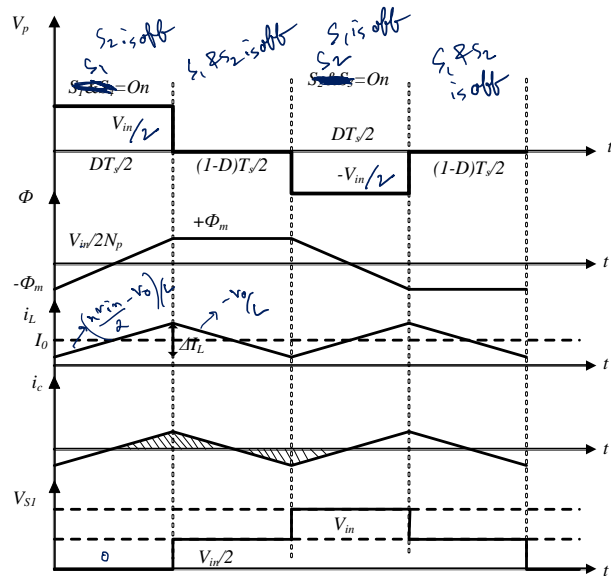

## half-bridge converter

$$\frac{N_s}{N_p} = n$$

$\frac{DT_s}{2}$  period

$$v_p = v_{in} - \frac{v_{in}}{2}$$

$$v_p = \frac{v_{in}}{2}$$

$$v_L = \frac{n v_{in}}{2} - v_o$$


$\frac{(1-D)T_s}{2}$  period

$$v_L = -v_o$$

volt-sec balance on  $v_L$

$$\Rightarrow v_o = \frac{n v_{in} D}{2}$$
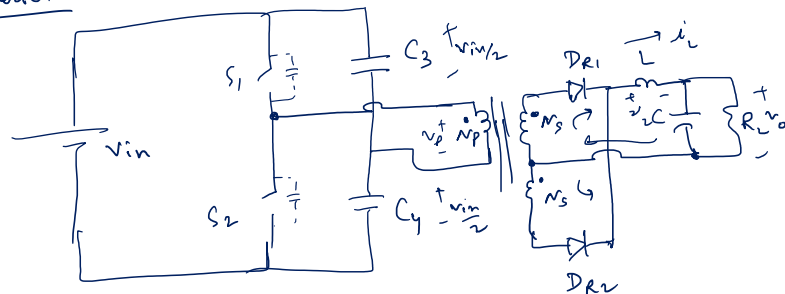
$$\left(\frac{n v_{in}}{2} - v_o\right) \frac{DT_s}{2} + (-v_o) \frac{(1-D)T_s}{2} = 0$$



# Thank You

