



IIT ROORKEE



NPTEL ONLINE
CERTIFICATION COURSE

Charging Infrastructure

Lecture-23

Three-phase AC-DC Converter-I

Dr. Apurv Kumar Yadav
Department of Electrical Engineering



Recap

- Single-phase AC-DC Converter
- Concept of PWM

7 kw
└─┐ OBC
└─┐ 1-φ ⇒ 1-φ AC-DC


$$\Rightarrow V_{Ao(\omega)}(t) = \frac{mV_m}{2} \sin \omega t$$

$$\left(m = \frac{V_m}{V_c} \right) \Rightarrow V_m < V_c$$

Three-phase AC-DC Converter

↳ front-end AC-DC Converter (FEC)

↳ Active Rectifier

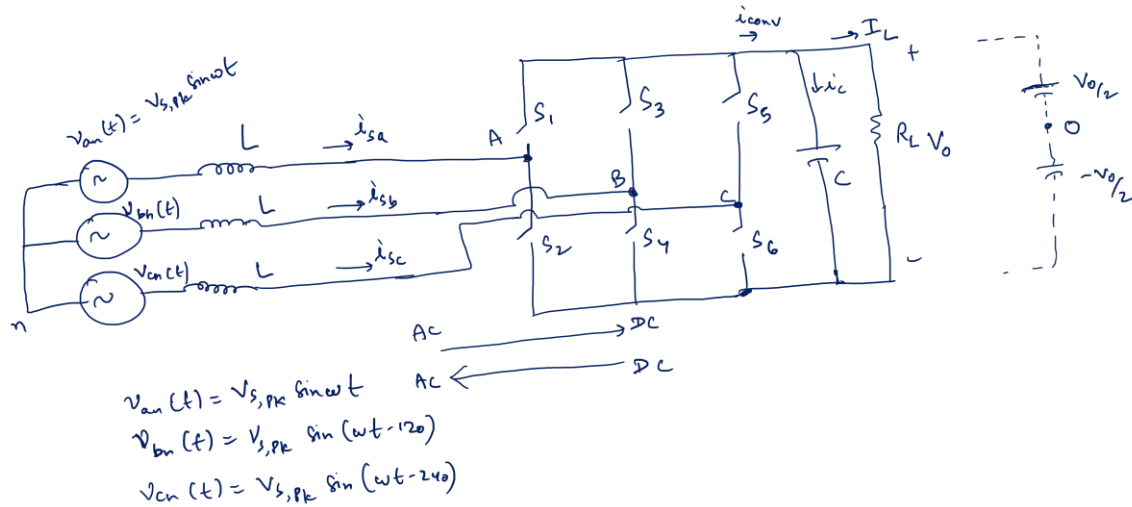


for fundamental frequency

$$f_m = f_s = 50 \text{ Hz}$$

$$\omega = 2\pi f_s$$

$$\begin{aligned} v_s(t) &= V_{s, \text{pk}} \sin \omega t \\ i_s(t) &= I_{s, \text{pk}} \sin \omega t \\ v_{\text{con}}(t) &= \frac{m V_o}{2} \sin \omega t \end{aligned}$$

$$\left(m = \frac{V_m}{V_c} \right)$$

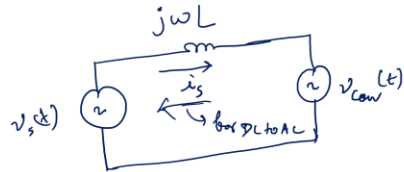

$$v_s(t) = v_{\text{con}}(t) + j\omega L i_s, \text{ using KVL}$$

$$\Rightarrow v_{\text{con}}(t) = v_s(t) - j\omega L i_s$$

in phasor form,

$$\vec{V}_{\text{con}} = \vec{V}_s - j\omega L \vec{I}_s$$


for reverse power flow (from DC to AC)

\Rightarrow Converter to source

in phasor form,

$$\vec{V}_{\text{con}} = \vec{V}_s + j\omega L \vec{I}_s$$

To have the unity power factor operation

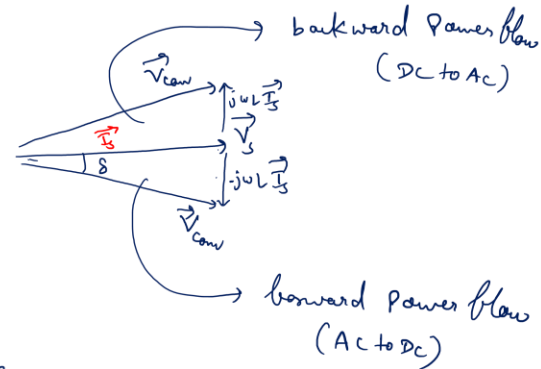


\Rightarrow boost-end converter because the power flow can be made bidirectional

$$\begin{pmatrix} |\vec{V}_s| = V_{s, \text{pk}} \\ |\vec{I}_s| = I_{s, \text{pk}} \\ |\vec{V}_{\text{con}}| = \frac{m V_o}{2} \end{pmatrix}$$

- By changing, the sign of ' δ ' → we can change the direction of power flow
- By changing the value of ' δ ' → we can change the amplitude of phasor corresponds to voltage drop across inductor ⇒ the magnitude of current.

Calculation of inductor ' L '

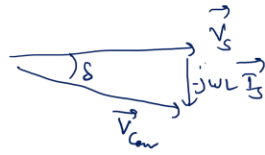

$$\begin{aligned}
 \Rightarrow |\vec{V}_{Lc}| &= \sqrt{(-j\omega L \vec{I}_s)^2 + |\vec{V}_s|^2} \\
 &= \sqrt{\omega^2 L^2 |\vec{I}_s|^2 + |\vec{V}_s|^2} \\
 &= \sqrt{\omega^2 L^2 (I_{s, rlc})^2 + V_{s, rlc}^2} \\
 \frac{mV_o}{2} &= \sqrt{\omega^2 L^2 (I_{s, rlc})^2 + V_{s, rlc}^2} \\
 \Rightarrow L^2 &= \frac{\left(\frac{mV_o}{2}\right)^2 - V_{s, rlc}^2}{\omega^2 I_{s, rlc}^2}
 \end{aligned}$$

⇒

$$L = \sqrt{\frac{\left(\frac{mV_o}{2}\right)^2 - V_{s,plc}^2}{(2\pi f_s I_{s,plc})^2}}$$

⇒ m = modulation index $\rightarrow 0.8$ to 0.9

$$f_s = f_m = 50 \text{ Hz}$$

$I_{s,plc}$ = peak of the phase current \rightarrow from specification

V_o = DC-link voltage

$V_{s,plc}$ = peak of the phase voltage

} from specification

⇒ the voltage drop across inductor must be within 10% of the supply voltage.
 (for fundamental frequency) \rightarrow ensured
 this has to be

$$\text{Rms current of this inductor} = \frac{I_{s,plc}}{\sqrt{2}} \left[= \sqrt{\frac{1}{T} \int_0^T (I_{s,plc} \sin t)^2 dt} \right]$$

Thank You

