



IIT ROORKEE



NPTEL ONLINE  
CERTIFICATION COURSE

# Charging Infrastructure

## Lecture-30


### Revisiting Isolated DC-DC Converters-I

Dr. Apurv Kumar Yadav  
Department of Electrical Engineering


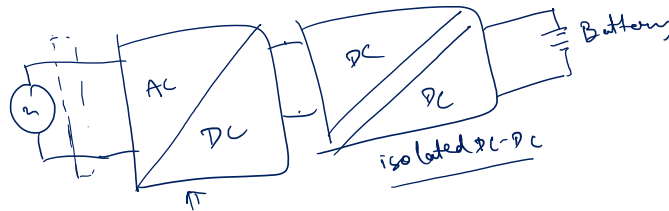
# Recap

- Single-phase AC-DC Converter: operation, Design, small signal model, closed loop control, CCM, DCM operation.
- Three-phase AC-DC Converter: operation, Design, small signal model, closed loop control.



# Isolated DC-DC Converter

- ① Forward converter
- ② Flyback converter
- ③ Push-Pull converter
- ④ half-bridge converter
- ⑤ full-bridge converter  $\rightarrow$  Phase-shift full bridge converter (PSFB)
- ⑥ Dual active bridge converter  $\rightarrow$  Resonant based DAB, multilevel DAB
- ⑦ Resonant based converter  $\rightarrow$  LLC, or CLLC based converters

$\rightarrow$  All have transformers for isolation, which is supplied by high frequency AC voltages



$$V = N \frac{d\phi}{dt}$$


$$\Rightarrow V = N \Delta \phi f$$

$$\Rightarrow V = N \Delta B \cdot A_c f$$

$\downarrow$   
flux density
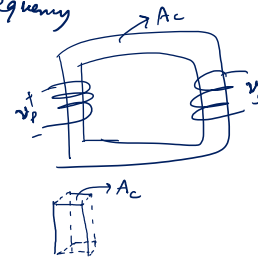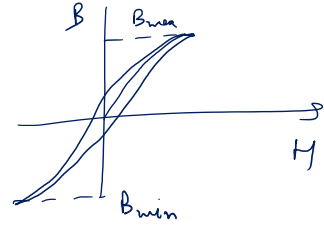
$$A_c \propto \frac{1}{f} \Rightarrow f \uparrow, A_c \downarrow$$



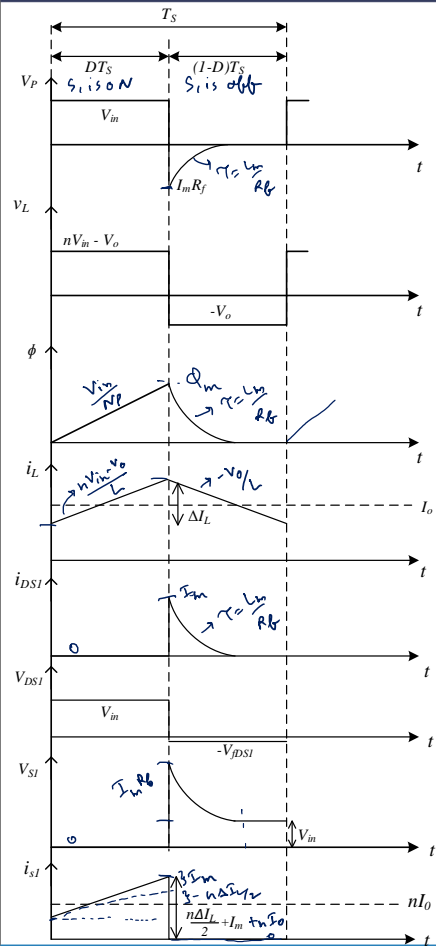


Forward Converter (Buck derived topology)

$$\frac{V_L}{V_p} = \frac{N_s}{N_p} = n$$

$$\Rightarrow V_s = nV_{in}$$

$$V_L = nV_{in} - V_o$$

during  $(1-D)T_s$

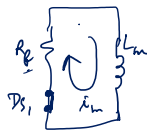


$$V_L = -V_o$$

volt-sec balance of  $L$

$$(nV_{in} - V_o)DT_s + (-V_o)(1-D)T_s = 0$$
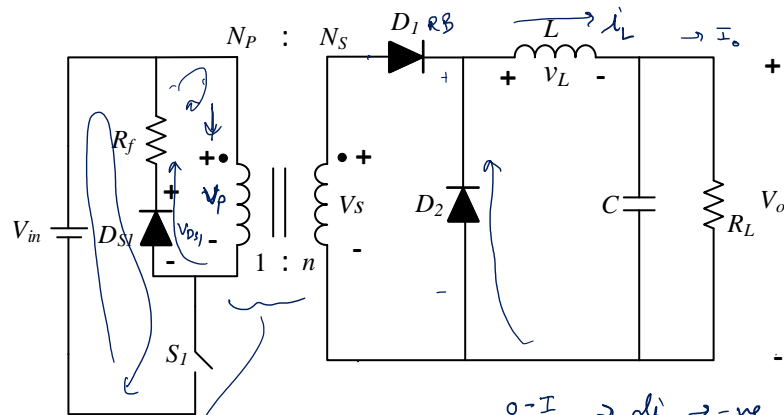
$$\Rightarrow V_o = nV_{in} \cdot D \quad (D \approx 0 \text{ to } 1)$$




$$V_{S1} = I_m R_B + V_{in}$$





$$\frac{0 - I}{\Delta t} \Rightarrow \frac{di}{dt} \rightarrow -ve \Rightarrow -L \frac{di}{dt}$$

$$T_s = 1/f_{sw}$$

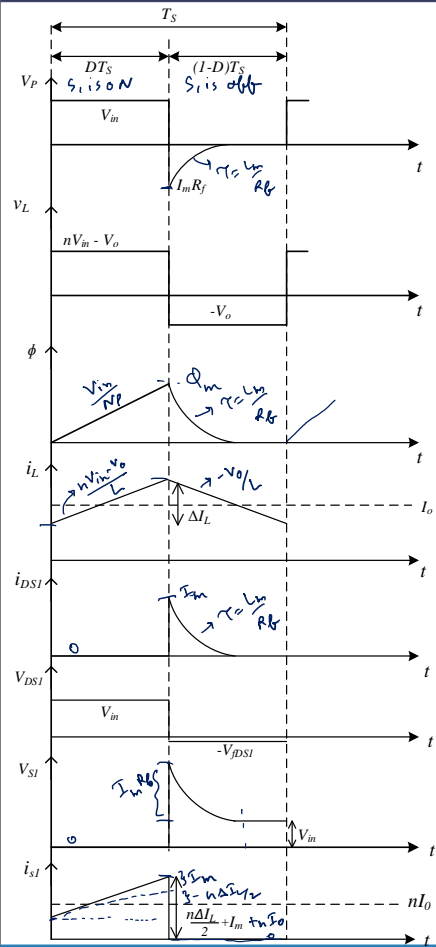
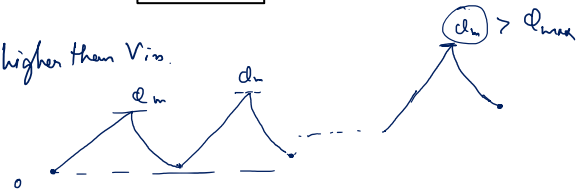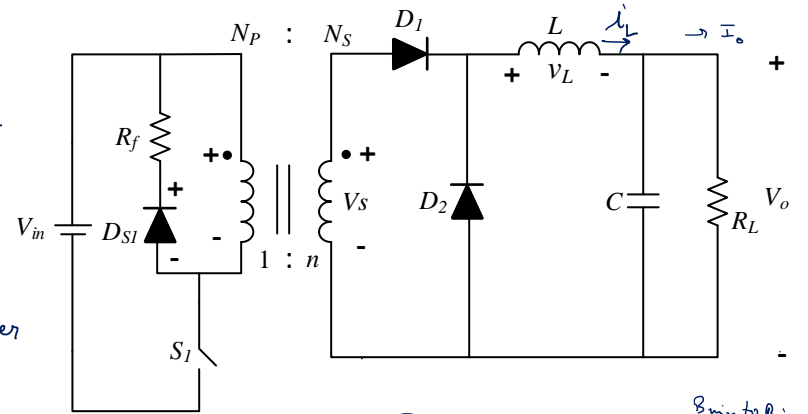
### Disadvantage

- ① Sufficient  $(1-D)T_s \rightarrow$  limits the switching freq. as flux in the transformer core must get reset to 0.
- ② The reverse recovery losses of the diode
- ③ Long reset of the flux in the transformer
- ④ Core utilization is limited  $\approx$  half
- ⑤ The switch ' $S_1$ ' voltage rating is higher than  $V_{in}$ .



$V = N \Delta B \cdot A \cdot f$   
 $\rightarrow B_{in} \text{ to } B_{max}$   
 $\rightarrow D \text{ to } B_{max}$   
 $\rightarrow$  larger core area is required

# Thank You

