



IIT ROORKEE



NPTEL ONLINE
CERTIFICATION COURSE

Charging Infrastructure


Lecture-25

Three-phase AC-DC Converter-III

Dr. Apurv Kumar Yadav
Department of Electrical Engineering



Recap

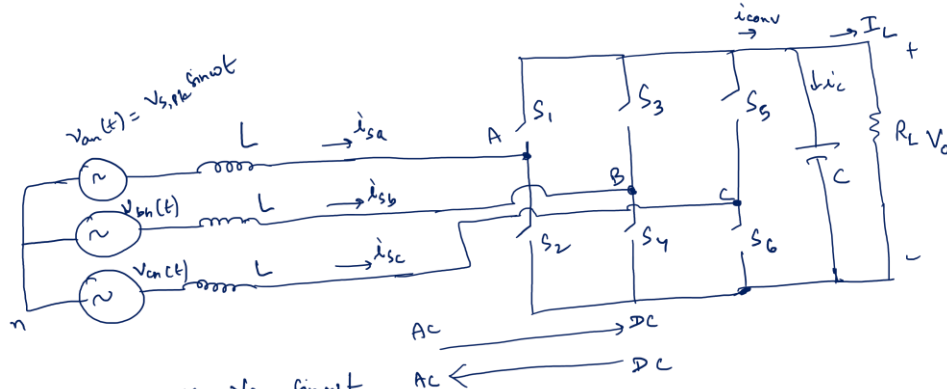

$$\begin{aligned} V_{an}(t) &= V_{s,PK} \sin \omega t \\ V_{bn}(t) &= V_{s,PK} \sin (\omega t - 120^\circ) \\ V_{cn}(t) &= V_{s,PK} \sin (\omega t - 240^\circ) \end{aligned}$$

$$\Rightarrow (\omega L \cdot I_{s,PK}) < 10\% \text{ of } V_{s,PK}$$

↑ required

$$L = \sqrt{\frac{\left(\frac{m V_o}{2}\right)^2 - V_{s,PK}^2}{(2\pi f_s \cdot I_{s,PK})^2}}$$

⇒ the voltage drop across inductor (corresponding to fundamental) must be less than 10% of the $V_{s,PK}$

FEC


⇒ m-modulation index \rightarrow designer's choice (0.8 to 0.9)

$V_{s,PK} \rightarrow$ specification

$V_o \rightarrow$ specification

$f_s \rightarrow$ line frequency given in specification
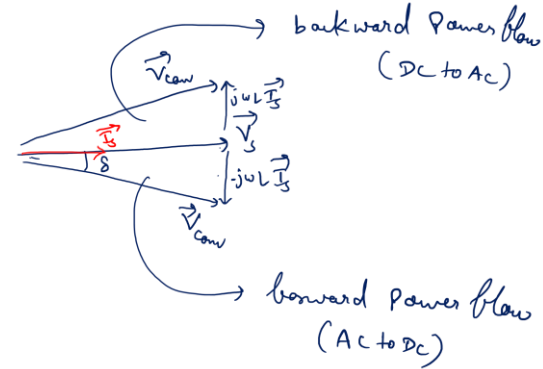
$$I_{s,PK} \rightarrow \frac{P_L \times \sqrt{2}}{3V_{ph,ms}} \leftarrow \text{assuming no loss in the power converter}$$



Recap


Sizing of Capacitance

⇒ The output power (at XY terminal)

$$= V_o \cdot i_{conv}$$

Input power = $V_{s, pk} \sin \omega t \cdot I_{s, pk} \sin \omega t$
 $+ V_{s, pk} \sin(\omega t - 120^\circ) \cdot I_{s, pk} \sin(\omega t - 120^\circ)$
 $+ V_{s, pk} \sin(\omega t - 240^\circ) \cdot I_{s, pk} \sin(\omega t - 240^\circ)$

→ assuming vfb operation

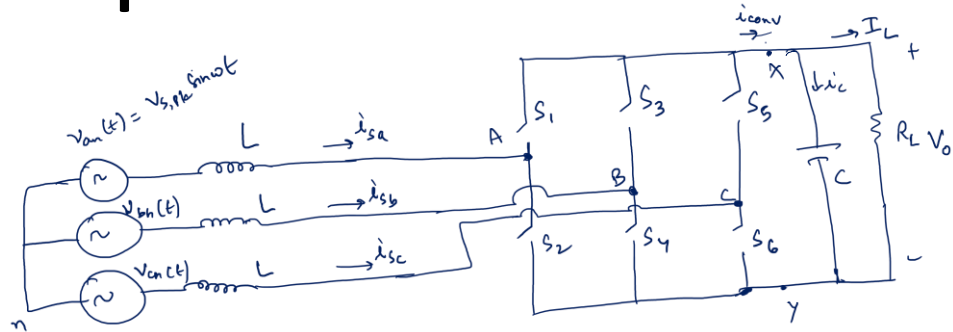

If there is loss-less converter

Apply power balance

⇒ Input power = Output power

$$\Rightarrow V_o \cdot i_{conv} = V_{s, pk} \sin \omega t \cdot I_{s, pk} \sin \omega t + V_{s, pk} \sin(\omega t - 120^\circ) \cdot I_{s, pk} \sin(\omega t - 120^\circ) + V_{s, pk} \sin(\omega t - 240^\circ) \cdot I_{s, pk} \sin(\omega t - 240^\circ)$$

$$= V_{s, pk} I_{s, pk} (\sin^2 \omega t + \sin^2(\omega t - 120^\circ) + \sin^2(\omega t - 240^\circ))$$

$$= V_{s, pk} I_{s, pk} \left(\frac{1 - \cos 2\omega t}{2} + \frac{1 - \cos(2\omega t - 240^\circ)}{2} + \frac{1 - \cos(2\omega t - 480^\circ)}{2} \right)$$


$$= V_{s, pk} I_{s, pk} \left(\frac{3}{2} - \underbrace{(\cos 2\omega t + \cos(2\omega t - 240^\circ) + \cos(2\omega t - 480^\circ))}_{= 0} \right)$$

Recap

$$\Rightarrow V_o, i_{con} = \frac{3}{2} V_{s,pk} \cdot I_{s,pk}$$

$$\Rightarrow i_{con} = \frac{3}{2V_o} V_{s,pk} \cdot I_{s,pk} \longrightarrow \text{there is absence of 2nd line freq. component (only DC-component exist)}$$


fundamental frequency

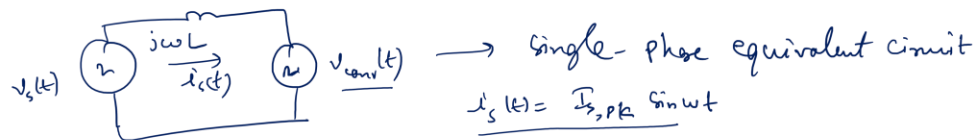

$v_{con}(t) \rightarrow$ fundamental component along with harmonics frequency component at side band of $\omega_f (\omega_f = \frac{\omega_c}{f_m}) \approx$ carrier frequency ($i_{mf \pm j}$)

harmonic frequency component

The single phase equivalent circuit

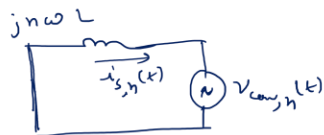




$$\Rightarrow i_{s,n}(t) = \frac{v_{con,n}(t)}{jn\omega L}$$

$$n = i_{mf \pm j}$$

$$\omega = 2\pi f_m$$

$$f_m = f_s$$

$$\omega = 2\pi f_s$$

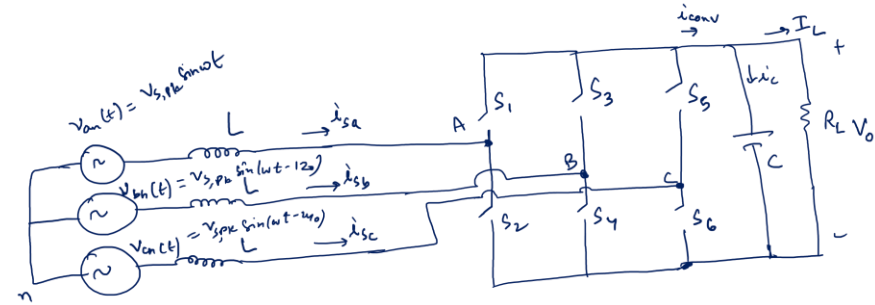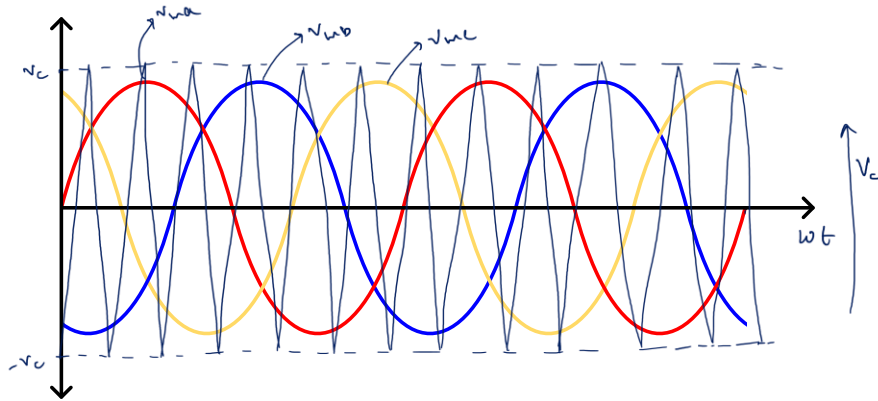
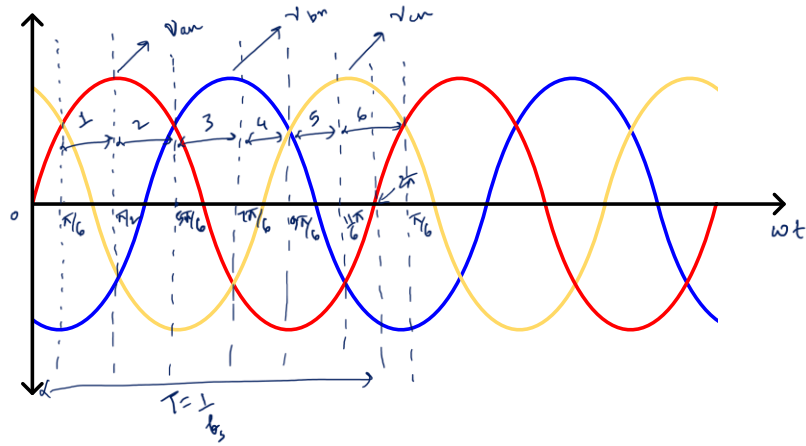


$$v_{la} = V_m \sin \omega t$$

$$v_{lb} = V_m \sin(\omega t - 120^\circ)$$

$$v_{lc} = V_m \sin(\omega t - 240^\circ)$$

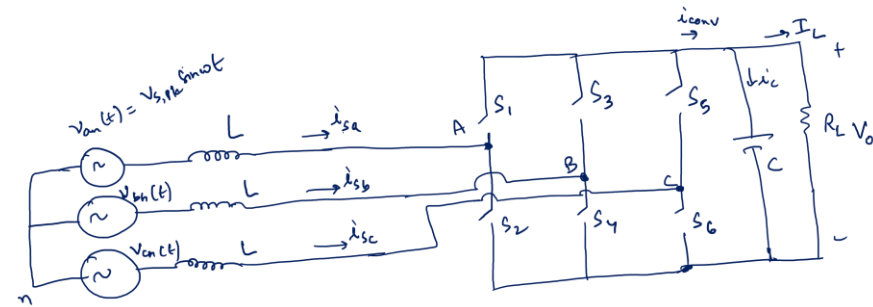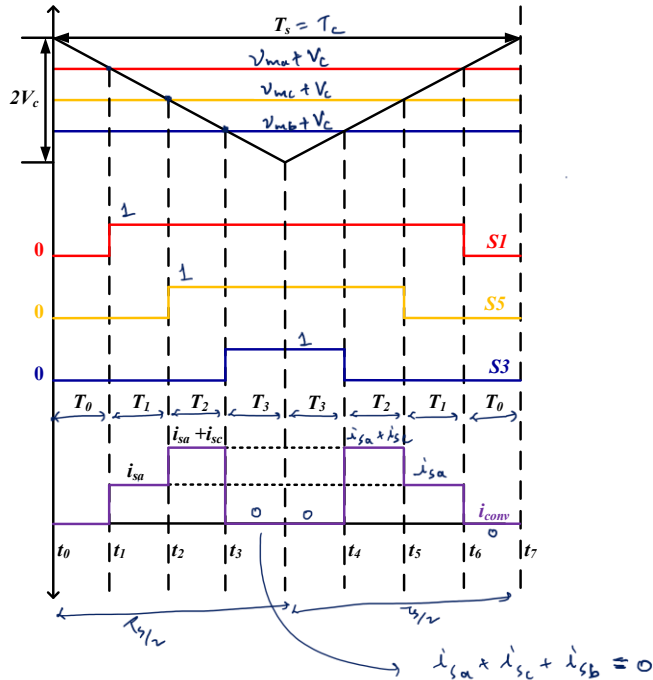→ operating mode - 1
 $T_c = 1/f_c \approx T_s = 1/f_{sw}$



if modulating wave > carrier

Top switch is ON
 Bottom switch is OFF

else

Bottom switch is ON
 Top switch is OFF

Assumption, balance 3-phase operation

$$i_{sa} + i_{sb} + i_{sc} = 0$$

$$T_1 = \frac{T_s}{2} \left(\frac{(v_{ma} + v_c) - (v_{mc} + v_c)}{2v_c} \right)$$

$$T_1 = \frac{T_s}{4} \left(\frac{v_{ma} - v_{mc}}{v_c} \right) \longrightarrow (1)$$

$$T_2 = \frac{T_s}{2} \left(\frac{(v_{me} + v_c) - (v_{mb} + v_c)}{2v_c} \right)$$

$$T_2 = \frac{T_s}{4} \left(\frac{v_{me} - v_{mb}}{v_c} \right) \longrightarrow (2)$$

$$T_3 = \frac{T_s}{2} \left(\frac{v_{mb} + v_c}{2v_c} \right)$$

$$\Rightarrow T_3 = \frac{T_s}{4} \left(1 + \frac{v_{mb}}{v_c} \right) \longrightarrow (3)$$

$$\begin{aligned} \Rightarrow T_0 &= \frac{T_s}{2} - (T_1 + T_2 + T_3) \\ &= \frac{T_s}{2} - \frac{T_s}{4} \left(\frac{v_{ma} - v_{mc} + v_{me} - v_{mb} + v_c + v_{mb}}{v_c} \right) \\ &= \frac{T_s}{2} \left[1 - \left(\frac{v_{ma} + v_c}{2v_c} \right) \right] \end{aligned}$$

$$\Rightarrow T_0 = T_s \left[\frac{2V_c - v_{ma} - V_c}{2V_c} \right]$$

$$T_0 = \frac{T_s}{4} \left[1 - \frac{v_{ma}}{V_c} \right] \longrightarrow (4)$$

$$T_1 = \frac{T_s}{4} \left[\frac{V_m \sin \omega t}{V_c} - \frac{V_m \sin(\omega t + 2\pi/3)}{V_c} \right]$$

$$T_1 = \frac{T_s}{4} \left(m \sin \omega t - m \sin(\omega t + 2\pi/3) \right) \longrightarrow (5)$$

$$T_2 = \frac{T_s}{4} \left[\frac{V_m \sin(\omega t + 2\pi/3)}{V_c} - \frac{V_m \sin(\omega t - 2\pi/3)}{V_c} \right]$$

$$T_2 = \frac{T_s}{4} \left(m \sin(\omega t + 2\pi/3) - m \sin(\omega t - 2\pi/3) \right) \longrightarrow (6)$$

$$T_1 = \frac{\sqrt{3}}{4} T_s m \sin(\omega t - \pi/6) \longrightarrow (7)$$

$$T_2 = \frac{\sqrt{3}}{4} T_s m \cos \omega t \longrightarrow (8)$$

$$\begin{aligned} v_{ma} &= V_m \sin \omega t \\ v_{mb} &= V_m \sin(\omega t - 120^\circ) \quad ; \quad m = \frac{V_m}{V_c} \\ v_{mc} &= V_m \sin(\omega t - 240^\circ) \end{aligned}$$

$$i_{conv,avg,T_s} = \frac{1}{T_s} \left[\int_0^{T_s} i_{conv} \cdot dt \right]$$

$$= 2 \times \frac{1}{T_s} \left[\int_{t_1}^{t_2} i_{sa} \cdot dt + \int_{t_2}^{t_3} (i_{sa} + i_{sc}) \cdot dt + 0 \right]$$

$$= \frac{2}{T_s} \left[i_{sa} (t_2 - t_1) + (-i_{sb}) \cdot (t_3 - t_2) \right]$$

$$i_{conv,avg,T_s} = \frac{2}{T_s} \left[i_{sa} T_1 - i_{sb} T_2 \right] \longrightarrow \textcircled{9}$$

$$i_{conv,avg,T_s}^2 = \frac{1}{T_s} \left[\int_0^{T_s} i_{conv}^2 \cdot dt \right]$$

$$= 2 \times \frac{1}{T_s} \left[\int_{t_1}^{t_2} i_{sa}^2 \cdot dt + \int_{t_2}^{t_3} (i_{sa} + i_{sc})^2 \cdot dt + 0 \right]$$


[the factor '2' comes from symmetry around $\frac{T_s}{2}$]

$$i_{sa} + i_{sb} + i_{sc} = 0$$

$$\Rightarrow i_{sa} + i_{sc} = -i_{sb}$$

$$T_s \gg T$$

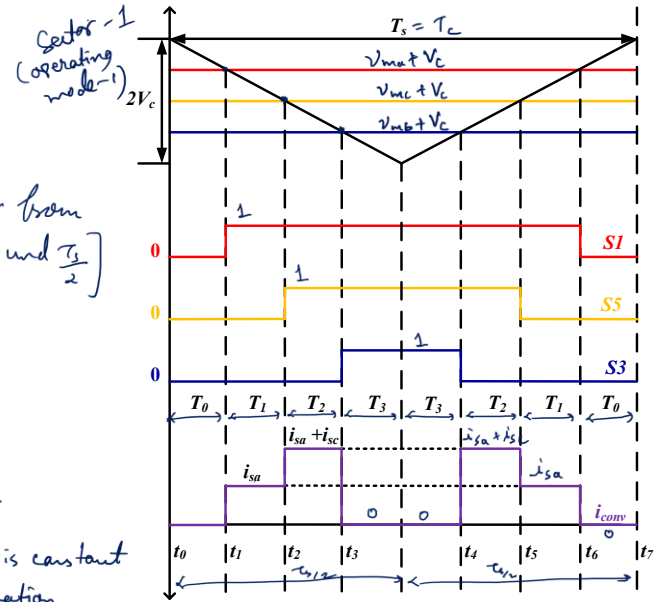$\Rightarrow i_{sa}, i_{sc}, i_{sb}$ is constant in T_s duration



$$i_{\text{com}, \text{rms}}^2 = \frac{2}{T_s} \left[i_{sa}^2 \cdot T_1 + (i_{sa} + i_{sc})^2 T_2 \right]$$

$$i_{\text{com}, \text{rms}}^2 = \frac{2}{T_s} \left[i_{sa}^2 T_1 + i_{sb}^2 T_2 \right] \longrightarrow (10)$$

$$i_{\text{com}, \text{avg}} = \frac{3}{\pi} \left[\int_{\pi/6}^{\pi/2} i_{\text{com}, \text{avg}, T_s} \cdot d(\omega t) \right]$$

$$= \frac{3}{\pi} \left[\int_{\pi/6}^{\pi/2} \frac{2}{T_s} (i_{sa} T_1 - i_{sb} T_2) \cdot d(\omega t) \right] \quad (\text{from } \textcircled{10})$$

$$i_{\text{com}, \text{avg}} = \frac{3}{\pi} \times \frac{2}{T_s} \left[\int_{\pi/6}^{\pi/2} I_{s, \text{pk}} \sin \omega t \left(\frac{\sqrt{3}}{4} T_s m \cdot \sin(\omega t - \pi/6) \right) \cdot d(\omega t) \right. \\ \left. - \int_{\pi/6}^{\pi/2} I_{s, \text{pk}} \sin(\omega t - 2\pi/3) \cdot \frac{\sqrt{3}}{4} T_s m \cos \omega t \cdot d(\omega t) \right]$$

$$i_{\text{com}, \text{avg}} = \frac{3}{4} I_{s, \text{pk}} m \longrightarrow (11)$$

over the line cycle

$$\left. \begin{aligned} i_{sa} &= I_{s, \text{pk}} \sin \omega t \\ i_{sb} &= I_{s, \text{pk}} \sin(\omega t - 2\pi/3) \\ i_{sc} &= I_{s, \text{pk}} \sin(\omega t - 4\pi/3) \end{aligned} \right\} \text{assuming upf operation}$$

from (10)

$$i_{\text{con,avg}} = \sqrt{\frac{3}{\pi} \left[\int_{\pi/6}^{\pi/2} (i_{\text{con,m}})_{T_1}^2 \cdot d(\omega t) \right]}$$

$$= \sqrt{\frac{3}{\pi} \left[\int_{\pi/6}^{\pi/2} (i_{s_a}^2 T_1 + i_{s_b}^2 T_2) \cdot d(\omega t) \right]}$$

(T_1, T_2 from (7) & (8))

$$i_{\text{con,avg}} = I_{s,\text{pk}} \sqrt{\frac{\sqrt{3} \cdot m \cdot 5}{\pi} \frac{1}{4}} \rightarrow (12)$$

over the line cycle

$$i_{\text{c,ms}} = \sqrt{i_{\text{con,ms}}^2 - i_{\text{con,avg}}^2}$$

$$i_{\text{c,ms}} = \sqrt{I_{s,\text{pk}}^2 \left(\frac{\sqrt{3}}{\pi} m \frac{5}{4} \right) - \frac{9}{16} m^2 I_{s,\text{pk}}^2}$$

$$i_{\text{c,ms}} = I_{s,\text{pk}} \sqrt{\left(\frac{\sqrt{3}}{\pi} m \frac{5}{4} \right) - \frac{9}{16} m^2}$$

$i_{\text{con,avg}} \rightarrow$ going through the load (R_L)

$$I_{s,\text{pk}} = \frac{\sqrt{2} P_L}{3 V_{\text{ph,ms}}} \quad \begin{matrix} \text{converter is} \\ \text{(class B)} \end{matrix}$$

Calculation of Capacitance value

Minimum DC-link Capacitor

$$C_{min} \geq \frac{\Delta P_{max} T_d}{2 V_o \cdot \Delta V_o}$$

specification
designer's choice
specification

where $\Delta P_{max} \rightarrow$ maximum power variation of the converter

$T_d \rightarrow$ response time of closed loop

$\Delta V_o \rightarrow$ the permissible voltage ripple

$V_o \rightarrow$ output voltage


$$\Rightarrow \frac{1}{2} C_{min} V_1^2 - \frac{1}{2} C_{min} V_2^2 \geq \frac{\Delta P_{max} T_d}{2}$$

$$\Rightarrow C_{min} (V_1^2 - V_2^2) \geq \Delta P_{max} T_d$$

$$\Rightarrow C_{min} (V_1 + V_2) (V_1 - V_2) \geq \Delta P_{max} T_d$$

$$\Rightarrow C_{min} 2 V_o \cdot \Delta V_o \geq \Delta P_{max} T_d$$
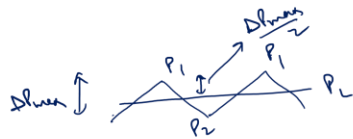
$$\Rightarrow C_{min} \geq \frac{\Delta P_{max} \cdot T_d}{2 V_o \Delta V_o}$$



$$\frac{V_1 + V_2}{2} = V_o$$

$$\Rightarrow V_1 - V_2 = \Delta V_o$$

The voltage rating of capacitor $> V_o + \frac{\Delta V_o}{2}$

Thank You

