



IIT ROORKEE



NPTEL ONLINE
CERTIFICATION COURSE

Charging Infrastructure

Lecture-29

Closed loop control of three-phase AC-DC converter-IV

Dr. Apurv Kumar Yadav


Department of Electrical Engineering




Recap

Control objectives

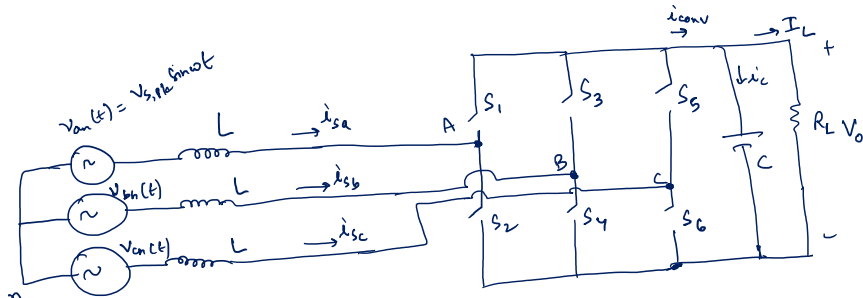- ① To regulate the output voltage to a desired value. ($> \sqrt{2} V_{L-L}$)
- ② The current drawn should have unity power factor (upf) operation



Recap

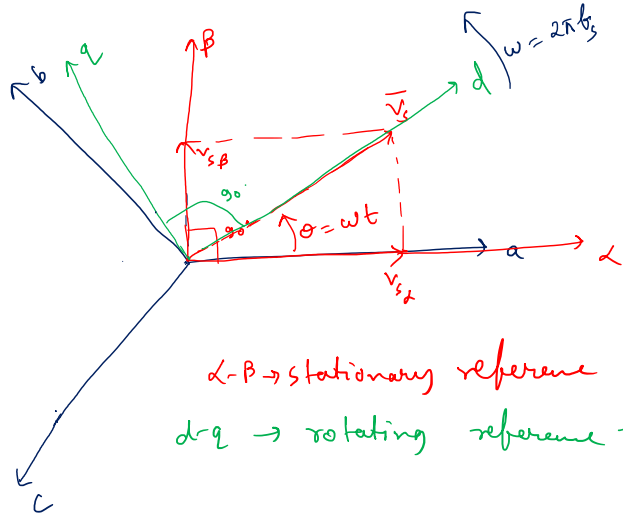


α - β → stationary reference frame
 d - q → rotating reference frame

$$i_{sa} + i_{sb} + i_{sc} = 0$$

3ph → 2-phase → d-q
 α - β

$$v_{sq} = 0$$

→ d-axis is aligned along the \bar{V}_s

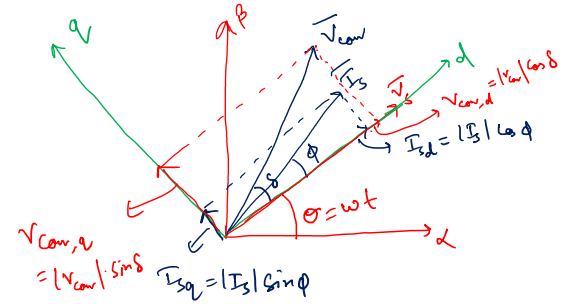


→ cross-coupling

d-axis model,
$$L \frac{d}{dt} I_{sd} + R_s I_{sd} = -V_{cross,d} + \omega L I_{sq} + V_{sd}$$


q-axis model,
$$L \frac{d}{dt} I_{sq} + R_s I_{sq} = -V_{cross,q} - \omega L I_{sd} \rightarrow \text{cross-coupling}$$

Recap

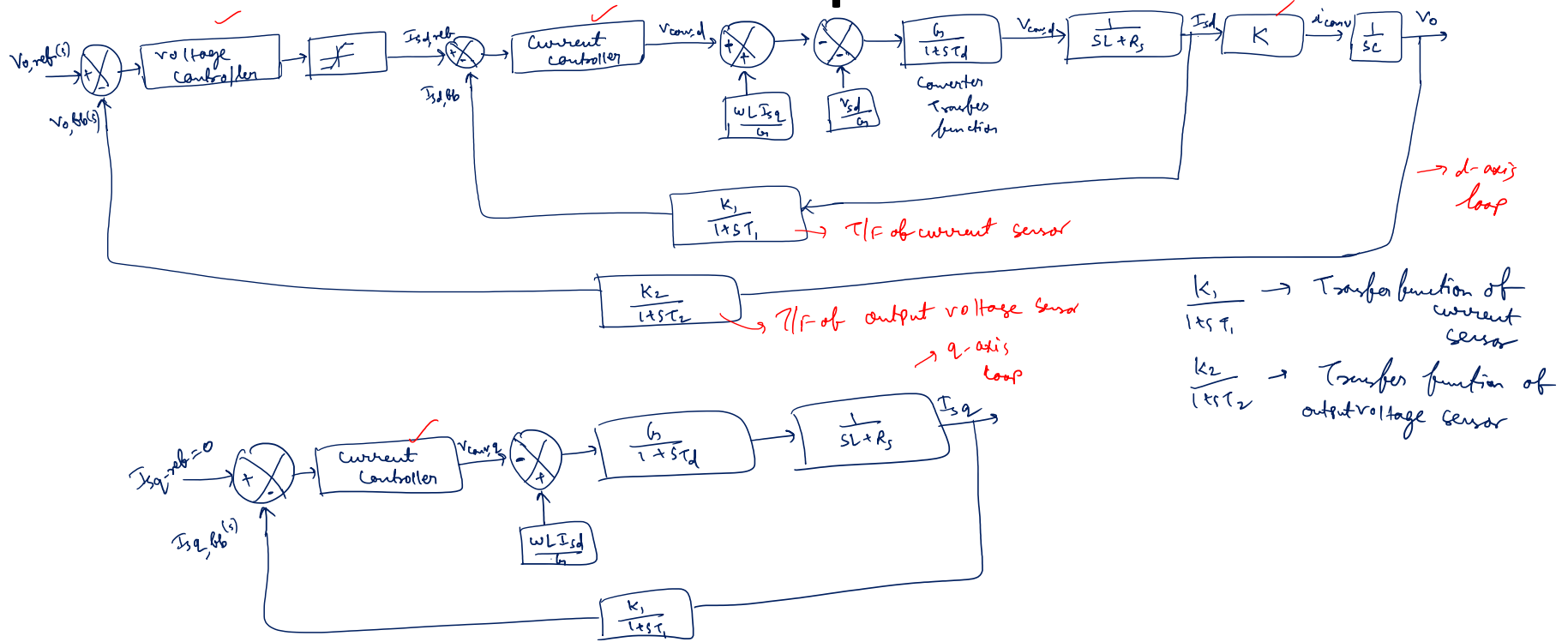

Source: Siva Prasad, J.S., Bhavsar, T., Ghosh, R. *et al.* Vector control of three-phase AC/DC front-end converter. *Sadhana* **33**, 591–613 (2008)

Current loop

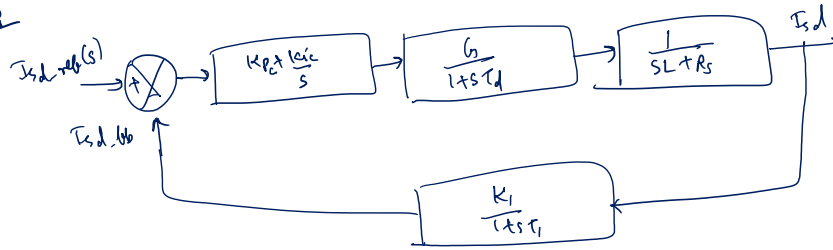

closed-loop T/F

$$\frac{I_{sd}(s)}{I_{sd_ref}(s)} = \frac{G K_{pc}}{L(1+sT_d)s} \cdot \frac{1}{1 + \frac{G K_{pc} K_i}{L(1+sT_d)(1+sT_i)s}}$$

$$\frac{I_{sd}(s)}{I_{sd_ref}(s)} = \frac{G K_{pc} (1+sT_i)}{s(1+sT_d)(1+sT_i)L + G K_{pc} K_i} \rightarrow \textcircled{1}$$

$$(1+sT_d)(1+sT_i) = 1 + s^2 T_d T_i + s(T_d + T_i)$$

$T_d = \frac{T_{sig}}{2}$; T_i is the bandwidth of current sensor $\Rightarrow T_d \& T_i$ are small value $\Rightarrow T_d \cdot T_i \approx \text{very small} \approx 0$

Current controller

$$K_{pc} + \frac{K_{ic}}{s} \Rightarrow \frac{K_{pc} \left(s + \frac{K_{ic}}{K_{pc}} \right)}{s}$$

$$\Rightarrow \frac{1}{sL+R_s} = \frac{1/L}{s + R_s/L} = \frac{1/L}{s + 1/T_s}$$

Where $T_s = L/R_s$

$$\Rightarrow \boxed{\frac{K_{pc}}{K_{ic}} = T_s} \rightarrow \textcircled{A}$$

$$\Rightarrow (1+sT_d)(1+sT_i) = 1 + s(T_d + T_i) \quad (\text{approximated value})$$

$$T_d + T_i = T_o$$

$$\Rightarrow (1+sT_d)(1+sT_i) = 1 + sT_o$$

from eq. ①

$$\frac{I_{sd}(s)}{I_{sd-ref}(s)} = \frac{G_c K_{pc} (1+sT_i)}{s(1+sT_o)L + G_c K_{pc} k_i}$$

$$= \frac{G_c K_{pc} (1+sT_i)}{sL + s^2 T_o L + G_c K_{pc} k_i}$$

$$\frac{I_{sd}(s)}{I_{sd-ref}(s)} = \frac{G_c K_{pc} (1+sT_i)}{T_o L \left(s^2 + \frac{s}{T_o} + \frac{G_c K_{pc} k_i}{T_o L} \right)} \longrightarrow \textcircled{2}$$

we can compare with standard second order closed loop T/F (CLTF)

$\Rightarrow (s^2 + 2\zeta\omega_n s + \omega_n^2)$ denominator of 2nd order CLTF

$$\Rightarrow 2\zeta\omega_n = \frac{1}{T_o} \quad ; \quad \omega_n^2 = \frac{G_c K_{pc} k_i}{T_o L}$$

Source: Siva Prasad, J.S., Bhavsar, T., Ghosh, R. et al. Vector control of three-phase AC/DC front-end converter. *Sadhana* **33**, 591–613 (2008)

$$l_y = 0.707$$

$$\Rightarrow 2 \cdot \frac{1}{\sqrt{2}} \omega_n = \frac{1}{T_o}$$

$$\omega_n^2 = \frac{1}{2T_o^2} \quad ; \quad \omega_n^2 = \frac{G K_{pc} K_i}{T_o L}$$

$$\Rightarrow \boxed{K_{pc} = \frac{L}{2G K_i T_o}} \rightarrow \textcircled{B}$$

from \textcircled{A} & \textcircled{B} we can calculate the current controller Parameters

from eq. $\textcircled{2}$

$$\frac{I_{sd}(s)}{I_{sd,ref}(s)} = \frac{(1+sT_i)}{K_i (2T_o^2 s^2 + 2T_o s + 1)} \quad \begin{array}{l} \text{(putting } \textcircled{B} \text{ in eq. } \textcircled{2}) \\ \text{neglected due to slower outer voltage loop} \end{array}$$


Since our outer voltage loop is a slower loop, thus the dynamics due to zero ($\omega_{z1} = 1/T_i$) & due to s^2 terms in denominator can be neglected

$$\left. \frac{I_{sd}(s)}{I_{sd,ref}(s)} \right|_{\omega_{ref}} = \frac{1}{K_i (2T_o s + 1)} \rightarrow \textcircled{3}$$

Source: Siva Prasad, J.S., Bhavsar, T., Ghosh, R. et al. Vector control of three-phase AC/DC front-end converter. *Sadhana* **33**, 591–613 (2008)



voltage loop

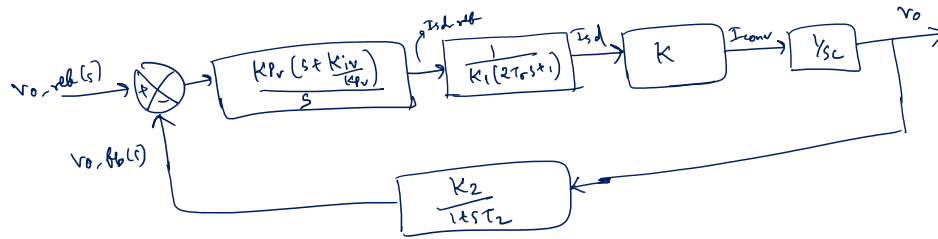

open loop Transfer function (OLTF)

$$\left. \frac{V_o(s)}{v_{o,ref}(s)} \right|_{OLTF} = \frac{K_{pv} \cdot K \cdot K_2 \left(s + \frac{K_{iv}}{K_{pv}} \right)}{s^2 C K_i (1 + 2\tau_o s)(1 + sT_2)} \rightarrow (4)$$

$$(1 + 2\tau_o s)(1 + sT_2) = 1 + 2\tau_o T_2 s^2 + (2\tau_o + T_2)s$$

τ_o & T_2 are small quantities $\Rightarrow \tau_o \cdot T_2 \approx 0$ (very small)

$$\begin{aligned} \Rightarrow (1 + 2\tau_o s)(1 + sT_2) &= 1 + (2\tau_o + T_2)s \quad (2\tau_o + T_2 = T_s) \\ &= 1 + T_s s \end{aligned}$$

$$\left. \frac{v_o(s)}{v_{ref}(s)} \right|_{out F} = \frac{K_{pv} \cdot K \cdot K_2 \left(s + \frac{K_{iv}}{K_{pv}} \right)}{s^2 C \cdot K_1 (1 + s T_g)}$$

$$\omega_c = \sqrt{\frac{K_{iv}}{K_{pv} \cdot T_g}} = \frac{1}{a T_g}$$


$$\Rightarrow a^2 T_g = \frac{K_{pv}}{K_{iv}}$$

$$\Rightarrow \boxed{\frac{K_{pv}}{K_{iv}} = a^2 T_g} \rightarrow \textcircled{C}$$


$$\left. \frac{v_o(s)}{v_{ref}(s)} \right|_{\omega=\omega_c} = 1$$

$$\Rightarrow \boxed{K_{pv} = \frac{C K_1}{K_2 K a T_g}} \rightarrow \textcircled{D}$$

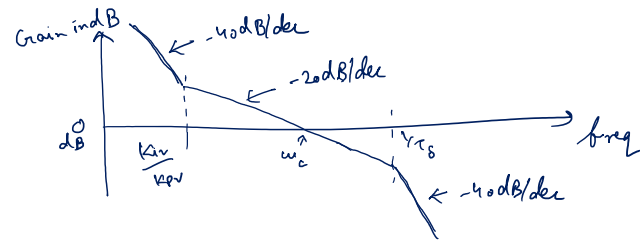from \textcircled{C} & \textcircled{D} voltage controller parameter can be obtained



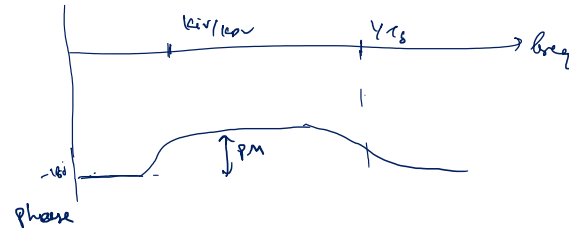\Rightarrow If we cross the 0 dB line with a slope of -20 dB/dec, then high PM can be achieved \Rightarrow stable CL operation



$$\Rightarrow a = 2$$

$$\Rightarrow PM \approx 37^\circ$$

$$\phi_{\omega_c} = \tan^{-1} \left(\omega_c \frac{K_{pv}}{K_{iv}} \right) - \tan^{-1} (\omega_c T_g)$$

$$\Rightarrow \phi_{\omega_c} = \tan^{-1} \left(\frac{1}{a T_g} \cdot a^2 T_g \right) - \tan^{-1} \left(\frac{1}{a T_g} T_g \right)$$

$$\Rightarrow \phi_{\omega_c} = \tan^{-1} (a) - \tan^{-1} \left(\frac{1}{a} \right)$$

$$\Rightarrow PM = 180^\circ + \phi_{\omega_c}$$

$$\Rightarrow a = 2 \Rightarrow PM = 36.86^\circ$$

To obtain 'k'.

$$3\text{-Ph Power} = \frac{3 V_{s, pk} \cdot I_{s, pk}}{2} \rightarrow (1)$$

$$2\text{-Ph Power} = V_{sd} I_{sd} + V_{sq} I_{sq}$$

$$V_{sq} = 0 \text{ \& } I_{sq} = 0$$

$$V_{sd} = \frac{3}{2} V_{s, pk}, I_{sd} = \frac{3}{2} I_{s, pk}$$

$$\Rightarrow 2\text{-Ph Power} = \frac{3}{2} V_{s, pk} I_{s, pk} \rightarrow (2)$$

From (1) & (2)


$$3\text{-Ph Power} = \frac{2}{3} (2\text{-Ph Power}) = I_{con} \cdot V_o$$

$$\Rightarrow \frac{2}{3} (V_{sd} \cdot I_{sd}) = I_{con} \cdot V_o$$

$$\Rightarrow I_{con} = \frac{2}{3} \frac{V_{sd}}{V_o} \cdot I_{sd}$$

$\underbrace{\frac{2}{3} \frac{V_{sd}}{V_o}}_{\rightarrow 'k'}$
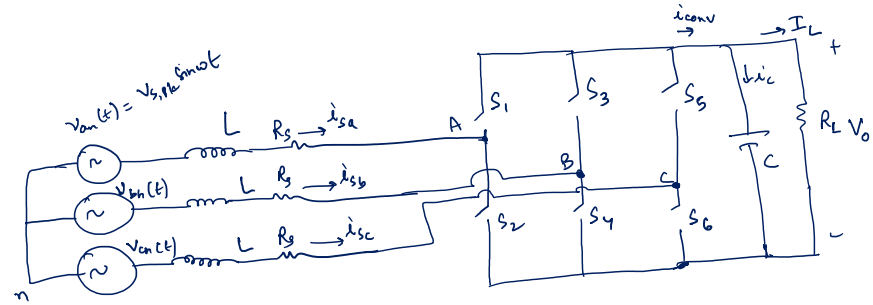
$$\Rightarrow \boxed{k = \frac{2}{3} \frac{V_{sd}}{V_o}}$$



$$K_1 = \frac{\text{Max. voltage of Controller}}{\frac{3}{2} \times \text{Max. value of supply current}}$$

$$K_2 = \frac{\text{Max. voltage of Controller}}{\text{Output voltage}}$$

Thank You

