



IIT ROORKEE



NPTEL ONLINE  
CERTIFICATION COURSE

# Charging Infrastructure

## Lecture-15


### Closed Loop Control of Single-phase Boost PFC Converter-III

Dr. Apurv Kumar Yadav

Department of Electrical Engineering



# Recap

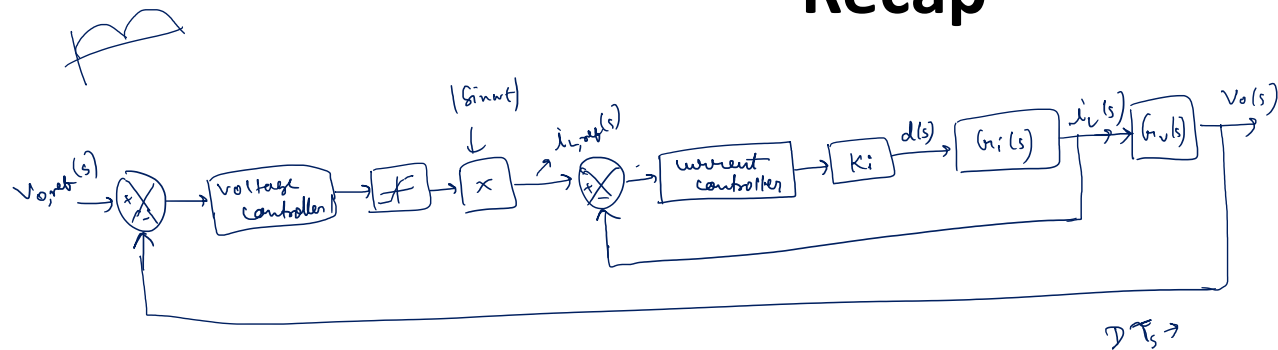

$$G_i(s) = \frac{i_L(s)}{d(s)}$$

$$G_v(s) = \frac{V_o(s)}{i_L(s)} \approx \frac{V_c(s)}{i_L(s)}$$

$$\Rightarrow \tilde{A}_1 = \begin{bmatrix} 0 & 0 \\ 0 & -\frac{1}{R_{LC}} \end{bmatrix}; \tilde{A}_2 = \begin{bmatrix} 0 & -\frac{1}{L} \\ \frac{1}{C} & -\frac{1}{R_{LC}} \end{bmatrix}$$

$$B_1 = B_2 = \begin{bmatrix} \frac{1}{L} \\ 0 \end{bmatrix}; C_1 = C_2 = [0 \ 1]$$

$$D_1 = D_2 = [0]$$

$$\begin{bmatrix} \frac{di_L}{dt} \\ \frac{dv_c}{dt} \end{bmatrix} = \underbrace{\begin{bmatrix} 0 & -\frac{(1-D)}{L} \\ \frac{(1-D)}{C} & -\frac{1}{R_{LC}} \end{bmatrix}}_A \begin{bmatrix} i_L \\ v_c \end{bmatrix} + \underbrace{\begin{bmatrix} \frac{1}{L} \\ 0 \end{bmatrix}}_B |v_s|$$


$$V_o = \underbrace{\begin{bmatrix} 0 & 1 \end{bmatrix}}_C \begin{bmatrix} i_L \\ v_c \end{bmatrix}$$

$$A = A_1 D + A_2 (1-D)$$

$$B = B_1 D + B_2 (1-D)$$

$$C = C_1 D + C_2 (1-D)$$

$$\begin{aligned}
 D &\Rightarrow D + \tilde{d} & (\tilde{d} \ll D) \\
 i_L &\Rightarrow i_L + \tilde{i}_L & (\tilde{i}_L \ll i_L) \\
 v_c &\Rightarrow v_c + \tilde{v}_c & (\tilde{v}_c \ll v_c) \\
 |v_s| &\Rightarrow |v_s| + |\tilde{v}_s| & (|\tilde{v}_s| \ll |v_s|) \\
 v_o &\Rightarrow v_o + \tilde{v}_o & (\tilde{v}_o \ll v_o) \\
 x = \begin{bmatrix} i_L \\ v_c \end{bmatrix} &\Rightarrow x = x + \tilde{x}
 \end{aligned}$$

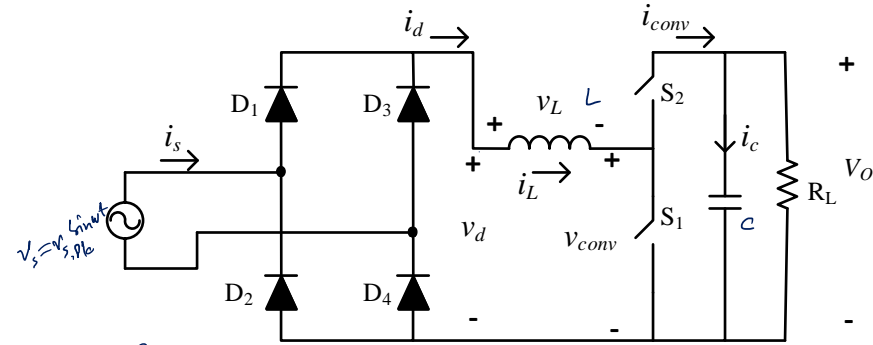

$$\frac{dx + \tilde{x}}{dt} = \left[ A_1 (D + \tilde{d}) + A_2 (1 - D - \tilde{d}) \right] (x + \tilde{x}) + \left[ B_1 (D + \tilde{d}) + B_2 (1 - D - \tilde{d}) \right] (v_s + \tilde{v}_s) \rightarrow (1)$$

$$v_o + \tilde{v}_o = \left[ C_1 (D + \tilde{d}) + C_2 (1 - D - \tilde{d}) \right] (x + \tilde{x}) \rightarrow (2)$$

$$\Rightarrow |\tilde{v}_s| \cdot \tilde{d} = 0 \quad ; \quad \tilde{x} \cdot \tilde{d} = 0 \quad \rightarrow \text{this indicates very small quantities}$$

$$\frac{dx}{dt} + \frac{d\tilde{x}}{dt} = (A_1 D + A_2 (1-D))x + (A_1 D + A_2 (1-D))\tilde{x} + (B_1 D + B_2 (1-D))|v_s| + (B_1 D + B_2 (1-D))|\tilde{v}_s| + [(A_1 - A_2)x + (B_1 - B_2)|v_s|]\tilde{d}$$

$$\frac{dx}{dt} + \frac{d\tilde{x}}{dt} = Ax + A\tilde{x} + B|v_s| + B|\tilde{v}_s| + [(A_1 - A_2)x + (B_1 - B_2)|v_s|]\tilde{d} \rightarrow (3)$$

$$v_o + \tilde{v}_o = Cx + C\tilde{x} + [(C_1 - C_2)x]\tilde{d} \rightarrow (4)$$

$$\begin{cases} |\tilde{v}_s| \cdot \tilde{d} = 0 \\ \tilde{x} \cdot \tilde{d} = 0 \end{cases}$$

linearize the  
State equation in the  
Presence of small  
Perturbation

Steady state terms

$$\frac{dx}{dt} = Ax + B|v_s|$$

$$v_o = Cx$$

$$\frac{dx}{dt} = 0$$

$$\Rightarrow \begin{cases} x = -A^{-1}B|v_s| \\ v_o = -CA^{-1}B|v_s| \end{cases}$$

$\Rightarrow$  A matrix must be an invertible matrix

$$A = \begin{bmatrix} 0 & \frac{-(1-D)}{L} \\ \frac{1-D}{C} & -\frac{1}{R_L C} \end{bmatrix} \Rightarrow A^{-1} = \frac{1}{\frac{(1-D)^2}{LC}} \begin{bmatrix} -\frac{1}{R_L C} & \frac{1-D}{L} \\ -\frac{(1-D)}{C} & 0 \end{bmatrix}; B = \begin{bmatrix} \frac{1}{L} \\ 0 \end{bmatrix}; \tilde{x} = \begin{bmatrix} \tilde{x}_L \\ \tilde{v}_C \end{bmatrix}$$

$$C = [0 \quad 1]$$

$$X = \frac{-1}{\frac{(1-D)^2}{LC}} \begin{bmatrix} -\frac{1}{R_L C} & \frac{(1-D)}{L} \\ -\frac{(1-D)}{LC} & 0 \end{bmatrix} \begin{bmatrix} V_L \\ 0 \end{bmatrix} |V_S|$$

$$X = \frac{-1}{\frac{(1-D)^2}{LC}} \begin{bmatrix} -\frac{1}{R_L C} \\ -\frac{(1-D)}{LC} \end{bmatrix} |V_S|$$

$$\Rightarrow X = \begin{bmatrix} i_L \\ V_C \end{bmatrix} = \begin{bmatrix} \frac{|V_S|}{R_L (1-D)^2} \\ \frac{|V_S|}{1-D} \end{bmatrix} \longrightarrow \textcircled{5}$$

$$\text{from } V_o = \begin{bmatrix} 0 & 1 \end{bmatrix} \begin{bmatrix} \frac{|V_S|}{R_L (1-D)^2} \\ \frac{|V_S|}{1-D} \end{bmatrix}$$

$$\Rightarrow V_o = \frac{|V_S|}{1-D}$$

Small-signal terms

$$B_1 = \begin{bmatrix} 1/L \\ 0 \end{bmatrix}; B_2 = \begin{bmatrix} 1/L \\ 0 \end{bmatrix}$$

$$\frac{d\tilde{x}}{dt} = A\tilde{x} + B(|\tilde{v}_s| + [(A_1 - A_2)x + (B_1 - B_2)|v_s]|)\tilde{d}$$

$$\tilde{v}_o = C\tilde{x} + [(C_1 - C_2)x + \tilde{d}]$$

$$\begin{bmatrix} \frac{d\tilde{i}_L}{dx} \\ \frac{d\tilde{v}_o}{dx} \end{bmatrix} = \begin{bmatrix} 0 & -\frac{(1-D)}{L} \\ \frac{(1-D)}{C} & -\frac{1}{R_{LC}} \end{bmatrix} \begin{bmatrix} \tilde{i}_L \\ \tilde{v}_o \end{bmatrix} + \begin{bmatrix} 1/L \\ 0 \end{bmatrix} |\tilde{v}_s| + \left[ \begin{bmatrix} 0 & 0 \\ 0 & -\frac{1}{R_{LC}} \end{bmatrix} - \begin{bmatrix} 0 & -1/L \\ 1/C & -1/R_{LC} \end{bmatrix} \right] \begin{bmatrix} \frac{|v_s|}{R_L(1-D)^2} + 0 \end{bmatrix} \tilde{d}$$

$$\begin{bmatrix} \frac{d\tilde{i}_L}{dt} \\ \frac{d\tilde{v}_o}{dx} \end{bmatrix} = \underbrace{\begin{bmatrix} 0 & -\frac{(1-D)}{L} \\ \frac{(1-D)}{C} & -\frac{1}{R_{LC}} \end{bmatrix}}_A \underbrace{\begin{bmatrix} \tilde{i}_L \\ \tilde{v}_o \end{bmatrix}}_{\tilde{x}} + \underbrace{\begin{bmatrix} 1/L \\ 0 \end{bmatrix}}_B \underbrace{|\tilde{v}_s|}_{\tilde{x}} + \underbrace{\begin{bmatrix} \frac{|v_s|}{L(1-D)} \\ -\frac{|v_s|}{R_L(1-D)^2} \end{bmatrix}}_K \tilde{d}$$

$$\tilde{v}_o = \underbrace{\begin{bmatrix} 0 & 1 \end{bmatrix}}_C \underbrace{\begin{bmatrix} \tilde{i}_L \\ \tilde{v}_o \end{bmatrix}}_{\tilde{x}} + \underbrace{\begin{bmatrix} 0 & 0 \end{bmatrix}}_Q \underbrace{\begin{bmatrix} \tilde{i}_L \\ \tilde{v}_o \end{bmatrix}}_{\tilde{x}} \cdot \tilde{d}$$

$$\frac{d\tilde{x}}{dt} = A\tilde{x} + B|\tilde{v}_s| + K\tilde{d} \rightarrow (6)$$

$$\tilde{v}_o = C\tilde{x} + D\tilde{d} \rightarrow (7)$$

Apply Laplace Transform in eq. (6)

$$s\tilde{x}(s) = A\tilde{x}(s) + B|\tilde{v}_s(s)| + K\tilde{d}(s)$$

$$\Rightarrow (sI - A)\tilde{x}(s) = B|\tilde{v}_s(s)| + K\tilde{d}(s) \rightarrow (8)$$

$$\text{from eq. (7)} \quad \tilde{v}_o(s) = C\tilde{x}(s) + D\tilde{d}(s) \rightarrow (9)$$

from eq. (8)

$$\left. \frac{\tilde{x}(s)}{\tilde{d}(s)} \right|_{|\tilde{v}_s(s)|=0} = (sI - A)^{-1}K \rightarrow (10)$$

from eq. (9)

$$\left. \frac{\tilde{v}_o(s)}{\tilde{d}(s)} \right|_{|\tilde{v}_s(s)|=0} = C \left. \frac{\tilde{x}(s)}{\tilde{d}(s)} \right|_{|\tilde{v}_s(s)|=0} \rightarrow (11)$$

Substitute eq. (1) in eq. (10)

$$\Rightarrow \left. \frac{\tilde{V}_o(s)}{\tilde{d}(s)} \right|_{\tilde{V}_s(s)=0} = C(SI - A)^{-1}K$$

from eq. (10)

$$\Rightarrow \left. \begin{bmatrix} \frac{\tilde{x}_L(s)}{\tilde{d}(s)} \\ \frac{\tilde{V}_o(s)}{\tilde{d}(s)} \end{bmatrix} \right|_{\tilde{V}_s(s)=0} = (SI - A)^{-1}K$$

$$\Rightarrow \left. \frac{\tilde{x}_L(s)}{\tilde{d}(s)} \right|_{\tilde{V}_s(s)=0} = \frac{|V_s|}{R_L(1-D)^3} \left[ \frac{R_LCs + 2}{\frac{s^2LC}{(1-D)^2} + \frac{SL}{R_L(1-D)^2} + 1} \right] = G_{i1}(s)$$

$$(SI - A)^{-1} = \left( \begin{bmatrix} s & 0 \\ 0 & s \end{bmatrix} - \begin{bmatrix} 0 & -\frac{(1-D)}{L} \\ \frac{1-D}{C} & -\frac{1}{R_LC} \end{bmatrix} \right)^{-1}$$

$$= \begin{bmatrix} s & \frac{(1-D)}{L} \\ -\frac{(1-D)}{C} & s + \frac{1}{R_LC} \end{bmatrix}^{-1}$$

$$(SI - A)^{-1} = \frac{1}{s(s + \frac{1}{R_LC}) + \frac{(1-D)^2}{LC}} \begin{bmatrix} s + \frac{1}{R_LC} & -\frac{(1-D)}{L} \\ \frac{1-D}{C} & s \end{bmatrix}_{2 \times 2}$$

$$K = \begin{bmatrix} \frac{|V_s|}{L(1-D)} \\ -\frac{|V_s|}{R_LC(1-D)^2} \end{bmatrix}_{2 \times 1}$$



# Thank You

