



IIT ROORKEE



NPTEL ONLINE
CERTIFICATION COURSE

Charging Infrastructure


Lecture-33

Switching Loss


Dr. Apurv Kumar Yadav
Department of Electrical Engineering




Recap

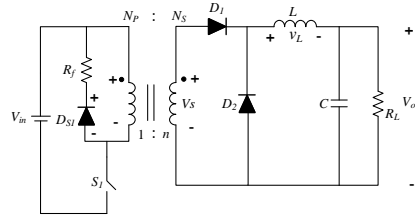


forward converter

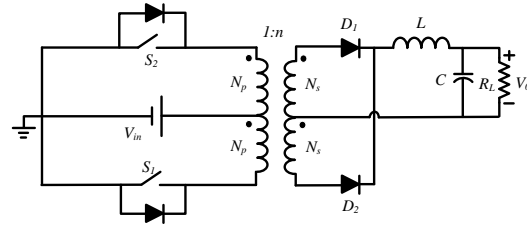

push-pull converter

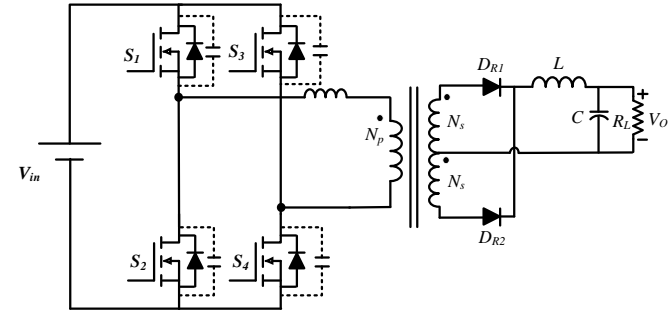


full-bridge

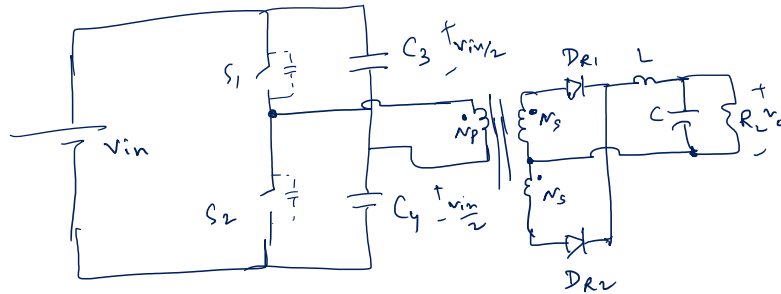

half-bridge

Recap

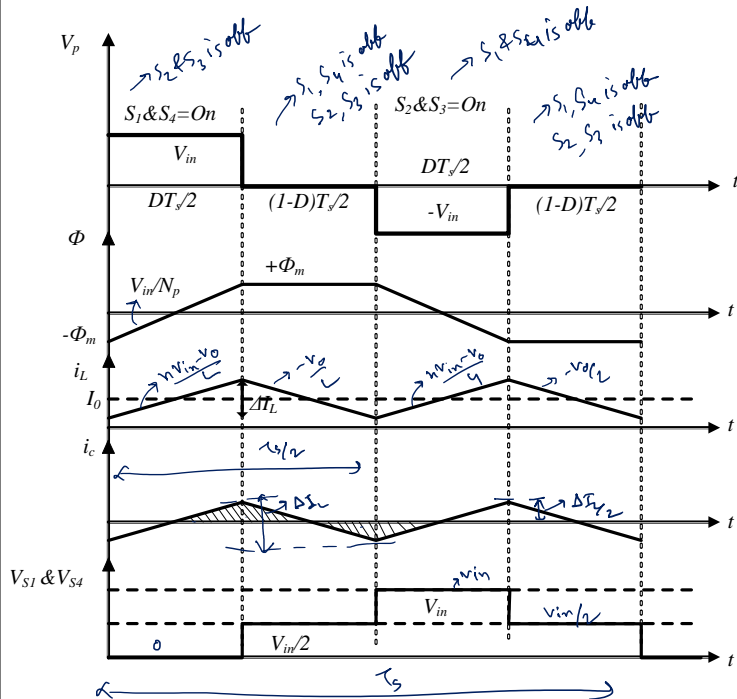

$$\Rightarrow (nV_{in} - v_o) \frac{DT_s}{2} + (-v_o) \frac{(1-D)T_s}{2} = 0$$

$$\Rightarrow v_o = nV_{in}D$$

$$\frac{N_s}{N_p} = n$$

$$\frac{DT_s}{2} \text{ period,}$$

$$v_L = nV_{in} - v_o$$

$$\frac{(1-D)T_s}{2} \text{ period,}$$


$$v_L = -v_o$$

$$\frac{DT_s}{2} \text{ period}$$

$$v_L = nV_{in} - v_o$$



$$\frac{(1-D)T_s}{2} \text{ period}$$

$$v_L = -v_o$$

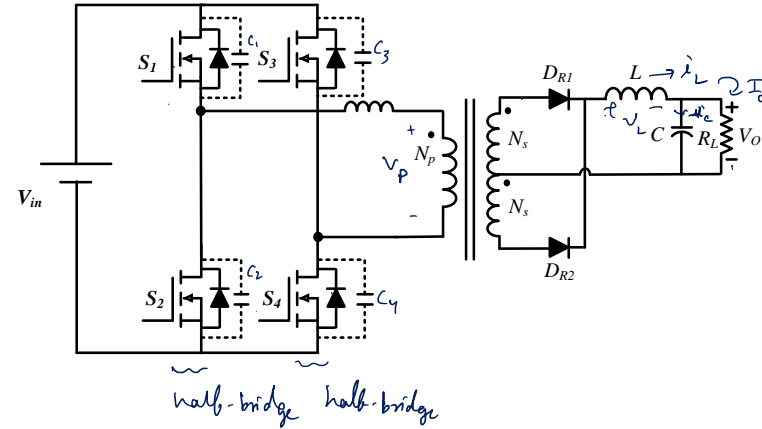

Switching Loss

let us take a simple buck converter

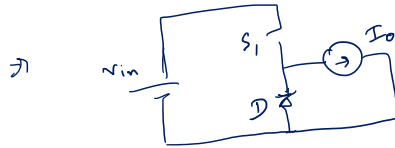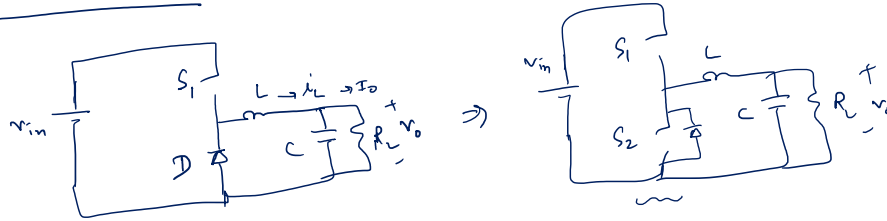

$$f_{sw} \uparrow ; A_c \downarrow ; L \& C \propto \frac{1}{f_{sw}} \Rightarrow$$


Smaller inductor & Capacitor (better)

$$A_c = \frac{V}{N \Delta B \cdot f_{sw}} \Rightarrow L = \frac{n v_{in} D (1-D)}{2 f_{sw} \Delta i_L}$$

$$C = \frac{\Delta i_L}{8 (2 f_{sw}) \cdot \Delta v_o}$$

Size of Power capacitor \propto Size of $L, C, \text{ HF transformer}$
 $f_{sw} \uparrow$; size of Passives \downarrow ; size of Power capacitor \downarrow

Switching Loss

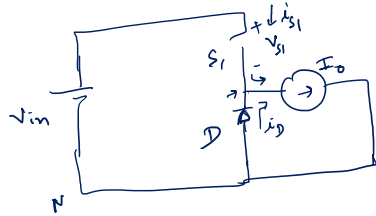

$$I_o = i_{s1} + i_D$$


$$t_{sw(on)} = t_{ri} + t_{fv}$$

When, $0 < t < t_{ri}$

$$\Rightarrow i_{s1}(t) = \frac{I_o}{t_{ri}} \cdot t$$

$$\Rightarrow v_{s1}(t) = V_{in}$$

$$T_s = 1/f_{sw}$$

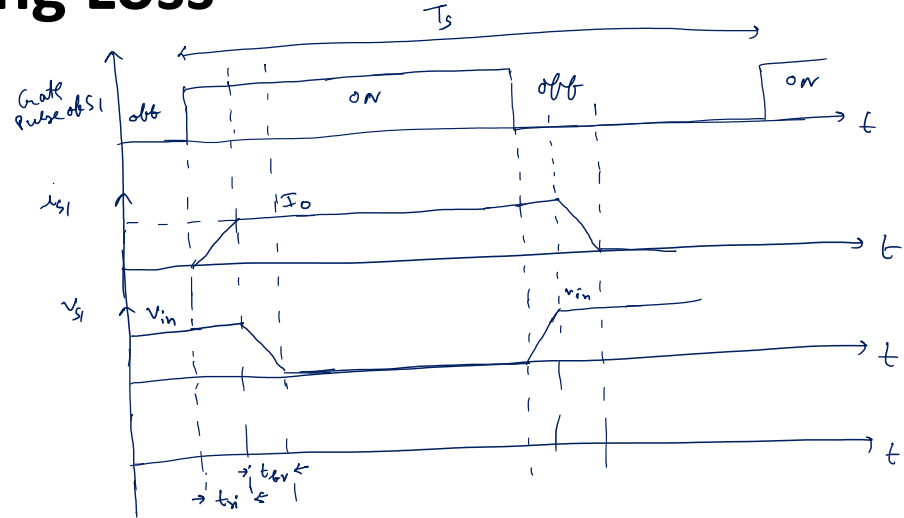

\Rightarrow Energy loss during t_{ri} period

$$E_{tri} = \int_0^{t_{ri}} i_{s1}(t) \cdot v_{s1}(t) \cdot dt$$

$$\Rightarrow E_{tri} = \int_0^{t_{ri}} \frac{I_o}{t_{ri}} \cdot t \cdot V_{in} \cdot dt = \frac{V_{in} I_o}{t_{ri}} \int_0^{t_{ri}} t \cdot dt$$

$$\Rightarrow E_{tri} = \frac{V_{in} I_o}{t_{ri}} \cdot \frac{t_{ri}^2}{2} = \frac{V_{in} I_o}{2} \cdot t_{ri} \longrightarrow \textcircled{1}$$

When $0 < t < t_{br}$

$$i_{S1}(t) = I_0$$

$$v_{S1}(t) = v_{in} - \frac{v_{in} \cdot t}{t_{br}}$$

⇒ Energy loss during t_{br} period

$$\Rightarrow E_{tbr} = \int_0^{t_{br}} v_{S1}(t) \cdot i_{S1}(t) \cdot dt$$

$$= \int_0^{t_{br}} \left(v_{in} - \frac{v_{in} \cdot t}{t_{br}} \right) \cdot I_0 \cdot dt$$


$$= v_{in} I_0 \int_0^{t_{br}} \left(1 - \frac{t}{t_{br}} \right) \cdot dt$$

$$= v_{in} I_0 \left[\int_0^{t_{br}} 1 \cdot dt - \int_0^{t_{br}} \frac{t \cdot dt}{t_{br}} \right]$$

$$= v_{in} I_0 \left[t \right]_0^{t_{br}} - \frac{t^2}{2} \bigg|_0^{t_{br}} = v_{in} I_0 \left[t_{br} - \frac{t_{br}}{2} \right]$$

$$E_{tbr} = \frac{v_{in} I_0 t_{br}}{2}$$

②

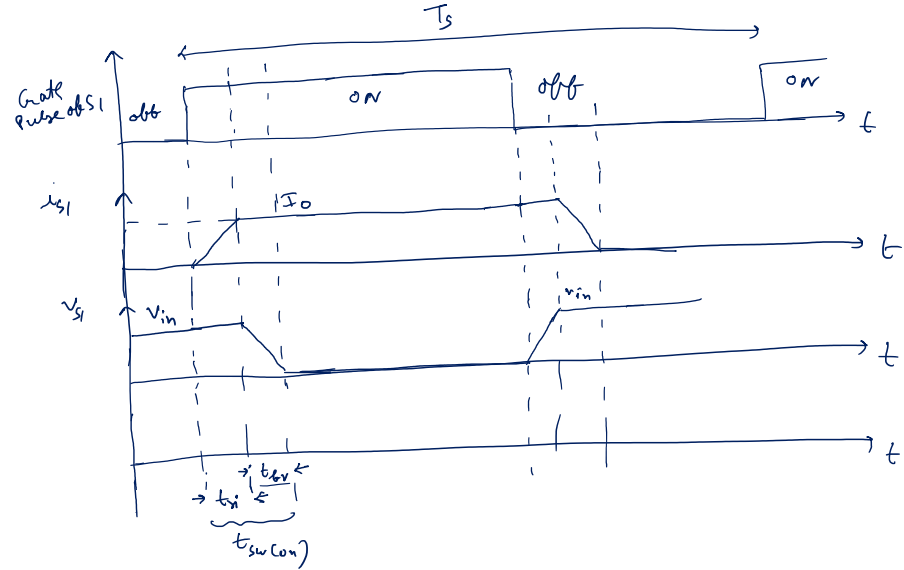


Energy loss during $t_{sw(on)}$

$$E_{on} = E_{tri} + E_{trv} \\ = \frac{V_{in} I_o}{2} (t_{tri} + t_{trv}) \quad (\text{from eq (1) \& (2)})$$

$$E_{on} = \frac{V_{in} I_o}{2} t_{sw(on)}$$

⇒ The power loss during switching on ⇒ $P_{sw,on} = \frac{V_{in} I_o}{2} \frac{t_{sw(on)}}{T_s}$

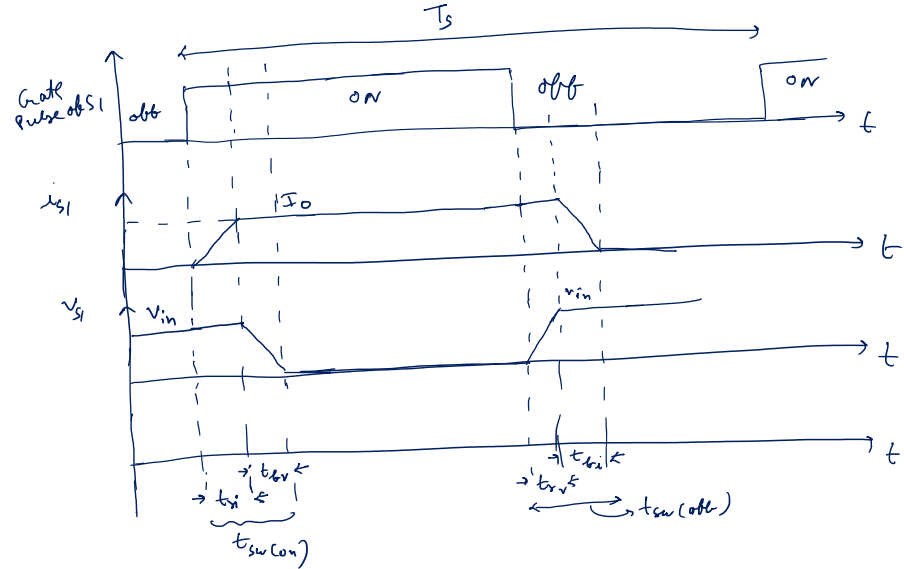⇒ $P_{sw,on} = \frac{V_{in} I_o}{2} t_{sw(on)} f_{sw} \rightarrow (3)$



During Switching-off

when $0 < t < t_{trv}$

$$i_{s1}(t) = I_o \\ v_{s1}(t) = \frac{V_{in} t}{t_{trv}}$$

⇒ Energy loss during t_{trv}

$$E_{trv} = \int_0^{t_{trv}} i_{s1}(t) v_{s1}(t) dt = \int_0^{t_{trv}} I_o \cdot \frac{V_{in} t}{t_{trv}} dt = \frac{V_{in} I_o}{2} \frac{t^2}{t_{trv}} \Big|_0^{t_{trv}} = \frac{V_{in} I_o t_{trv}}{2}$$

$$E_{trv} = \frac{V_{in} I_o t_{trv}}{2}$$



When $0 < t < t_{hi}$

$$\Rightarrow i_{s1}(t) = I_o - \frac{I_o t}{t_{hi}}$$


$$\Rightarrow v_{s1}(t) = V_{in}$$

$$\begin{aligned} \Rightarrow \text{Energy loss during } t_{hi}, E_{thi} &= \int_0^{t_{hi}} i_{s1}(t) \cdot v_{s1}(t) \cdot dt \\ &= \int_0^{t_{hi}} \left(I_o - \frac{I_o t}{t_{hi}} \right) V_{in} \cdot dt \\ &= V_{in} I_o \int_0^{t_{hi}} 1 \cdot dt - \frac{1}{t_{hi}} \int_0^{t_{hi}} t \cdot dt \\ &= V_{in} I_o \left[t \Big|_0^{t_{hi}} - \frac{1}{t_{hi}} \cdot \frac{t^2}{2} \Big|_0^{t_{hi}} \right] \\ &= V_{in} I_o \left[t_{hi} - \frac{t_{hi}}{2} \right] \end{aligned}$$

$$E_{thi} = \frac{V_{in} I_o t_{hi}}{2} \longrightarrow (4)$$


$$\begin{aligned} \Rightarrow \text{Energy loss during turn-off} \Rightarrow E_{sw(off)} &= \frac{V_{in} I_o}{2} (t_{trv} + t_{hi}) \quad (\text{from eq. (3) \& (4)}) \\ &= \frac{V_{in} I_o}{2} t_{sw(off)} \end{aligned}$$
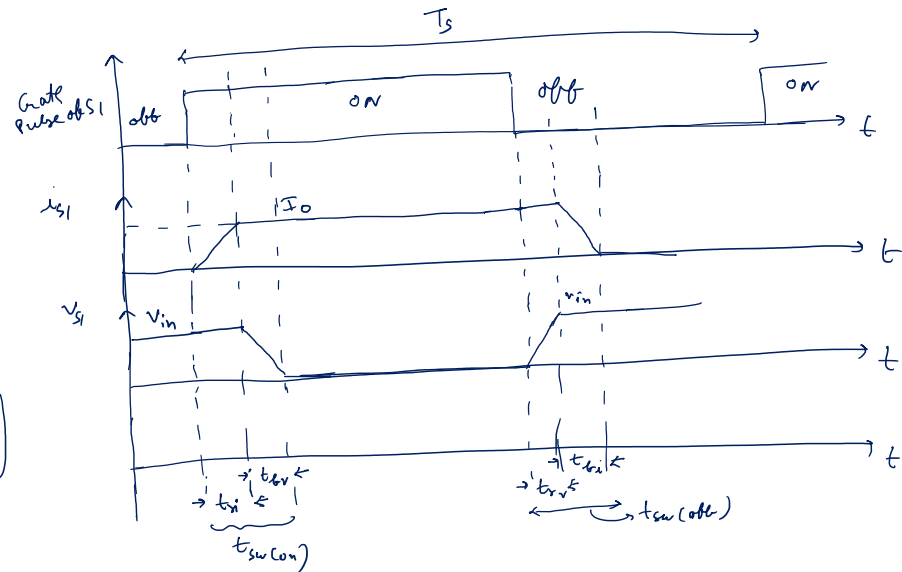
$$\Rightarrow \text{Power loss during turn-off} = \frac{V_{in} I_o}{2} t_{sw(off)} \cdot f_{sw} \longrightarrow (5)$$




⇒ The power loss during switching, $P_{sw} = P_{sw(on)} + P_{sw(off)}$
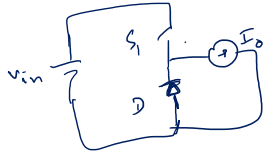
$$P_{sw} = \frac{V_{in} I_o}{2} (t_{sw(on)} + t_{sw(off)}) f_{swo}$$



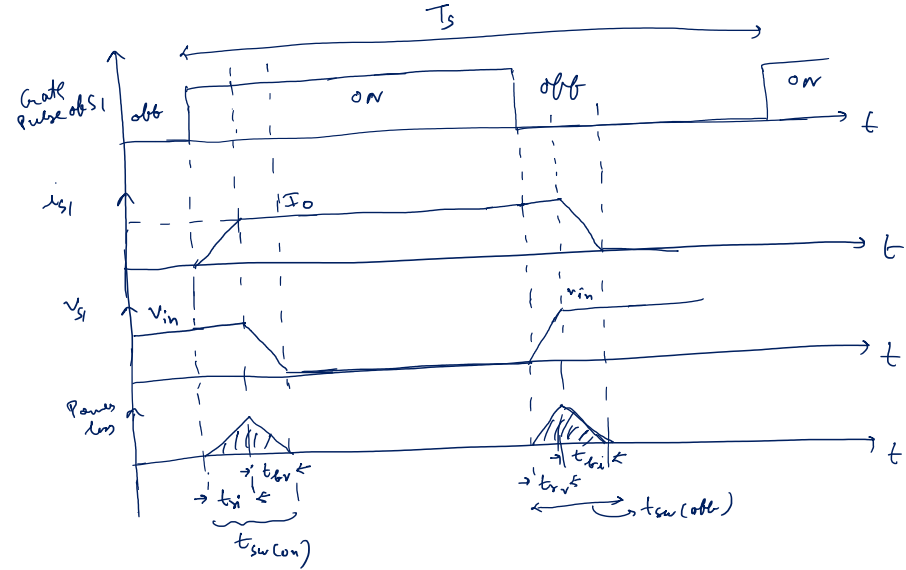- ⇒ Switching loss depends on
- Switching frequency
 - The blocking voltage
 - The current during switching instant
 - time ^{required for} turning on & turning off



Thank You

